

Reference Design RD-353

This user guide supports the reference design for the FAN6920MR, FAN7382, and FAN6204 in a dual-switch flyback application. It should be used in conjunction with the product datasheets as well as Fairchild's application notes and technical support team. Please visit Fairchild's website at www.fairchildsemi.com.

Dual Switch Flyback Solution – 120 W/19 V Design

Featured Device	Application	Input Voltage Range	Output Voltage (Rated Current)	Rated Output Power	Topology
FAN6920MR FAN7382 FAN6204	SMPS AIO PC Power	90~264 V _{AC}	19 V / 6.32 A	120 W	Dual Switch Flyback

Featured Fairchild Products: FAN6920MR, FAN7382, FAN6204

- Ultra-Low Standby Power: Under 0.2 W at 230 V_{AC} meet with 2013 ErP Requirement
- Zero-Current Detection for PFC Stage
- Quasi-Resonant Operation for PWM Stage with 5 ms Soft-Start
- High-Voltage Startup
- Protection Functions (V_{DD} OVP/UVLO, OCP, OLP, Line Voltage Sensing, and OTP)
- Secondary Synchronous Rectifier with CCM/DCM Operation
- No Standby Power Stage Necessary

1. Schematic

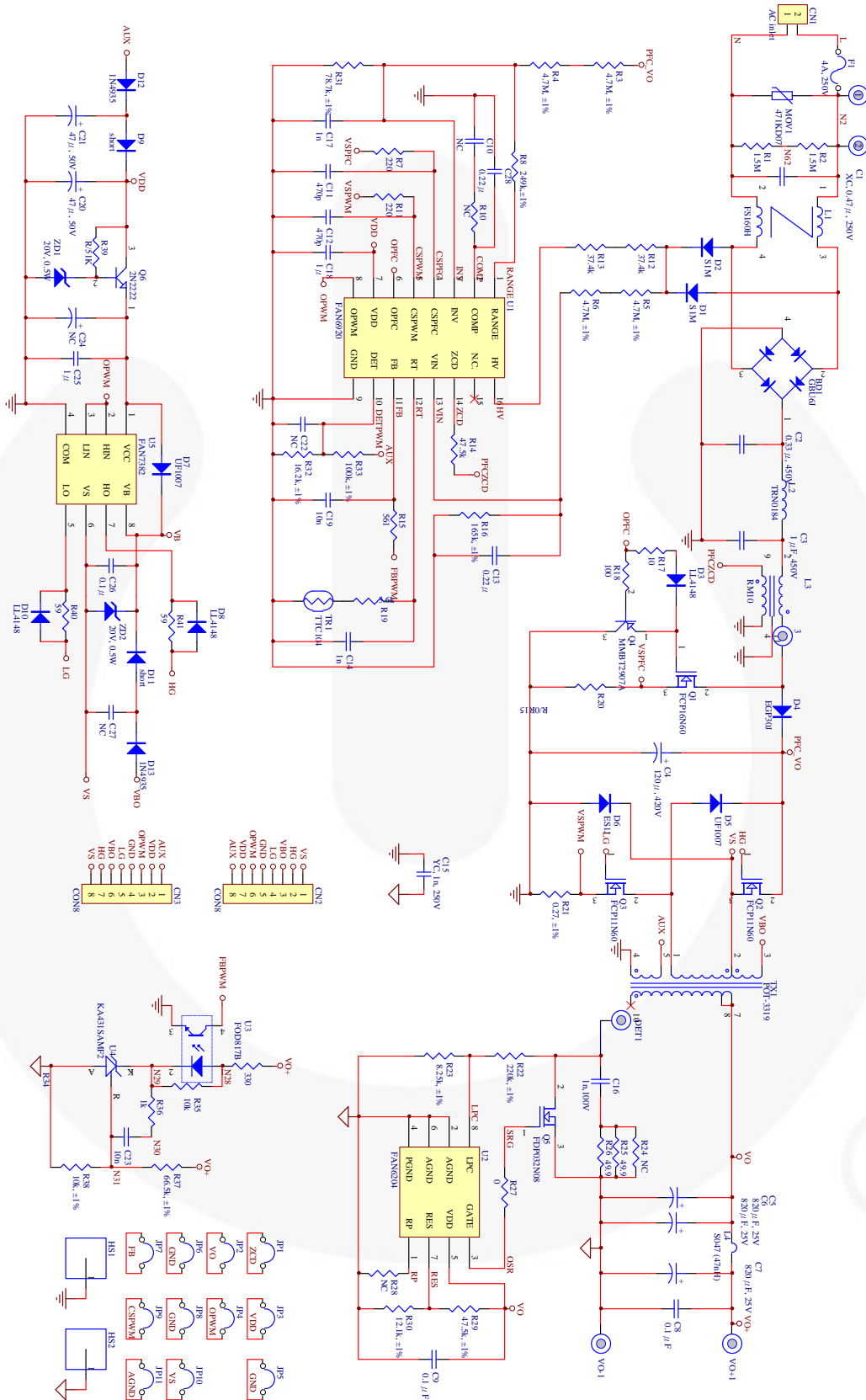


Figure 1. Dual Switch Flyback 120 W Application Schematic

2. Transformer

2.1. Transformer Schematic Diagram

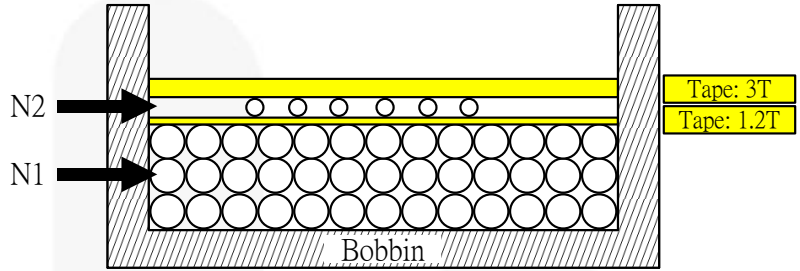
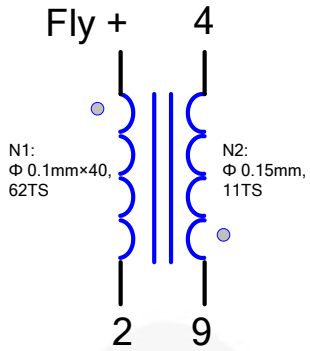


Figure 2. PFC Choke

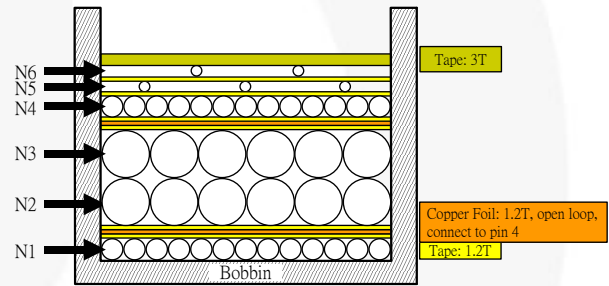
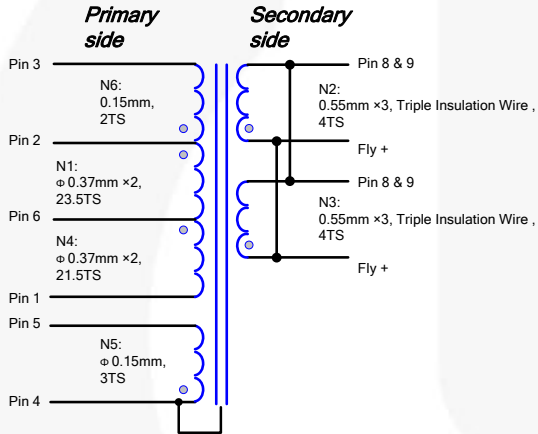


Figure 3. Main Power

2.2. Winding Specification

	Pin (S → F)	Wire	Turns	Isolation Tape	Winding Method
PFC Choke					
N1	2 → Fly+	0.1φ x 40	62	1.2	
N2	4 → 9	0.15φ	11	3	Space Winding
Main Transformer					
	Pin (S → F)	Wire	Turns	Isolation Tape	Winding Method
N1	2 → 6	0.37φ x 2	23.5	1.2	
Shielding	4	Copper Foil	1.2 Open	1.2	
Isolation				1.2	
N2	8,9 → Fly+	0.55φ x 3 Triple Isolation Wire	4		Parallel Winding
N3	8,9 → Fly+	0.55φ x 3 Triple Isolation Wire	4	1.2	Parallel Winding
Shielding	4	Copper Foil	1.2 Open	1.2	
N4	6 → 1	0.37φ x 2	21.5	1.2	
N5	5 → 4	0.15φ	3	1.2	Space Winding
N6	3 → 2	0.15φ	2	3	Space Winding

PFC Choke

- Core: 3C96
- Bobbin: RM-10

Main Transformer

- Core: 3C96
- Bobbin: POT-3319

2.3. Electrical Characteristics

PFC Choke	Pin	Specification	Remark
Primary-Side Inductance	Fly+ - 2	400 μH ±5%	100 kHz, 1 V
Main Transformer	Pin	Specification	Remark
Primary-Side Inductance	1 - 2	1000 μH ±5%	100 kHz, 1 V

3. Typical Performance

3.1. Power Consumption

Output Wattage		Actual Output Wattage	Input Wattage	Specification
No Load	115 V _{AC}		0.168	Input Watt. <0.3 W
	230 V _{AC}		0.190	
0.25 W	115 V _{AC}	0.247	0.456	Input Watt. <0.5 W
	230 V _{AC}	0.247	0.473	
0.5 W	115 V _{AC}	0.502	0.772	Input Watt. <1 W
	230 V _{AC}	0.502	0.776	
1 W	115 V _{AC}	1.011	1.387	Input Watt. <1.7 W
	230 V _{AC}	1.011	1.369	
1.15 W	115 V _{AC}	1.155	1.564	Input Watt. <2.16 W
	230 V _{AC}	1.155	1.538	
1.5 W	115 V _{AC}	1.499	1.980	Input Watt. <2.4 W
	230 V _{AC}	1.499	1.937	
1.7 W	115 V _{AC}	1.704	2.213	Input Watt. <2.4 W
	230 V _{AC}	1.704	2.177	

3.2. Efficiency

Output Wattage	30 W	60 W	90 W	120 W	Avg.	Specification
115 V / 60 Hz	88.42%	92.02%	92.51%	92.18%	91.28%	Avg. > 87%
230 V / 50 Hz	90.15%	91.58%	93.03%	93.51%	92.07%	

Related Resources

[FAN6920MR — Integrated Critical Mode PFC and Quasi-Resonant Current Mode PWM Controller](#)

[FAN7382 — Half Bridge Gate Driver](#)

[FAN6204 — Secondary Synchronous Rectifier Controller for Flyback Topology and Forward Freewheeling Rectification](#)

Reference Design Disclaimer

Fairchild Semiconductor Corporation ("Fairchild") provides these reference design services as a benefit to our customers. Fairchild has made a good faith attempt to build for the specifications provided or needed by the customer. Fairchild provides this product "as is" and without "recourse" and MAKES NO WARRANTY, EXPRESSED, IMPLIED OR OTHERWISE, INCLUDING ANY WARRANTY OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE.

Customer agrees to do its own testing of any Fairchild reference designs in order to ensure design meets the customer needs. Neither Fairchild nor Customer shall be liable for incidental or consequential damages, including but not limited to, the cost of labor, re-qualifications, rework charges, delay, lost profits, or loss of goodwill arising out of the sale, installation or use of any Fairchild product.

Subject to the limitations herein, Fairchild will defend any suit or proceeding brought against Customer if it is based on a claim that any product furnished hereunder constitutes an infringement of any intellectual property rights. Fairchild must be notified promptly in writing and given full and complete authority, information and assistance (at Fairchild's expense) for defense of the suit. Fairchild will pay damages and costs therein awarded against Customer but shall not be responsible for any compromise made without its consent. In no event shall Fairchild's liability for all damages and costs (including the costs of the defense by Fairchild) exceed the contractual value of the products or services that are the subject of the lawsuit. In providing such defense, or in the event that such product is held to constitute infringement and the use of the product is enjoined, Fairchild, in its discretion, shall procure the right to continue using such product, or modify it so that it becomes noninfringing, or remove it and grant Customer a credit for the depreciated value thereof. Fairchild's indemnity does not extend to claims of infringement arising from Fairchild's compliance with Customer's design, specifications and/or instructions, or the use of any product in combination with other products or in connection with a manufacturing or other process. The foregoing remedy is exclusive and constitutes Fairchild's sole obligation for any claim of intellectual property infringement and Fairchild makes no warranty that products sold hereunder will not infringe any intellectual property rights.

All solutions, designs, schematics, drawings, boards or other information provided by Fairchild to Customer are confidential and provided for Customer's own use. Customer may not share any Fairchild materials with other semiconductor suppliers.