

AN1736 Application note

VIPower: VIPer22A dual output reference board 90 to 264 VAC input, 10W output

Introduction

This is an off-line wide range VIPer22A dual outputs power supply at a switching frequency of 60kHz and is set up for secondary regulation with an optocoupler. One output delivers 5V at 1A and while a second output delivers12V at 0.42A, making up the total output power of 10W.

- Switch mode general purpose power supply
- Single-sided board
- 75% efficiency
- Output short circuit protection
- Thermal shutdown protection
- Meets EN55022 class B EMI specification
- Meets Blue Angel

Operating conditions

Parameter	Limits
Input voltage range	90 to 264Vac
Input Frequency Range	50/60 Hz
Output voltages	V1= 5V; V2=12V
Output current	I=0.84A
Output power	10W
Efficiency	75% typical
Line regulation	+/- 0% for 5V output
Load regulation	+/- 0.3% for 5V output
Output ripple voltage	20mVpp
EMI	EN55022 Class B

Contents AN1736

Contents

1	PCB lay-out	5
2	Line regulation	. 6
3	Load regulation	7
4	Efficiency	8
5	Line frequency ripple	. 9
6	Switching frequency ripple	. 10
7	Transient load response	. 11
8	EMI results	. 12
9	Blue Angel	
10	Transformer specification	. 14
11	Output current and voltage capability	. 15
12	Thermal considerations	. 16
13	Component list	. 17
14	Revision history	10

AN1736 List of figures

List of figures

Figure 1.	Board lay-out	5
Figure 2.	Board top legend (not in scale)	5
Figure 3.	Board bottom foil (not in scale)	5
Figure 4.	Line regulation	6
Figure 5.	Load regulation for 5V output	7
Figure 6.	Load regulation for 12V output	7
Figure 7.	Efficiency vs. input voltage	8
Figure 8.	Efficiency vs. Pout	8
Figure 9.	Line ripple for 5V output	9
Figure 10.	Line ripple for 12V output	9
Figure 11.	Switching ripple for 5V output	0
Figure 12.	Switching ripple for 12V output	0
Figure 13.	Transient load response	1
Figure 14.	EMI	2
Figure 15.	Mechanical drawings of the transformer	4
Figure 16.	Schematic diagram 1	8

List of tables AN1736

List of tables

Table 1.	Input power in no load condition at different input voltage	13
Table 2.	Change in output voltage and current	15
Table 3.	Bill of material	17
Table 4.	Revision history	19

AN1736 PCB lay-out

1 PCB lay-out

Figure 1. Board lay-out

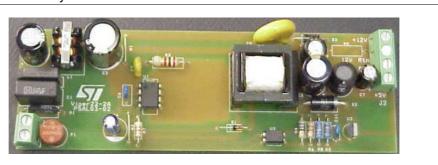


Figure 2. Board top legend (not in scale)


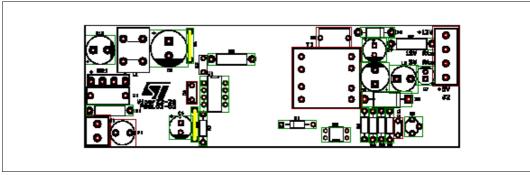


Figure 3. Board bottom foil (not in scale)

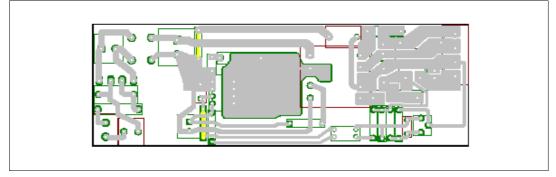


Line regulation AN1736

2 Line regulation

Figure 4. shows the line regulation of both the +5V and the +12V output. The output voltages are measured for the input voltage range of 85 to 264VAC at the maximum output power of 10W. The +5V output shows a 0% line regulation while the +12V output has a line regulation of 0.25%.



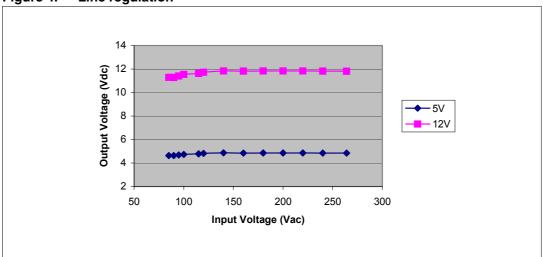

AN1736 Load regulation

3 Load regulation

The load regulation measurements are taken at the input voltage of 120Vac. Here, the load regulation measured for the +5V output is $\pm 0.3\%$ while the +12V output shows a load regulation of $\pm 0.46\%$. See *Figure 5*. and *Figure 6*.

Figure 5. Load regulation for 5V output


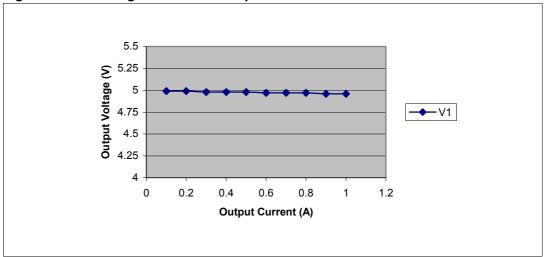


Figure 6. Load regulation for 12V output

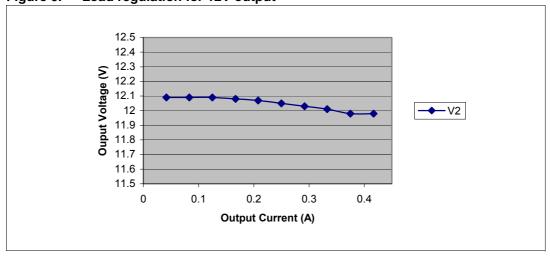


Efficiency AN1736

4 Efficiency


Figure 7. shows the efficiency curve of the reference board when the input voltage is varied from 90 to 264Vac at the maximum output power of 10W. Here, the typical efficiency value is measured to be 75%.

Meanwhile, *Figure 8.* shows the efficiency measurement taken at 120Vac while the output power is varied from 1W to the maximum 10W. The typical efficiency measured is also around 75%.

Figure 7. Efficiency vs. input voltage

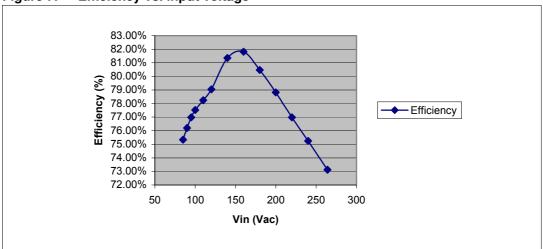



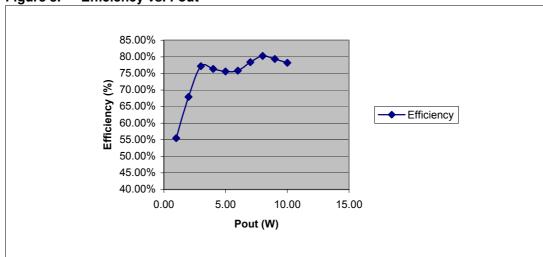

5 Line frequency ripple

Figure 9. Line ripple for 5V output

Figure 10. Line ripple for 12V output


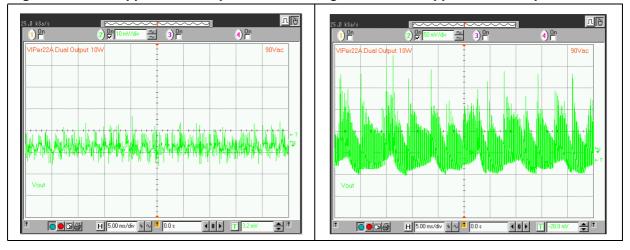


Figure 9. and *Figure 10.* show the line frequency ripple waveforms of the +5V and +12V output respectively taken at 90Vac input. The line frequency ripple for +5V is 10mVpp while for the +12V output; it is 50mVpp.

6 Switching frequency ripple

Figure 11. Switching ripple for 5V output

Figure 12. Switching ripple for 12V output

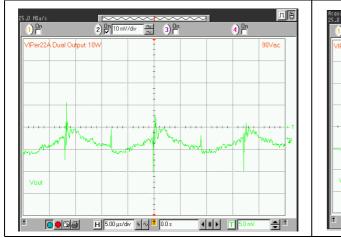




The switching ripple for the +5V output measured is 12mVpp while this ripple measured for the +12V output is 200mVpp. The low ripple for the +5V output is obtained using the low pass LC (PI) filter configuration of L2 and C10. The waveforms are taken at the input voltage of 90Vac.

7 Transient load response

Figure 13. Transient load response

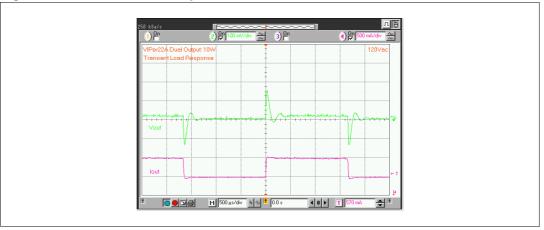


The transient load response is measured at the input voltage of 90Vac where the +5V output load is varied from 50% load (0.5A) to 100% load (1A) while the +12V is kept at the nominal load value of 0.21A. The dynamic response measured is 140mV or 2.8% while the settling time is 500ms. See *Figure 13*.

EMI results AN1736

8 EMI results

Figure 14. EMI

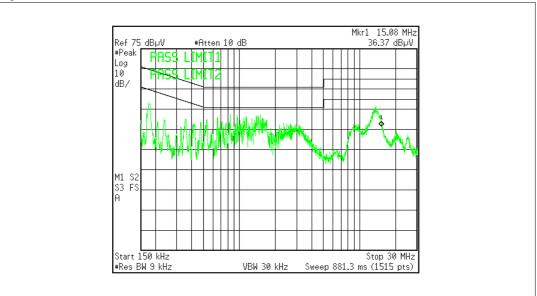

The unit passes the European Norm, EN55022 Class B EMI.

AN1736 Blue Angel

9 Blue Angel

The reference board meets the Blue Angel Norm, consuming less than 1W total when working in stand-by mode. The board operates in burst mode when both the output loads are reduced to zero and the output voltages still remain regulated.

9.1 Stand-by input power


Table 1. Input power in no load condition at different input voltage

Input Voltage	Input Wattage at No Load
115Vac	210.38mW
230Vac	331.85mW

At the input voltage of 120Vac, a minimum load of 100mA is needed to keep the total input power consumption to be less than 1W.

10 Transformer specification

Figure 15. Mechanical drawings of the transformer

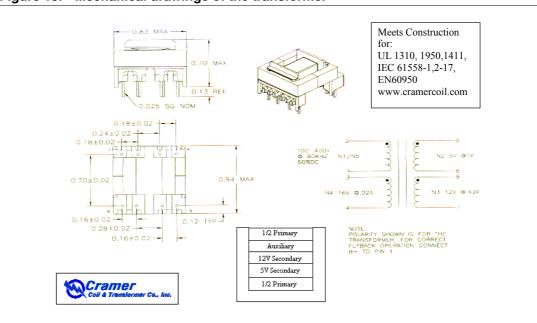

When the VIPer22A (U1) is on, energy is stored in the primary winding of transformer (1-2), TX1. This energy is transferred to the auxiliary winding (3-4), and to the output (5-6) when the VIPer22A is off. The auxiliary winding provides the bias voltage for the VIPer22A at pin 4 (Vdd).

The electrical specifications of the transformer are as follow:

- Primary Inductance 2.25mH±15%
- Primary Leakage Inductance 22μH typical
- Turns Ratio (N1/N5:N2) 1:0.053
- Turns Ratio (N1/N5:N3) 1:0.127
- Turns Ratio (N1/N5:N4) 1:0.167

The transformer is designed and manufactured by Cramer Coil and Transformer.

11 Output current and voltage capability

The standard voltage and current values for the reference board can be changed to deliver a different voltage and current value, with changes to the following components as detailed in *Table 2*.

Table 2. Change in output voltage and current

Output Voltages	T1	C9
5 and 12V	CVP32-002	220μF/25V
5 and 15V	CVP32-003	220μF/35V
5 and 24V	CVP32-004	220μF/50V

Thermal considerations AN1736

12 Thermal considerations

The reference board is single-sided and utilizes a wide area of two ounces copper pad to act as a heat sink for the VIPer22ADIP. All other traces utilize one-ounce copper.


AN1736 Component list


13 Component list

Table 3. Bill of material

Quantity	Reference	Description	
1	BR1	KBP210GDI	
1	C1	0.047μF/250V boxcap	
1	C2	22μF/400V electrolytic	
1	C3	100pF 1kV ceramic	
1	C4	22μF/25V electrolytic	
1	C5	680μF/25V electrolytic	
1	C6	22nF/50V ceramic	
1	C7	100μF/25V electrolytic	
1	C8	4.7nF/250V Y cap	
1	C9	210μF/25V electrolytic	
1	C11	0.01μF/50V ceramic	
1	C12	10μF/400V electrolytic	
1	D1	1N4148	
1	D2	1N5821	
1	D3	STMicroelectronics BYW100-200	
1	F1	0.5A 250V Fuse	
2	J1, J2	Connectors	
1	L1	Compostar 2x30mH common-mode line choke	
1	L2	Coilcraft 10μH inductor	
1	R1	$5\Omega5\%$ 1W Wire wound	
1	R2	2KΩ5% 1/2W	
1	R4	68Ω5% 1/4W	
1	R5	2.438KΩ1% 1/4W	
1	R6	470Ω5% 1/4W	
1	R7	R7 9.1kΩ5% 1/4W	
1	R8	2.49KΩ1% 1/4W	
1	R9	15KΩ5% 1/2W	
1	T1	T1 Cramer coil transformer CVP32-002	
1	U1	STMicroelectronics VIPer22ADIP	
1	U2	H11A817A or LTV817 optocoupler	
1	U3	STMicroelectronics TL431	
2	W1, W2	Jumper wire	

Component list AN1736

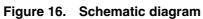

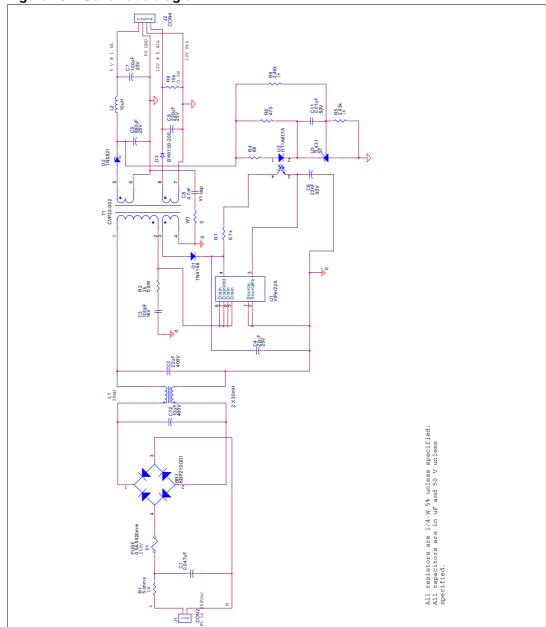

AN1736 Revision history

14 Revision history

Table 4. Revision history

Date	Revision	Changes
16-Jul-2003	1	First issue
13-Jun-2005	2	- Schematic changed - Component list table modified
09-Sep-2005	3	Schematic modified
31-Jul-2006	4	- New template - Component list value modified

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2006 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com