



AN2001

Application note

VIPower: VIPer53 single output reference board 90 to 264 VAC input, 24W output

Introduction

The VIPer53 combines an enhanced current mode PWM controller with a high voltage MDMesh Power Mosfet in the same package. VIPer53 is available in two different packages, DIP-8 and PowerSO-10. This reference board is an offline wide range power supply that incorporates VIPer53 and is set up for secondary regulation by driving the PWM controller through an optocoupler. The switching frequency is set at 100 kHz and the total output power is 24W.

- Switch mode general purpose power supply
- Current mode control with adjustable limitation
- 75% efficiency
- Output short circuit and overload protection
- Thermal shutdown protection
- Meets EN55022 class B EMI specification
- Blue Angel compliant

Operating conditions

Parameter	Limits
Input voltage range	90 to 264Vac
Input Frequency	100kHz
Output voltage	V=12V
Output power	24W
Efficiency	75% typical
Line regulation	+/- 0
Load regulation	+/- 0.2%
Output ripple voltage	15mVpp
EMI	EN55022 Class B

Contents

1	PCB lay-out	5
2	Efficiency	6
3	Load regulation	7
4	Line regulation	8
5	Transient response	9
6	Line and switching frequency ripple	10
7	Waveforms	11
8	Blue Angel	12
9	EMI results	13
10	Transformer specification	14
11	Different output current and voltage capability	15
12	Revision history	18

List of figures

Figure 1.	Board layout (not in scale)	5
Figure 2.	Efficiency vs. I _{out}	6
Figure 3.	Efficiency vs. V _{in}	6
Figure 4.	Load regulation	8
Figure 5.	Line regulation	8
Figure 6.	Transient response	9
Figure 7.	Line frequency ripple	10
Figure 8.	Switching frequency ripple	10
Figure 9.	V _{ds} and drain current	11
Figure 10.	EMI	13
Figure 11.	Transformer specifications	14
Figure 12.	PC board top legend (not in scale)	15
Figure 13.	PC board bottom copper (not in scale)	15
Figure 14.	Schematic diagram	17

List of tables

Table 1. Secondary component value to obtain different output voltage and current. 15

Table 2. Component list 15

Table 3. Revision history 18

Obsolete Product(s) - Obsolete Product(s)

2 Efficiency

Figure 2. and *Figure 3.* shows the two efficiency curves of the reference board. The measurements on *Figure 2.* are taken at the input voltage of 120Vac while the output load is varied from 0A to the full load of 2A. Meanwhile, *Figure 3.* shows the efficiency when the input voltage is varied from 90 to 264Vac while the output load is fixed at 2A.

Figure 2. Efficiency vs. I_{out}


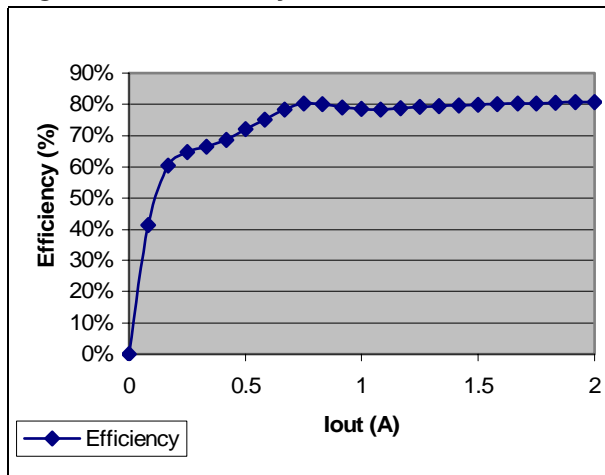


Figure 3. Efficiency vs. V_{in}

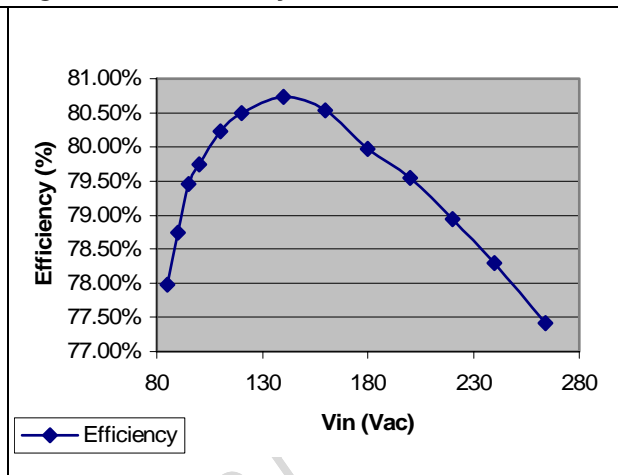

3 Load regulation

V_{out} is measured while the output load is varied from 0A to 2A at the nominal input voltage of 120Vac. [Figure 4.](#) shows the load regulation measured, which is 0.2%.

Obsolete Product(s) - Obsolete Product(s)

4 Line regulation

The line regulation is measured to be 0%. Here, the output load is kept at the full load of 2A while the input voltage is varied from 90 to 264V and the output voltage for the reference board remains regulated.

Figure 4. Load regulation


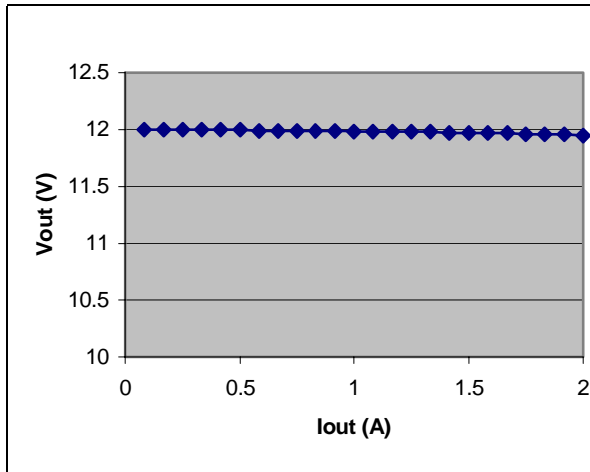


Figure 5. Line regulation

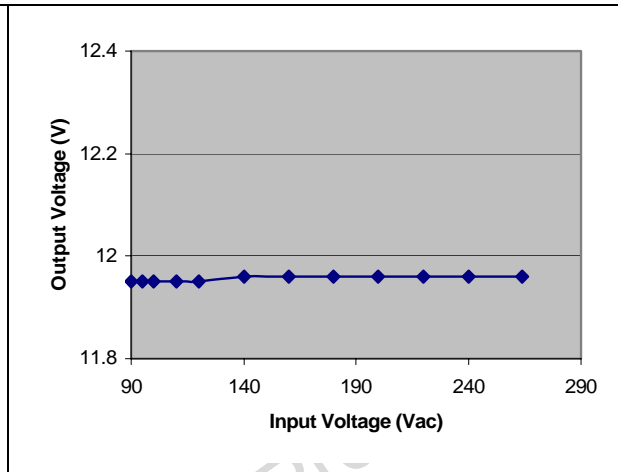

5 Transient response

Figure 6. Transient response

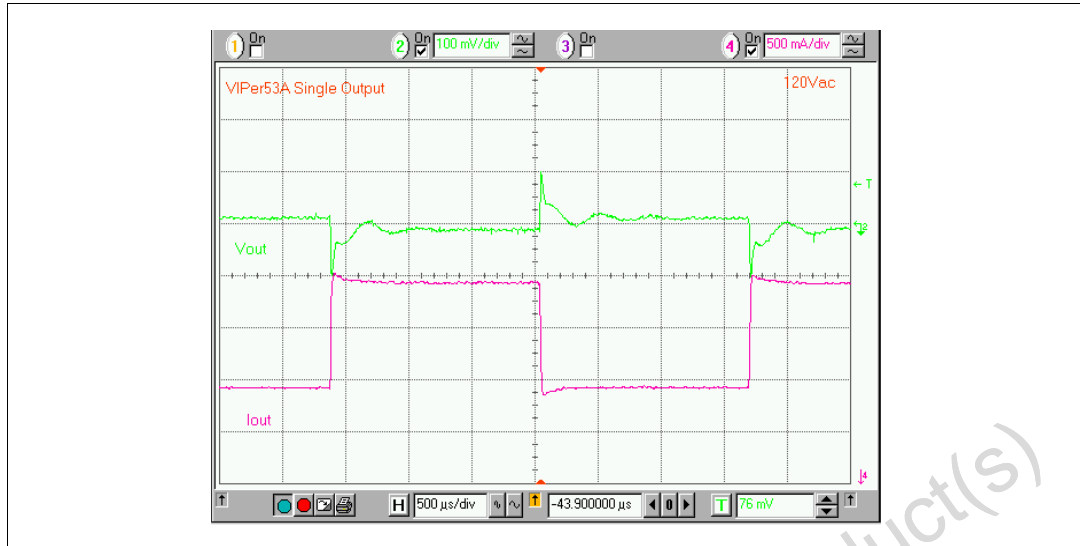


Figure 6. shows the transient load response as the output load is stepped from 1A to 2A (50% to 100% load) at the input voltage of 120Vac. The dynamic response is 80mV or 0.7% while the settling time is found to be 420µs.

6 Line and switching frequency ripple

Figure 7. and *Figure 8.* show the line and switching frequency ripple of the reference board measured at the input voltage of 120Vac and the output current is fixed at 2A.

Figure 7. Line frequency ripple


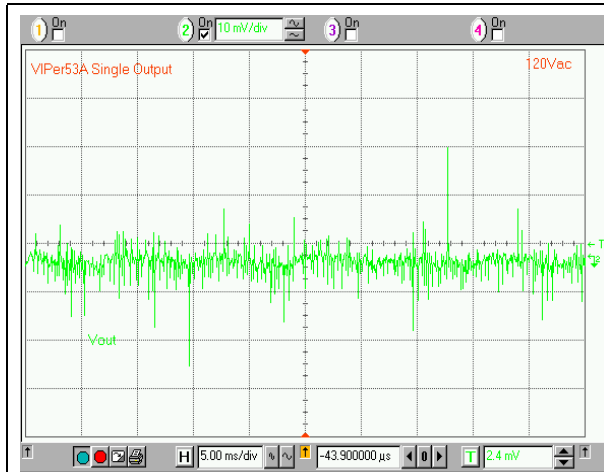


Figure 8. Switching frequency ripple

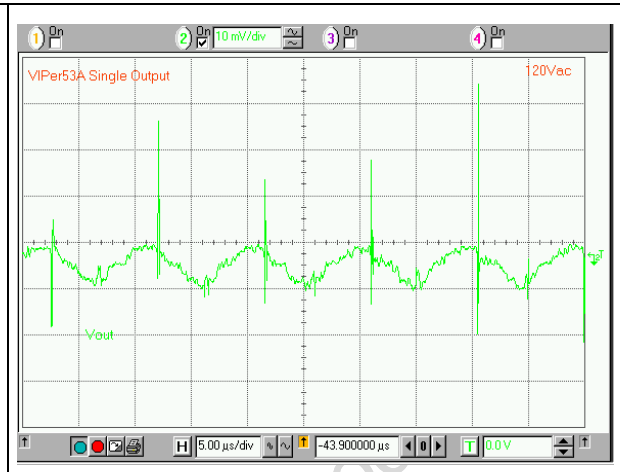


Both waveforms show a line frequency and switching frequency ripple of 10mVpp each.

7 Waveforms

Figure 9. shows the drain current and V_{ds} at 230Vac full load. The converter is working in discontinuous mode as can be seen from the waveforms.

Figure 9. V_{ds} and drain current

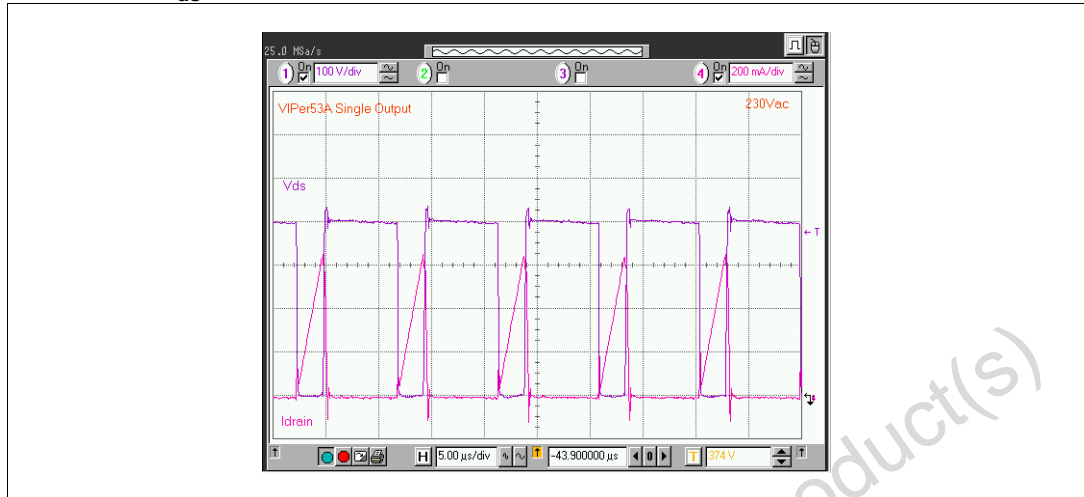

8 Blue Angel


The reference board consumes less than 1W total when working in stand-by burst mode at the input voltage of 120Vac. The measured input power consumption is 569mW with zero loads at the output.

Therefore, the board meets Blue Angel norm.

Obsolete Product(s) - Obsolete Product(s)

9 EMI results


Figure 10. EMI

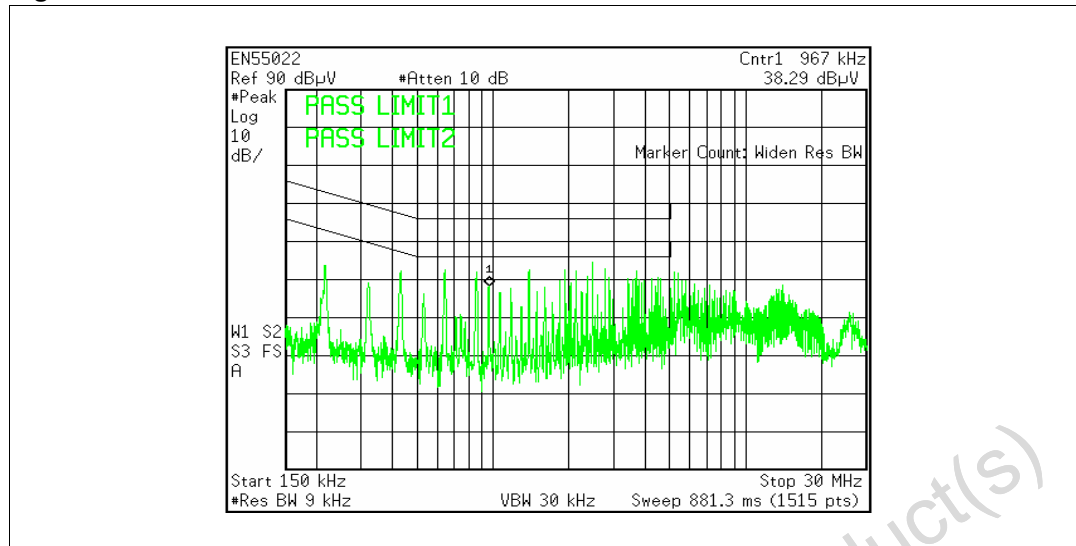

The reference board passes the EN55022 Class B EMI test as shown in [Figure 10](#).

10 Transformer specification

Figure 11. Transformer specifications

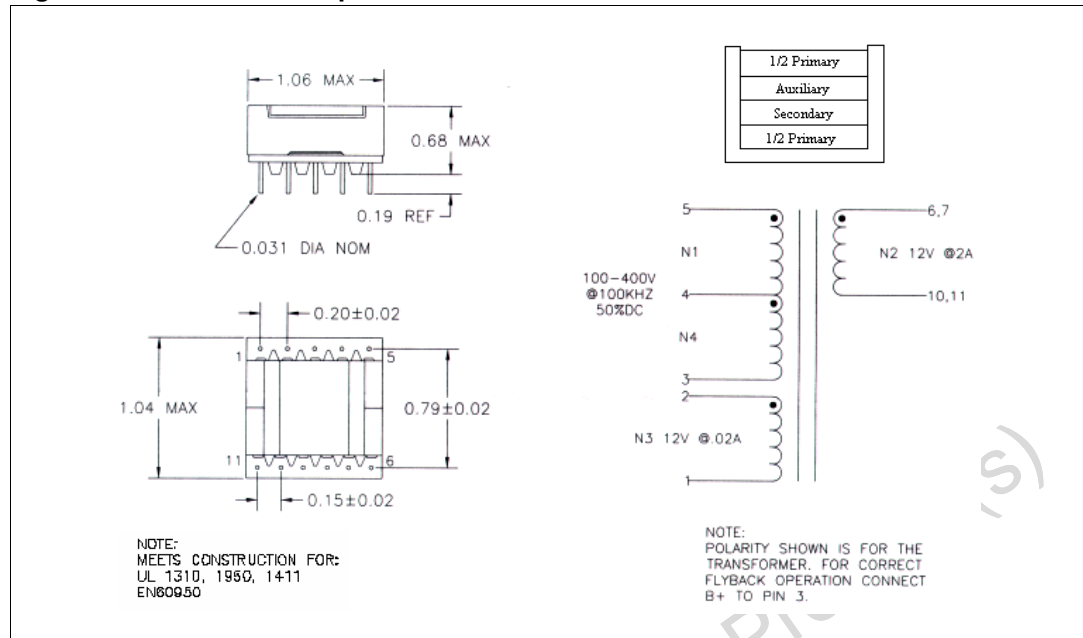

The transformer is designed and manufactured by Cramer Coil and Transformer Co., Inc. The electrical characteristics of the transformer are as follows:

The electrical specifications of the transformer are as follow:

- Primary Inductance $1.10\text{mH} \pm 10\%$
- Primary Leakage Inductance $6.4\mu\text{H}$ typical
- HIPOT (N1, N3, N4 to N2) 4000VAC, 1sec
- DCR (N1/N4) $0.905\ \Omega$ typical
- DCR (N2) $0.020\ \Omega$ typical
- DCR (N3) $0.112\ \Omega$ typical
- Turns Ratio (N1/N4:N2) $1:0.121 \pm 3\%$
- Turns Ratio (N1/N4:N3) $1:0.121 \pm 3\%$

When VIPer53 is on, energy is stored in the primary winding of the transformer (pins 3-5). This energy is transferred to the auxiliary winding (pins 1-2), and to the output (6, 7-10, 11) when the VIPer53 is off. The auxiliary winding provides the bias voltage for the VIPer53 at pin 7 (Vdd).

11 Different output current and voltage capability

The standard voltage and current values for the reference board can be changed to deliver a different voltage and current value, with changes to the following components as detailed in [Table 1](#).

Table 1. Secondary component value to obtain different output voltage and current

Vout and Iout	T1	R6	R9	C8, C16	D4
5.0V 4.8A	CVP53-003	2.49k Ω 1%	2.49k Ω 1%	3300 μ F 10V	STPS1045
12V 2.0A	CVP53-001	3.48k Ω 1%	13.3k Ω 1%	1000 μ F 25V	BYW98-200
15V 1.6A	CVP53-004	2.94k Ω 1%	14.7k Ω 1%	1000 μ F 35V	BYW98-200
24V 1.0A	CVP53-005	1.50k Ω 1%	13.0k Ω 1%	470 μ F 50V	BYW98-200

Figure 12. PC board top legend (not in scale)

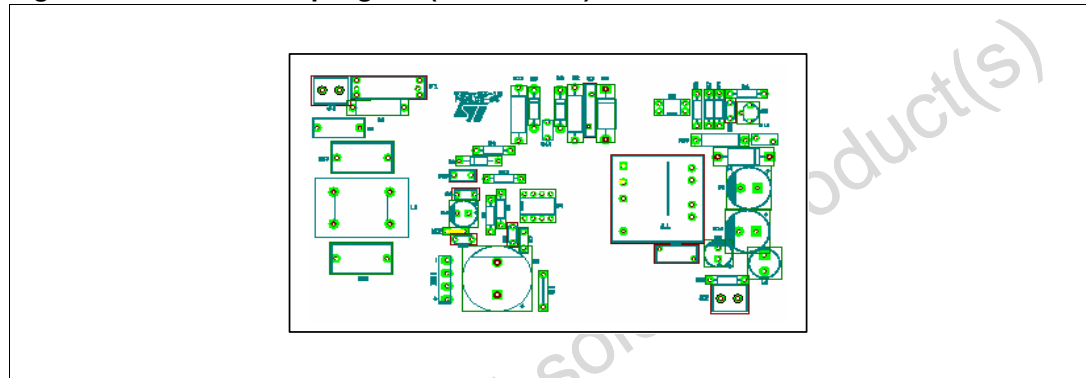


Figure 13. PC board bottom copper (not in scale)

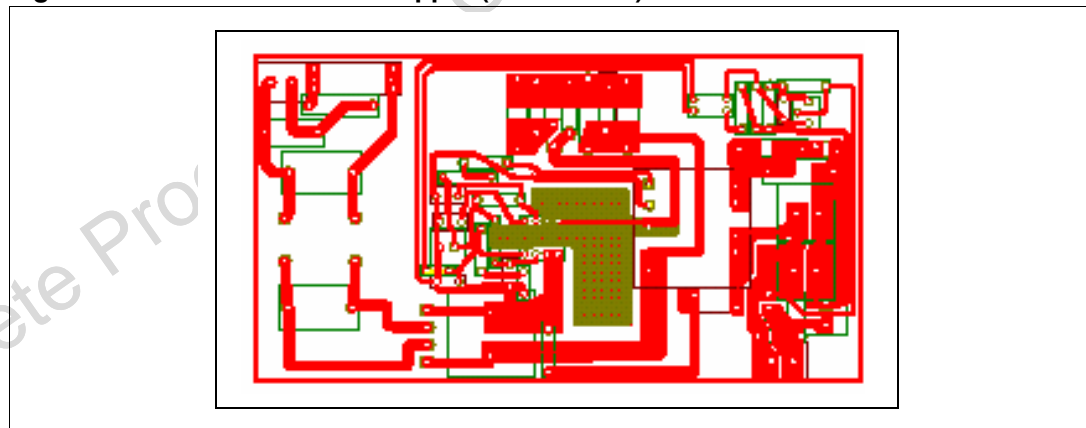


Table 2. Component list

Quantity	Reference	Description
1	BR1	KBP210GDI bridge rectifier
1	C1	0.047 μ F 250V boxcap
1	C2	68 μ F/400V electrolytic


Table 2. Component list

Quantity	Reference	Description
1	C3	4700pF 1kV ceramic
1	C4	100μF/25V electrolytic
1	C5	4.7nF 50V polyester
2	C6, C7	470nF 50V ceramic
2	C8, C16	1000μF/25V electrolytic
1	C9	220μF/25V electrolytic
1	C10	4.7nF/250V Y1 cap
2	C11, C12	0.01μF 50V ceramic
1	C13	470pF/1kV ceramic
1	C14	100pF/1kV ceramic
1	C15	Not used
2	C17, C18	0.33μF/250V boxcap
1	L1	Panasonic 35mH common-mode line choke
1	L2	Coilcraft 2.2μH inductor
1	T1	Cramer Coil CVP53-001
1	R1	4Ω 5% 3W Wire wound
1	R2	22kΩ 5% 2W resistor
1	R3	3kΩ 5% 0.5W resistor
1	R4	15Ω 5% 0.25W resistor
1	R5	3.3kΩ 5% 0.25W resistor
1	R6	3.48kΩ 1% 0.25W resistor
1	R7	1kΩ 5% 0.25W resistor
1	R8	68Ω 5% 0.25W resistor
1	R9	13.3kΩ 1% 0.25W resistor
1	R10	22Ω 5% 0.5W resistor
1	R12	1kΩ 5% 2W resistor
1	R13	Not used
1	D1	1N4148
2	D2, D3	STMicroelectronics STTH1R06
1	D4	STMicroelectronics BYW98-200
1	D5	STMicroelectronics 1.5KE220A transil
1	U2	H11A817A or LTV817A optocoupler
1	U3	STMicroelectronics TL431
1	U4	STMicroelectronics VPer53DIP

Table 2. Component list

Quantity	Reference	Description
2	W1, W2	Jumper wire
2	J1, J2	Connectors

Figure 14. Schematic diagram

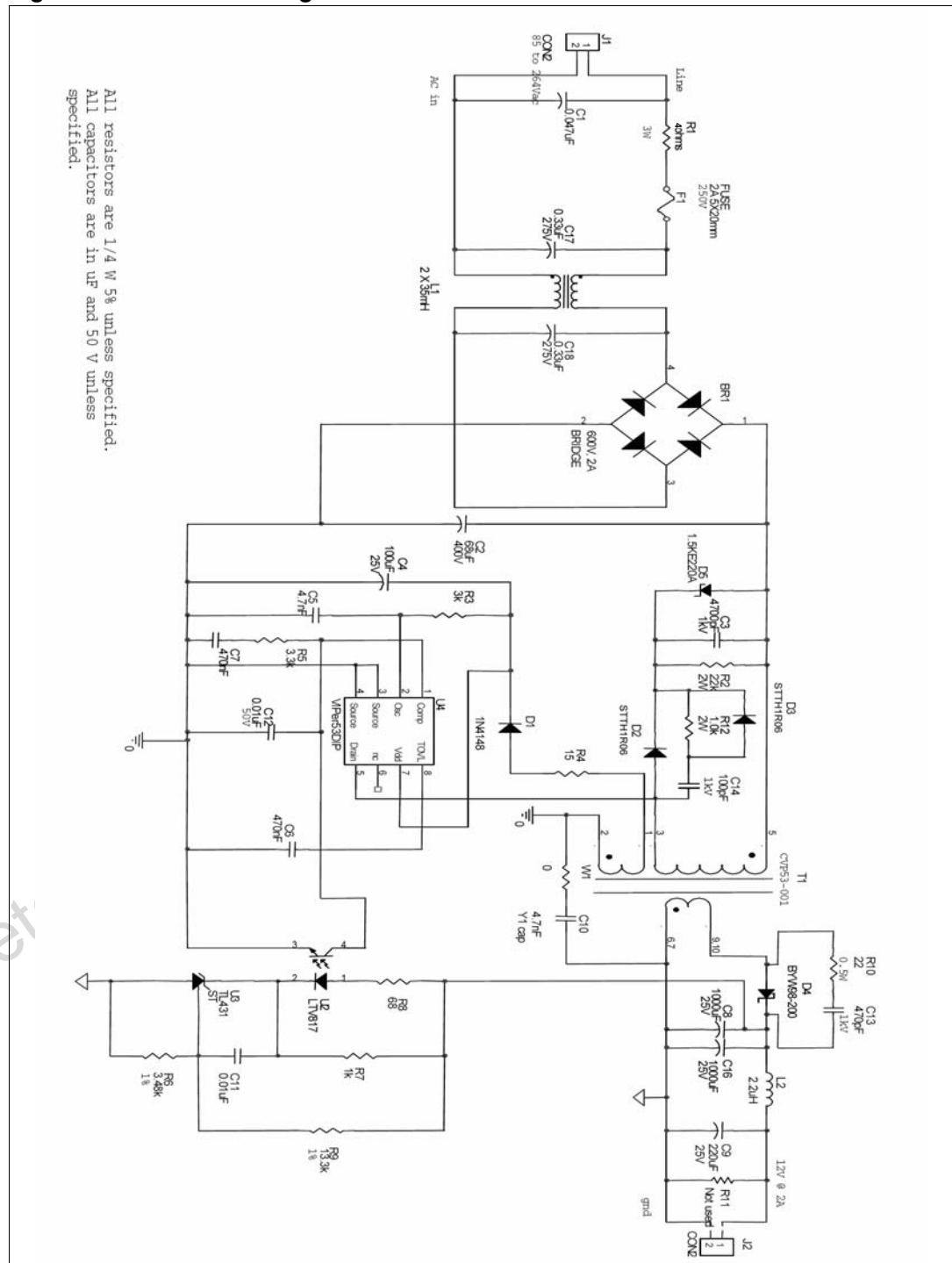

12 Revision history

Table 3. Revision history

Date	Revision	Changes
16-Jul-2004	1	First issue
12-Sep-2006	2	<ul style="list-style-type: none">- New template- Component list value modified- Schematic diagram modified

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2006 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com