

# **AN2122 APPLICATION NOTE**

## TV Hardware Design Rules: PCB Compatibility with ST92196/186

# Introduction

The purpose of this application note is to:

- 1. Describe how to design a printed circuit board (PCB) with optimum performance and compatibility between ST92E196 or ST92T196 (SDIP56 package), and ST92186 (SDIP32 and SDIP42 packages) microcontrollers.
- 2. Describe the external filters and components needed for the ST92186 family of microcontrollers (MCU).
- arollers in a arollers in a obsolete production Obsolete producti Obsolete production Obsolete producti 3. Provide advice on how to develop applications for ST92186 microcontrollers in SDIP32 or

# **Table of Contents**

#### Introduction 1 Chapter 1 1.1 1.2 1.2.1 **Chapter 2** 2.1 2.2 **Chapter 3** External Components ..... 6 3.1 3.2 **Chapter 4** Reference Layout ..... . . . . . . . . . . . 8 Chapter 5 CVBS and HSYNC Signals ... 5.1 CVBS Signal on ST92196 .....10 5.2 HSYNC Signal ......10 **Chapter 6** PCB Compatibility between ST92196 and ST92186 MCUs .....10 6.1 SDIP56/42 Mounting Instructions ......10 6.2 SDIP56/32 Mounting instructions ......11 Chapter 7

47/

oductls

## 1 Ground Plane and Power Supply Lines

#### 1.1 Ground Plane

A local ground plane must be placed under the entire area of the ST92196/186 component and connected using the widest possible line to the PCB ground as shown in Figure 1, Figure 2 and Figure 3. This plane and its associated lines are dedicated to the ST92196/186 microcontroller. It is strongly recommended not to connect any other lines from components not already connected to the ST92196/186 to this plane. This is to avoid adding any impedance or analog disturbances which could cause the IC ground to float.

All ground pins for the ST92196/186 (VSS1 and VSS2) and external components (PLL, oscillator, etc.) must be connected to this ground plane.

Ground pins VSS1 and VSS2 must be connected as close as possible to each other on the printed circuit board.

#### 1.2 Power Supply Lines

#### 1.2.1 Digital and Analog Power Supplies

Two different power supply lines are required for the ST92196/186:

- one Analog power supply line for VDDA pin.
- one Digital power supply line (pins VDD1 and VDD2 (only on ST92196)).

Those power supply levels must be within the +5V ±10% range with IVDD-AVDDI < 600 mV.

The supply pins must be decoupled as shown in Figure 1, Figure 2 and Figure 3. Decoupling capacitors must be set as close as possible to the IC supply pins.

An inductive component, with a low serial resistance, must be placed close to the decoupling capacitors to provide high impedance and to improve noise filtering. This component is required on both:

- the VDDA power supply pin to prevent noise disturbances from the PCB power source,
- the VDD power supply pins in order to prevent disturbances being sent towards the PCB power source and other ICs.

The VDD and VDDA lines must be dedicated to the ST92196/186. Any other connections between other IC supply pins and VDD and/or VDDA lines are not recommended. This does not include MCU Reset circuitry. (See Figure 1, Figure 2 and Figure 3).

All other components must be connected to the +5V power supply and not to the ST92196/186 VDD or VDDA lines.

<u>لرکم</u>



Figure 1: Ground Plane and Power Supply Lines for ST92196

Note: For ST92196 family devices, there is an internal connection between the VDD1 and VDD2 pins. Nevertheless, for better current distribution, it is highly advised to externally connect both VDD1 and VDD2 pins to digital +5V power supply.

Figure 2: Ground Plane and Power Supply Lines for ST92186 SDIP42 Packages





#### Figure 3: Ground Plane and Power Supply Lines for ST92186 SDIP32 Package

#### **Tied Pins** 2

#### 2.1 **Unused Pins**

2.2

Ĺ₹/

Table 1: Rules for Connecting Unused Pins

Pin Name	Rule	
TESTO	Tie to VDD	
VPP (only on ST92196)	Tie to VDD	

All unused I/O pins must be initialized as Bidirectional Weak Pull Up (default state after reset - set Note: by hardware), associated with a '0' in their data register. This prevents uncontrolled levels and reduces power consumption.

### I<sup>2</sup>C Pull-up Resistors

All the pull-up resistors (1.7 kΩ)of the ST92196/186 I<sup>2</sup>C line must be connected to the +5V power supply line (and not to the VDDA or VDD pins).

<u>ل ۲۸</u>

# 3 External Components

### 3.1 PLL

All PLL components must be connected as close as possible to the ST92196/186 PLL input pins (referenced as FCPU and FOSD) as shown in Figure 4, Figure 5 and Figure 6. This helps to prevent jitter problems from occuring with the OSD.

### 3.2 Crystal Oscillator

The crystal oscillator and its associated components must also be connected as close as possible to the ST92196/186 input/output pins, and the VSS2 ground must be used (for ST92196 and ST92186 SDIP42 packages). Refer to Figure 4, Figure 5 and Figure 6 for more details.

The capacitors must be grounded as close as possible to the MCU ground plane.

In order to provide a stable frequency for data slicing and OSD functions, the crystal oscillator must not be substituted by an external oscillator.



#### Figure 4: External Components for ST92196

57



Figure 5: External Components for ST92186 SDIP42 Package





#### AN2122

## 4 Reference Layout

All recommendations listed in previous sections on how to design a TV chassis using an ST92196/ 186 MCU are summarized below.



Figure 7: Reference Layout for ST92196

57



Figure 8: Reference Layout for ST92186 SDIP42 Package

Figure 9: Reference Layout for ST92186 SDIP32 Package



# 5 CVBS and HSYNC Signals

## 5.1 CVBS Signal on ST92196

The video signal (CVBS) is the most important signal provided to the ST92196 in terms of Closed Caption quality. It is strongly recommended that the CVBS line be protected on the PCB with a shielding (GND track) to prevent any analog disturbance.

## 5.2 HSYNC Signal

This signal is used to synchronize the RGB output signals sent by the ST92196/186 via the video lines. The following is required:

- The same HSYNC signal must be provided to both the Chroma Processor and the ST92196/ 186 MCU (same synchronization reference signal).
- The edge slope must be taken into consideration. The maximum HSYNC rising time (or falling time) depends on the signal-to-noise ratio. The lower the ratio, the steeper the HSYNC active edge.

# 6 PCB Compatibility between ST92196 and ST92186 MCUs

ST92E196 ou ST92T196 microcontrollers are available for development in SDIP56 packages.

The final ST92186 chip will be available in SDIP 32- or 42-pin packages. So you will need to have a PCB that can accept both packages.

This is very easy to set up.

## 6.1 SDIP56/42 Mounting Instructions

Figure 10 summarizes the neccessary connections between an SDIP56 socket (for ST92x196) and SDIP42 socket (for ST92186). The schematics is given for a single-layer PCB. It requires 6 straps.

The external filters and the crystal oscillator must be placed as close as possible to the SDIP42 socket (refer to Section 3: External Components for more details).

Please note that all the power and ground pins of the ST92196 SDIP56 package must be connected even if they are not used in the ST92186 SDIP42 package.

Ground pins VSS1 and VSS2 must be connected as close as possible to each other on the printed circuit board.

In addition, you MUST connect the following to pins VDD1 or VDD2:

- Pin 56 (VPP) of the ST92196 SDIP56 package
- Pin 55 (TEST0) of the ST92196 SDIP56 package

In order no to overload the drawing in Figure 10, only the 2 socket positions are shown.

The rules described in Section 1: Ground Plane and Power Supply Lines and Section 3: External Components must be applied.

Note: You do not need to use all the I/O pins in your software. It is advised not to use, if possible, the I/O pins that lead to "long" connections between the SDIP56 socket and the SDIP42 socket, such as P5.5, P5.6, P2.4, P2.5, P2.6, and P2.7. The PCB layout will be better as far as noise immunity is concerned.



#### Figure 10: Suggested SDIP56/SDIP42 Schematic Diagram

### 6.2 SDIP56/32 Mounting instructions

Figure 11 summarizes the neccessary connections between the SDIP56 socket (for ST92x196) and the SDIP32 socket (for ST92186). The schematic is given for a single- layer PCB. It requires 6 straps.

The external filters and the crystal oscillator must be placed as close as possible to the SDIP32 socket (refer to Section 3: External Components chapter for more details).

Please note that all the power and ground pin of the ST92196 SDIP56 package must be connected even if they are not used in the ST92186 SDIP32 package.

In addition to this, you MUST connect to VDD1 or VDD2 the following pins :

- Pin 56 (VPP) of the ST92196 SDIP56 package
- Pin 55 (TEST0) of the ST92196 SDIP56 package

In order not to overload the drawing in Figure 10, only the 2 socket positions are shown.

**ل ۲**۸

The rules described in Section 1: Ground Plane and Power Supply Lines and Section 3: External Components must be applied.

Note: You do not need to use all the I/O pins in your software. It is advised not to use, if possible, the I/O pins that lead to "long" connections between the SDIP56 socket and the SDIP32 socket, such as P5.0, P2.4, P2.5, P2.6, P2.7, P0.3, and P0.4. The PCB layout will be better as far as noise immunity is concerned.

![](_page_11_Figure_4.jpeg)

![](_page_11_Figure_5.jpeg)

# 7 Developing Applications for ST92186 using ST92x196

To avoid problems with your final ST92186 ROMed code, you must follow a few rules when developing your software:

- Configure your software scriptfile (application\_name.scr), makefile (makefile), and emulator configuration file (hardware.gdb) as if you were using the ST92186 with 32K or 24K of ROM (depending on your device), 640 bytes of RAM, and 256 bytes of OSDRAM.
- Only use the cells available in the ST92186.
- Only use the pins available in ST92186 (check the cells present on both the ST92x196 and ST92186, and for which not all I/Os or alternate functions are implemented on the ST92186).
- DO NOT USE THE OSD MOUSE feature.
- As some I/Os are not bounded on the SDIP32 package, you must configure P2.1, P2.2, P3.1, P3.5, P3.7, P5.1, P5.2, P5.5, and P5.6 as OUTPUT Push-Pull at the very first beginning of

your software, and NEVER CHANGE THIS CONFIGURATION after initialization. This will prevent undesired software behavior.

A detailed comparison of the ST92186 and ST92196 packages is given below.

Cell Name	ST92186 SDIP32	ST92186 SDIP42	ST92x196x SDIP56
ROM	0x00000 to 0x07FFF (32K) 0x00000 to 0x05FFF (24K)	0x00000 to 0x07FFF (32K) 0x00000 to 0x05FFF (24K)	0x00000 to 0x1FFFF (128K)
RAM	0x20F000 to 0x20F27F (640 bytes)	0x20F000 to 0x20F27F (640 bytes)	0x20F000 to 0x20FFFF (4K on ST92x196A) 0x20F000 to 0x20FBFF (3K on ST92x196B)
OSDRAM	0x220000 to 0x2200FF (256 bytes)	0x220000 to 0x2200FF (256 bytes)	0x220000 to 0x22017F (384 bytes)
External Interrupts	1 NMI + 6 external ITs (INT[7,5:4,2:0])	1 NMI + 8 external ITs (INT[7:0])	1 NMI + 8 external ITs (INT[7:0])
I/O ports	17 l/Os available : P0[4:3] P2[7:3,0] P3[6,4,2,0] P4[7:6,1:0] P5[0]	26 I/Os available : P0[4:3] P2[7:0] P3[7:4,2:0] P4[7:6,1:0] P5[6:5,2:0]	37 I/Os available : P0[7:0] P2[7:0] P3[7:0] P4[7:0] P5[6:5,2:0]
OSD	NO MOUSE up to 1024 characters in 9x13 up to 256 characters in 18x26 256 bytes of OSDRAM Translucency output	NO MOUSE up to 1024 characters in 9x13 up to 256 characters in 18x26 256 bytes of OSDRAM Translucency output	MOUSE up to 1536 characters in 9x13 up to 384characters in 18x26 384 bytes of OSDRAM Translucency output
IR Preprocessor	Available	Available	Available
Watchdog / Timer	One 16-bit timer with 8-bit prescaler	One 16-bit timer with 8-bit prescaler	One 16-bit timer with 8-bit prescaler
Standard Timer	One 16-bit timer with 8-bit prescaler	One 16-bit timer with 8-bit prescaler	One 16-bit timer with 8-bit prescaler
ADC	6-bit accuracy 3 channels (AIN[4:3,0]) External Trigger input	6-bit accuracy 5 channels (AIN[4:0]) External Trigger input	6-bit accuracy 8 channels (AIN[7:0]) External Trigger input
Voltage Synthesis	14-bit PWM/BRM 1 output (VSO2)	14-bit PWM/BRM 2 outputs (VSO1, VSO2)	14-bit PWM/BRM 2 outputs (VSO1, VSO2)
PWM	8-bit PWM 4 outputs (PWM[7:6,1:0])	8-bit PWM 6 outputs (PWM[7:6,3:0])	8-bit PWM 8 outputs (PWM[7:0])
DMA	Not Available	Not Available	Available
Multifunction Timer	Not Available	Not Available	Available on some devices
Closed Caption Data Slicer	Not Available	Not Available	1 or 2, depending on the device

|--|

Cell Name	ST92186 SDIP32	ST92186 SDIP42	ST92x196x SDIP56
Video Sync Error Detector	Not Available	Not Available	Available
12C	Not Available	Not Available	Available
SPI	Not Available	Not Available	Available
SCI	Not Available	Not Available	Available on some devices

obsolete Product(s) - Obsolete Product(s)

#### Table 2: Summary of ST92186/ST92196 Differences (Continued)

"The present note which is for guidance only aims at providing customers with information regarding their products in order for them to save time. as a result, STMicroelectronics shall not be held liable for any direct, indirect or consequential damages with respect to any claims arising from the content of such a note and/or the use made by customers of the information contained herein in connexion with their products."

Monator Bar Information furnished is believed to be accurate and reliable. However, STMicroelectronics assumes no responsibility for the consequences of use of such information nor for any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of STMicroelectronics. Specifications mentioned in this publication are subject to change without notice. This publication supersedes and replaces all information previously supplied. STMicroelectronics products are not authorized for use as critical components in life support devices or systems without express written approval of STMicroelectronics.

> The ST logo is a registered trademark of STMicroelectronics All other names are the property of their respective owners

© 2005 STMicroelectronics - All rights reserved

STMicroelectronics GROUP OF COMPANIES

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States

www.st.com

**لرجا**