

ST8R00 synchronous boost converter with output current cut-off function

Introduction


The ST8R00 family of synchronous step-up DC-DC converters with current output cut-off function provide up to 1 A over an input voltage range of 4 V to 6 V and an output voltage range of 6 V to 12 V.

The high switching frequency (1.2 MHz) allows the use of tiny surface-mount components. Along with the resistor divider to set the output voltage value, an inductor and two capacitors are required. A low output ripple is guaranteed by the current mode PWM topology and by the use of low ESR surface-mounted ceramic capacitors.

The device is available in two versions: burst mode (ST8R00) and continuous mode (ST8R00W).

The ST8R00 devices are thermal protected and available in the DFN8 4x4 package.

Figure 1. Simplified schematic diagram

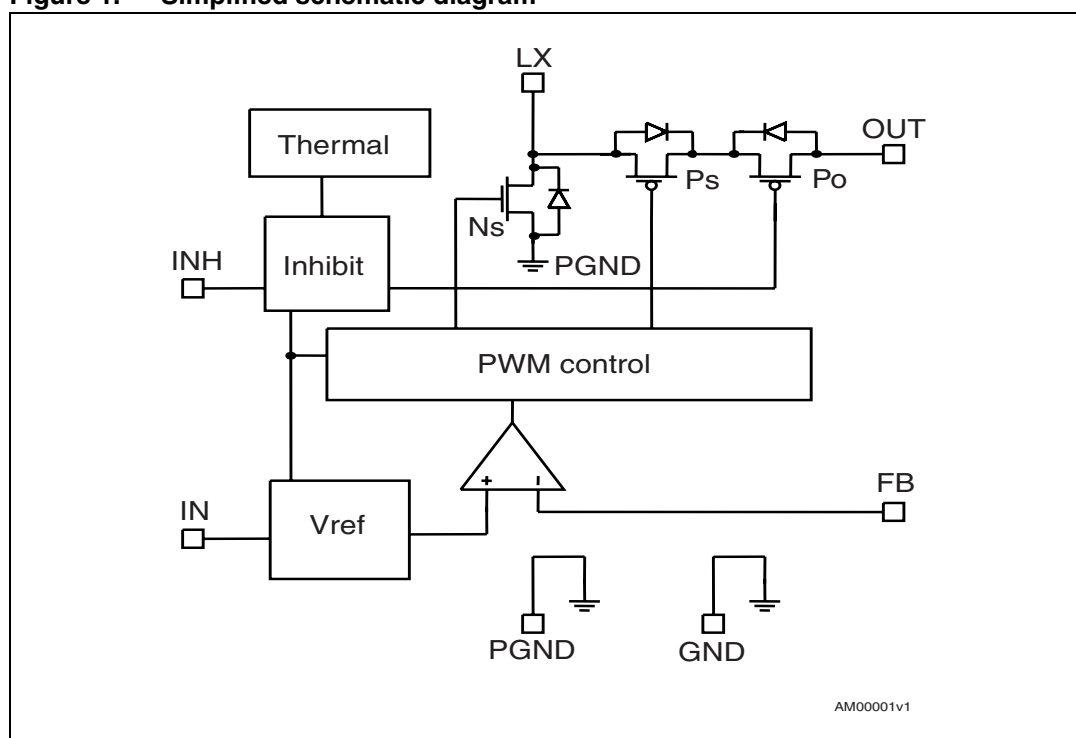

Contents

1	ST8R00 description	4
1.1	Inhibit function	7
2	Selecting components for applications	9
2.1	Output voltage selection	9
2.2	Input capacitor	10
2.3	Inductor	10
2.4	Output capacitor	10
2.5	Layout considerations	11
3	Thermal considerations	12
4	Demonstration board usage recommendation	13
4.1	External component selection	14
4.1.1	Capacitor selection	14
4.1.2	Inductor selection	14
5	BOM with most-used components	16
6	Footprint recommended data	17
7	Revision history	18

List of figures

Figure 1.	Simplified schematic diagram	1
Figure 2.	ST8R00 inductor current at light load	4
Figure 3.	ST8R00W inductor current at light load	5
Figure 4.	ST8R00W inductor current at no load	5
Figure 5.	ST8R00 cut-off block	6
Figure 6.	Current cut-off function	6
Figure 7.	Inrush current	7
Figure 8.	ST8R00 application schematic	7
Figure 9.	Inhibit voltage vs. temperature	8
Figure 10.	Typical application schematic	9
Figure 11.	Voltage feedback vs. temperature	9
Figure 12.	Layout considerations	11
Figure 13.	The ST8R00 demonstration board	13
Figure 14.	Demonstration board layers	13
Figure 15.	Demonstration board schematic	14
Figure 16.	Efficiency vs. output current	15
Figure 17.	Efficiency vs. output voltage	15
Figure 18.	ST8R00 efficiency vs. inductor	15
Figure 19.	ST8R00W efficiency vs. inductor	16
Figure 20.	DFN8 4x4 recommended footprint	17

1 ST8R00 description

The ST8R00 is a family of adjustable current mode PWM synchronous step-up DC-DC converters with internal 1 A power switch. It represents a complete 1 A switching regulator with internal compensation which eliminates the need for additional components.

The two devices in the family, the ST8R00 and ST8R00W, operate at light load in two different ways. The ST8R00 works in power-save mode to achieve good efficiency, as shown in [Figure 2](#). The ST8R00W, in order to guarantee the lowest switching ripple, operates in PWM (pulse width modulation) mode as show in [Figure 3](#) and [Figure 4](#).

At medium and high load current, both versions operate in PWM mode.

The thermal shutdown block turns off the regulator when the junction temperature exceeds 150 °C (typ), and the cycle-by-cycle current limiting provides protection against overcurrent sink.

Figure 2. ST8R00 inductor current at light load

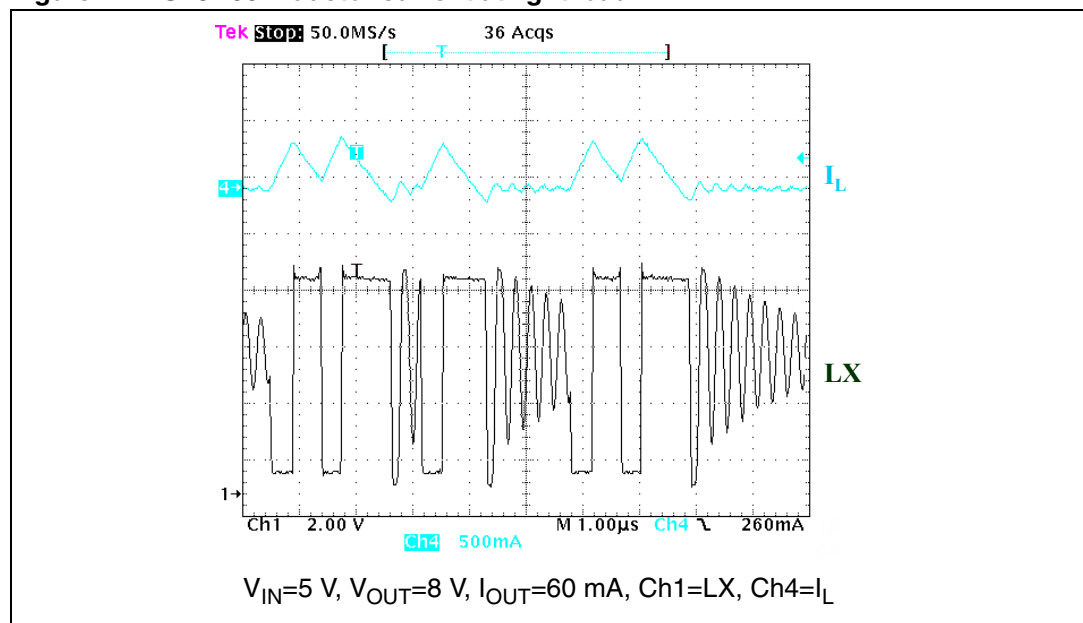
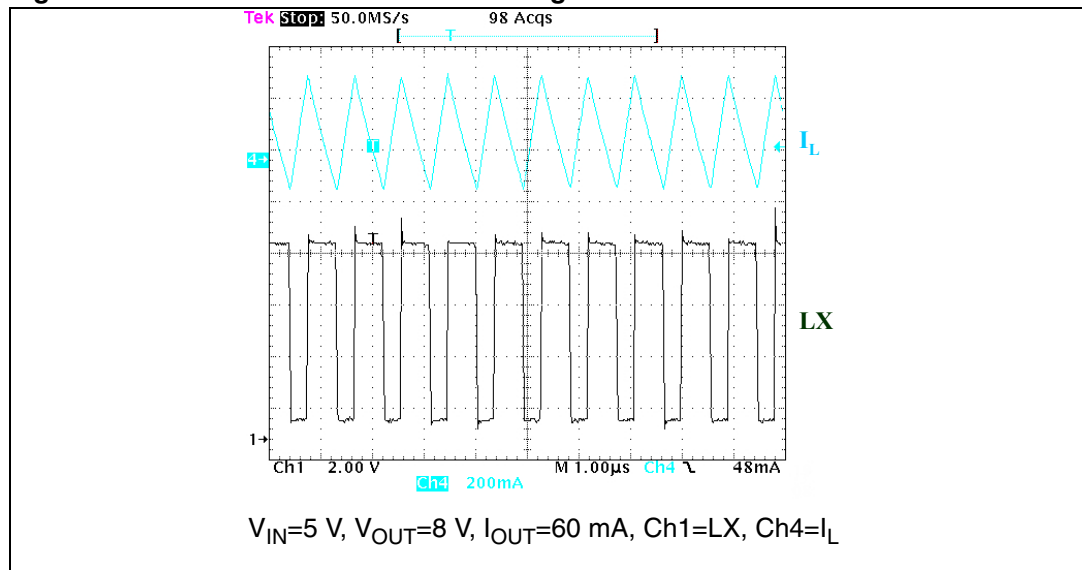
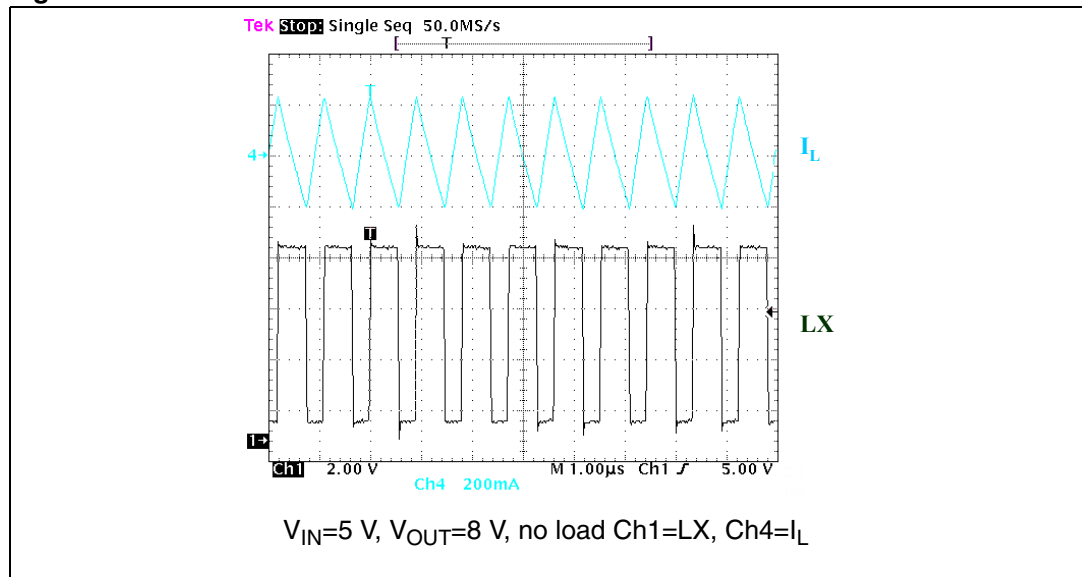


Figure 3. ST8R00W inductor current at light load**Figure 4. ST8R00W inductor current at no load**

For proper functioning of the device, only a few components are required: an inductor, two capacitors and the resistor divider. The inductor chosen must not saturate at the operating peak current. Its value should be selected taking into account that a large inductor value reduces output voltage ripple, while a smaller inductor can be selected when it is important to reduce package size and the total cost of the application. Finally, the ST8R00 family has been designed to work properly with X5R or X7R SMD ceramic capacitors both at the input and at the output. These types of capacitors, thanks to their very low series resistance (ESR), minimize the output voltage ripple. Other low ESR capacitors can be used in accordance with application requirements without compromising the correct functionality of the device.

This device features an output current cut-off function. Two P-channel MOSFETs in a back-to-back configuration, as shown in [Figure 5](#), stop the output current when the inhibit is low ([Figure 6](#)).

Figure 5. ST8R00 cut-off block

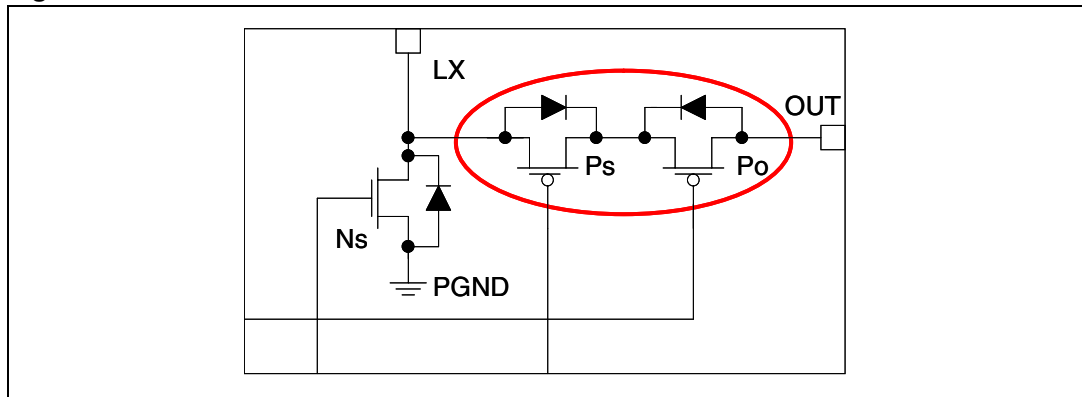


Figure 6. Current cut-off function

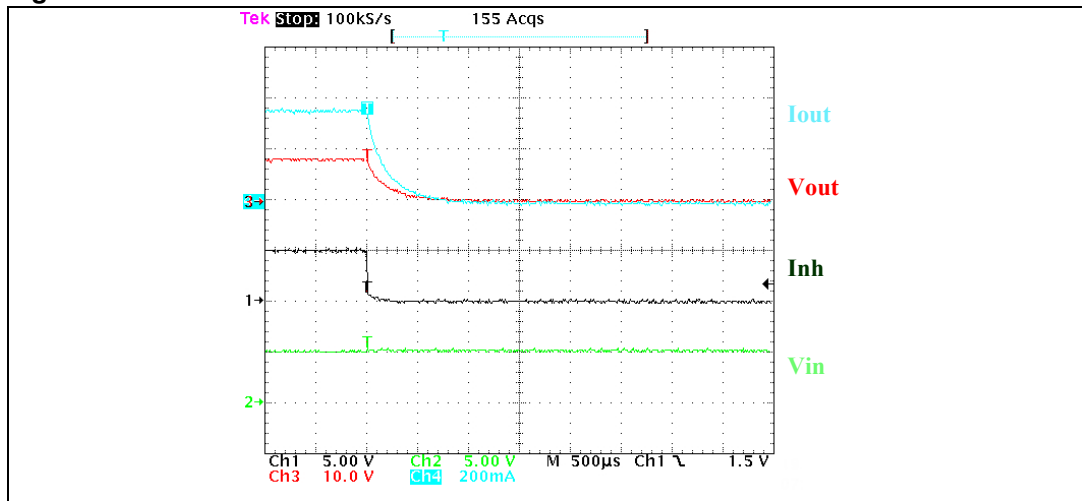
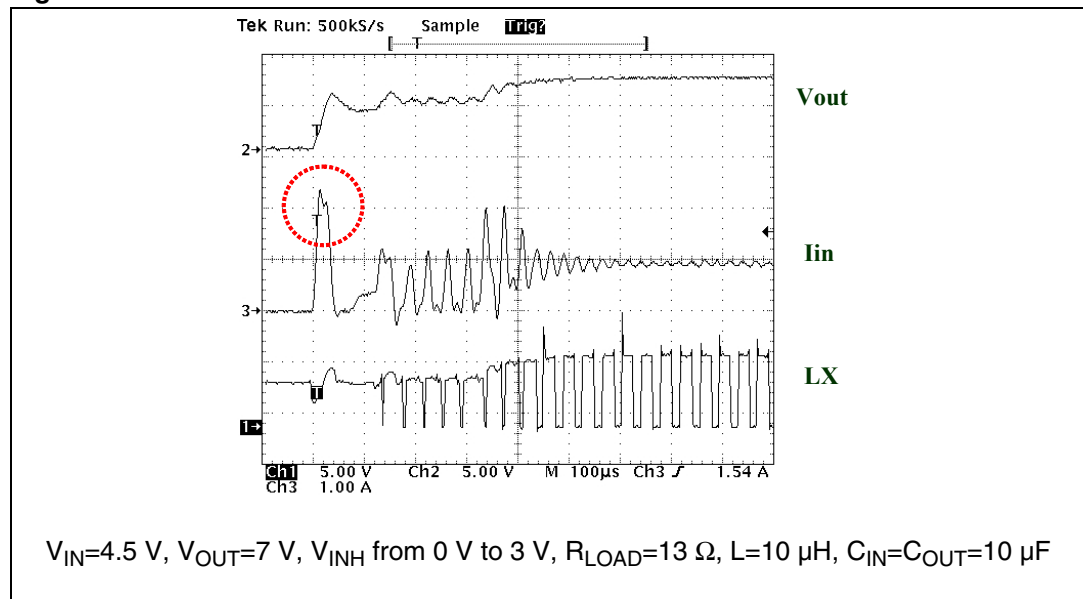


Figure 7 shows the in-rush current at start-up. Initially, the C_{OUT} capacitor is completely discharged and the current limitation is due only to the equivalent series resistor of the inductor, the power MOSFET parasitic diode and the cut-off MOSFETs' $R_{DS(ON)}$. As soon as the output voltage reaches the input voltage level, the device begins to switch and the current is limited cycle by cycle.

Figure 7. Inrush current

1.1 Inhibit function

The ST8R00 family of devices also include an inhibit function (pin 6). When the INH voltage is higher than 2 V, the device is ON and if it is lower than 0.8 V, the device is OFF.

The INH pin does not have an internal pull-up, which means that the pin cannot be left floating.

If the inhibit function is not used, the INH pin must be connected to V_{IN} as in the schematic in [Figure 8](#) below.

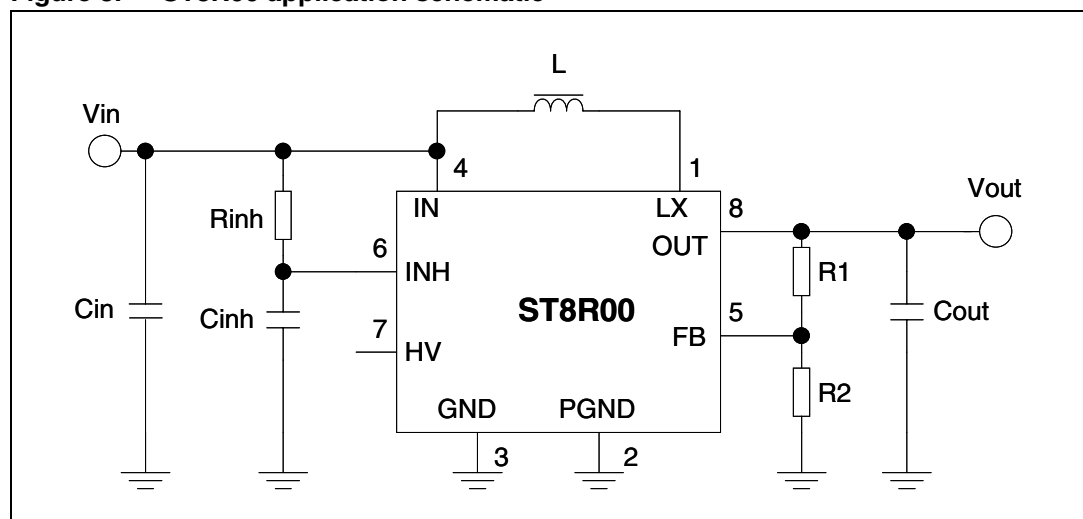
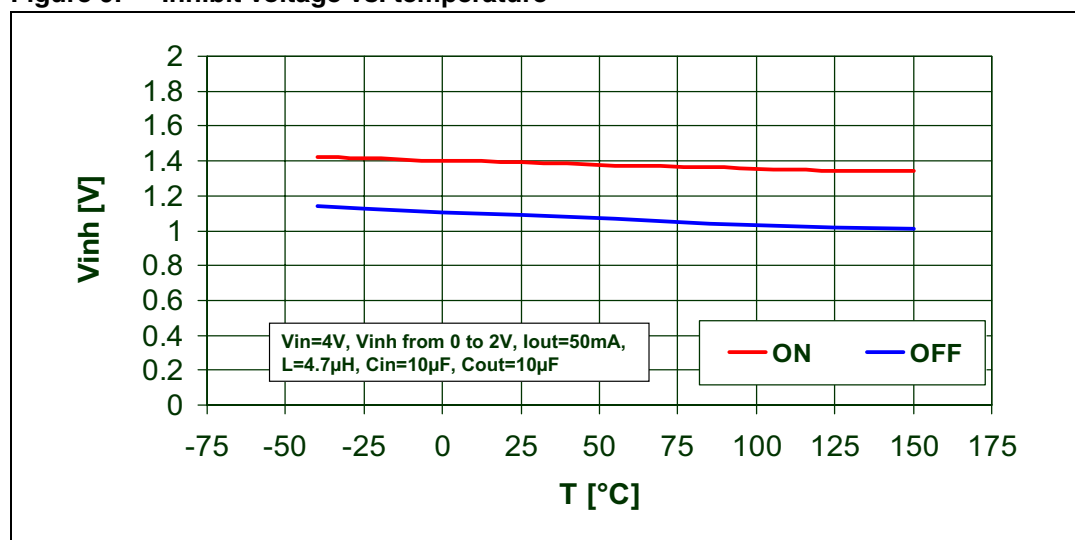
Figure 8. ST8R00 application schematic

Figure 9. Inhibit voltage vs. temperature




2 Selecting components for applications

This section provides information to assist in the selection of the most appropriate components for applications.

[Figure 10](#) shows a typical application schematic diagram.

Figure 10. Typical application schematic

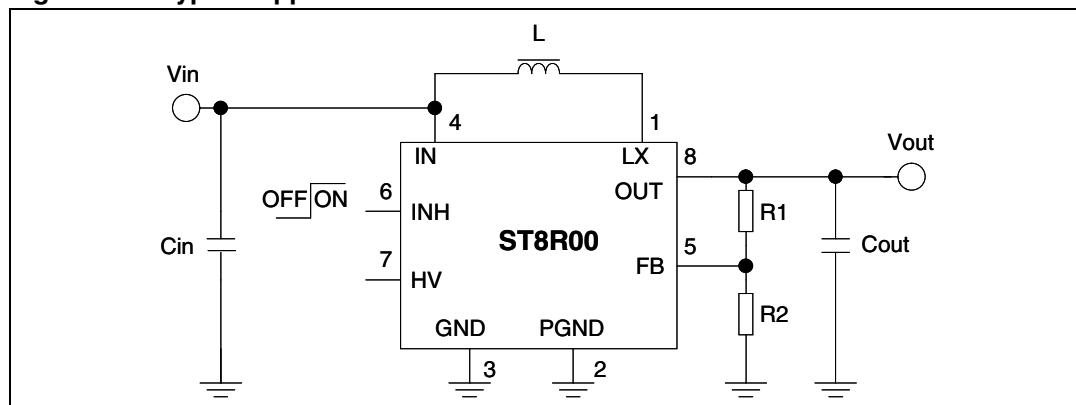

2.1 Output voltage selection

The output voltage can be adjusted from 6 V up to 12 V by connecting a resistor divider between the output and the FB pin.

The resistor divider should be chosen in accordance with the following equation:


Equation 1

$$V_{out} = V_{FB} \left[1 + \frac{R_1}{R_2} \right] \quad \text{with} \quad V_{FB} = 1.22 \text{ V}$$

The feedback voltage versus temperature is shown [Figure 11](#) below.

It is recommended to use a resistor with a value in the range of 10 kΩ to 100 kΩ. Lower values can be suitable as well, but will increase current consumption.

Figure 11. Voltage feedback vs. temperature

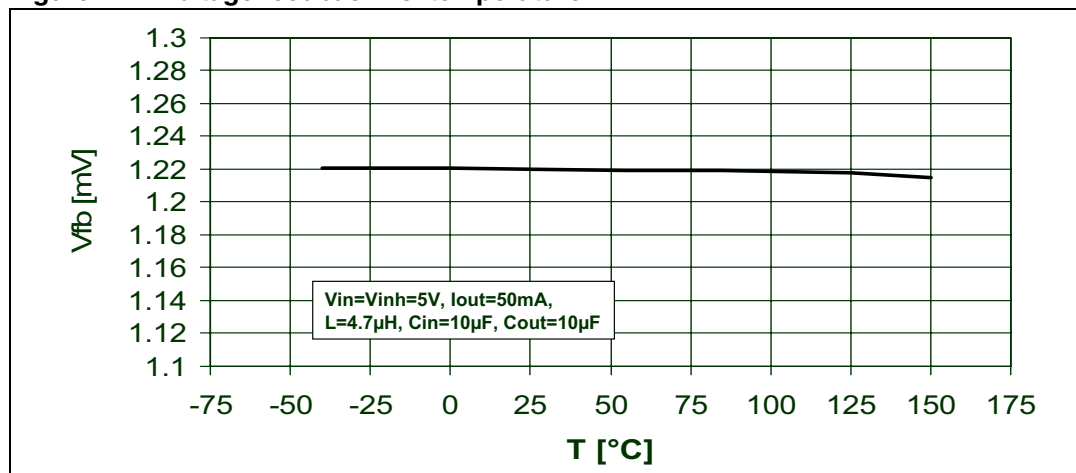

2.2 Input capacitor

The input capacitor must be able to provide AC ripple current to the inductor and to withstand the maximum input operating voltage.

Another important function of the input capacitor is to limit noise and therefore the interference with the other blocks connected to the same network.

The quality of these capacitors must be quite high to minimize the power dissipation generated by the internal ESR, thereby improving system reliability and efficiency.

Various capacitors can be considered:

- Ceramic capacitors - These capacitors usually have a higher RMS current rating for a given physical dimension (due to the very low ESR). The drawback is the high cost of capacitors with very large values.
- Electrolytic capacitor - The availability of small size tantalum capacitors with very low ESR is increasing. However, they are subject to thermal damage if subjected to very high current during charge. Since they can, in fact, be subjected to high surge current when connected to the power supply, it is better to avoid using this type of capacitor for the input filter of the device. Aluminum capacitors are not the best choice due to their high ESR.

2.3 Inductor

The inductor value is very important because it establishes the ripple current. The approximate inductor value is obtained with the following formula:

Equation 2

$$L = \frac{V_{in}}{\Delta I_L} \cdot T_{ON}$$

where T_{ON} is the ON time of the internal switch, given by $D \cdot T_{SW}$. The ripple current, ΔI_L , is usually fixed at 20-40% of I_{IN_MAX} .

Equation 3

$$I_{IN_MAX} = \frac{I_{OUT_max} \cdot V_{out}}{V_{in} \cdot \eta}$$

where η is the efficiency.

2.4 Output capacitor

The output capacitor is very important to satisfy the output voltage ripple requirement. To reduce the output voltage ripple, a low ESR capacitor is required.

The output voltage ripple (V_{RIPPLE}), in continuous mode is:

Equation 4

$$V_{RIPPLE} = I_{out} \cdot \left(ESR + \frac{(V_{out} - V_{in})}{V_{out} \cdot C_{out} \cdot F_{SW}} \right)$$

where F_{SW} is the switching frequency.

2.5 Layout considerations


Due to the high switching frequency and peak current, the layout is an important design step for all switching power supplies. If the layout is not done carefully, important parameters such as efficiency and output voltage ripple could be out of specification.

Short, wide traces must be implemented for main current and for power ground paths as shown in bold in [Figure 12](#). The input capacitor must be placed as close as possible to the IC pins as well as the inductor and output capacitor.

A common ground node minimizes ground noise, as shown in [Figure 12](#).

The HV pin must be floating or connected to GND and the exposed pad of the package must be connected to the common ground node.

Figure 12. Layout considerations

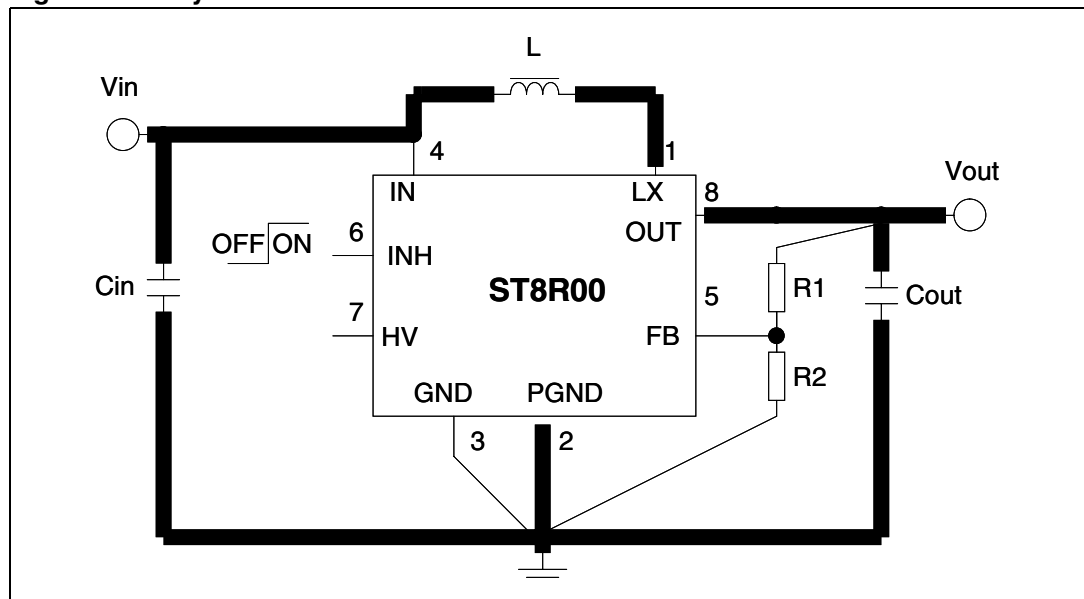

3 Thermal considerations

The dissipated power of the device is related to three different sources:

- Switching losses due to the (not negligible) $R_{DS(ON)}$. These are equal to:

Equation 5

$$P_{ON_N} = R_{DS(ON_N)} \cdot [I_{OUT} / (1-D)]^2 \cdot D$$

and

Equation 6

$$P_{ON_P} = R_{DS(ON_PEQ)} \cdot I_{OUT}^2 \cdot (1-D)$$

where D is the duty cycle of the application and $R_{DS(ON_PEQ)} = R_{DS(ON_PS)} + R_{DS(ON_PO)}$.

Note: the duty cycle is theoretically given by:

$$1 - \frac{V_{in}}{V_{out}}$$

but in practice it is quite higher than this value to compensate for the losses of the overall application. For this reason, the switching losses related to the $R_{DS(ON)}$ increase compared to an ideal case.

- Switching losses due to its turning on and off. These are calculated using the following equation:

Equation 7

$$P_{SW} = V_{IN} \cdot I_{OUT} \cdot \frac{(t_{ON} + t_{OFF})}{2} \cdot F_{SW} = V_{IN} \cdot I_{OUT} \cdot t_{R-F} \cdot F_{SW}$$

where t_{ON} and t_{OFF} are the overlap times of the voltage across the power switch and the current flowing into it during the turn-on and turn-off phases. t_{R-F} is the equivalent switching time.

- Quiescent current losses:

Equation 8

$$P_Q = V_{IN} \cdot I_Q$$

where I_Q is the quiescent current.

The overall losses are:

Equation 9

$$P_{TOT} = R_{DS(ON_N)} \cdot (I_{OUT} / (1-D))^2 \cdot D + R_{DS(ON_PEQ)} \cdot I_{OUT}^2 \cdot (1-D) + V_{IN} \cdot I_{OUT} \cdot t_{R-F} \cdot F_{SW} + V_{IN} \cdot I_Q$$

The junction temperature of device will be:

Equation 10

$$T_J = T_A + R_{thJA} \cdot P_{TOT}$$

where T_A is the ambient temperature and R_{thJA} is the thermal resistance junction-to-ambient.

4 Demonstration board usage recommendation

The demonstration board shown in [Figure 13](#) is provided with a Kelvin connection, so for each pin there are two lines available: one used to supply or sink current, and the other used to perform the needed measurement.

The ST8R00 inhibit pin does not have an internal pull-up, so the inhibit pin cannot be left floating.

Figure 13. The ST8R00 demonstration board


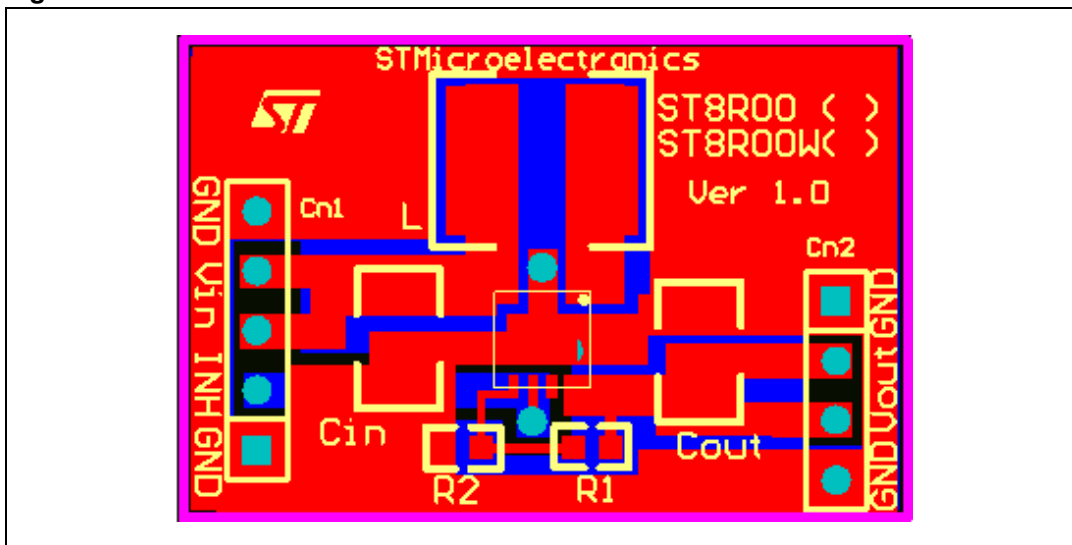


Figure 14. Demonstration board layers

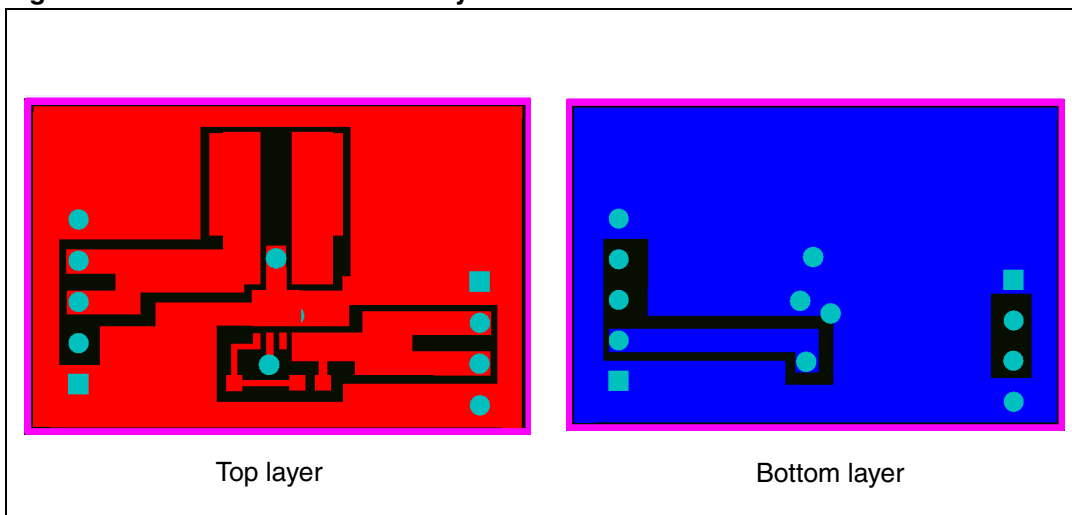


The board has one inhibit pin available, located on the top left of the board.

The inhibit pin can be used to supply an external voltage higher than 2 V to turn on the device, or an external voltage lower than 0.8 V to turn off the device.

4.1 External component selection

Figure 15 shows the schematic diagram of the demonstration board.

Figure 15. Demonstration board schematic

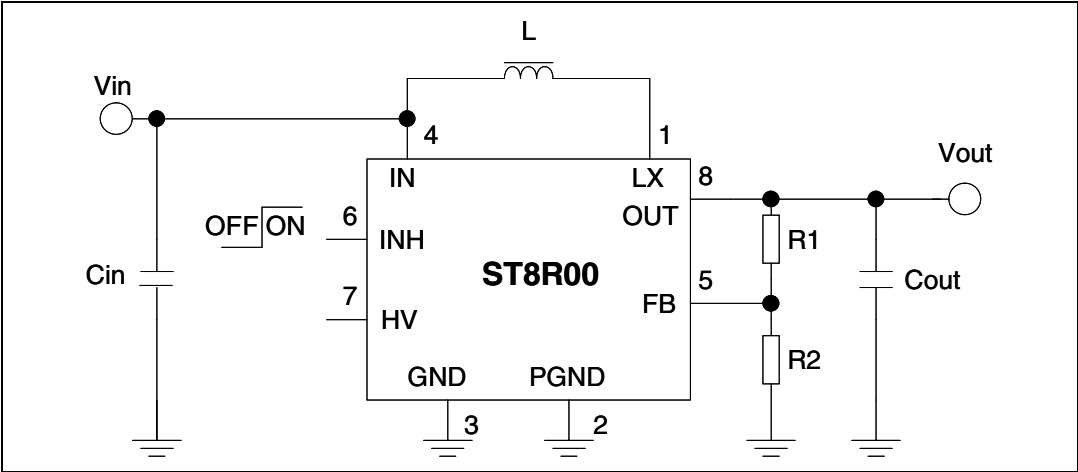

In order to obtain the needed output voltage, the resistor divider must be selected based on the following formula:

Equation 11

$$V_{out} = V_{FB} \left[1 + \frac{R1}{R2} \right] \text{ with } V_{FB} = 1.22 \text{ V}$$

Table 1. Recommended resistor divider

V_{out}	R1	R2
8 V	56 kΩ	10 kΩ
9.5 V	68 kΩ	10 kΩ

The resistors in Table 1 represent a good compromise in terms of current consumption and minimum output voltage.

4.1.1 Capacitor selection

It is possible to use any X5R or X7R ceramic capacitor:

- C_{IN} =10 μF (ceramic) or higher
- C_{OUT} =10 μF (ceramic) or higher. It is possible to put several capacitors in parallel to reduce the equivalent series resistance and improve the ripple present in the output voltage.

4.1.2 Inductor selection

Due to the high (1.2 MHz) frequency, it is possible to use very small inductor values. In the demonstration board, the device was tested with inductors in the range of 1 μH to 10 μH, with very good efficiency performance (see Figure 18 and Figure 19).

Because the device is able to provide an operating output current of 1 A, we strongly recommend the use of inductors capable of managing at least 3.5 A.

Figure 16. Efficiency vs. output current

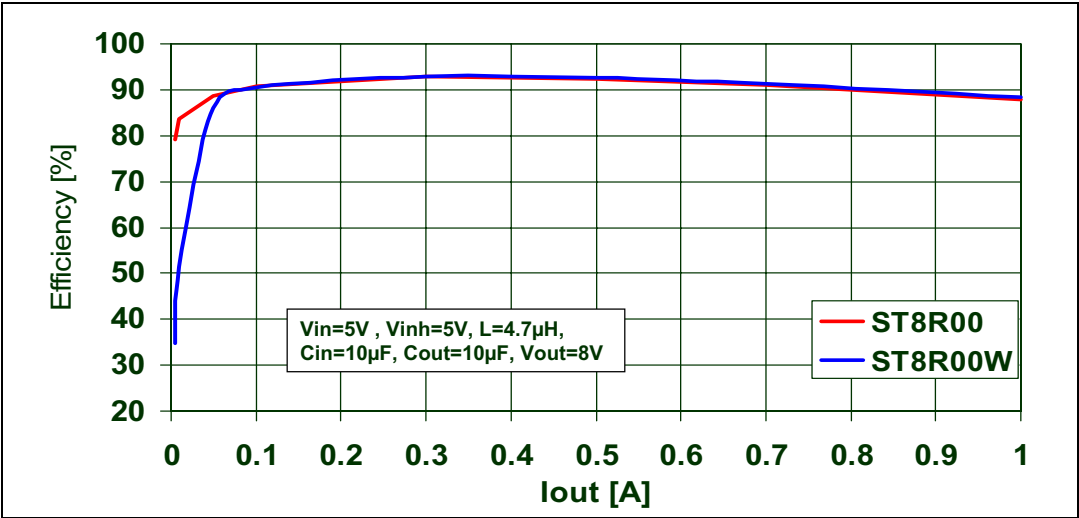


Figure 17. Efficiency vs. output voltage

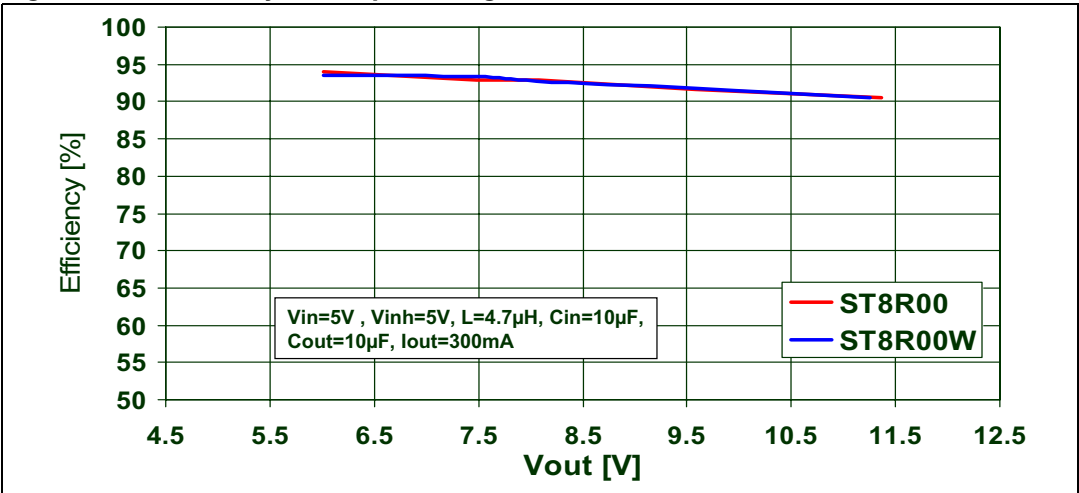


Figure 18. ST8R00 efficiency vs. inductor


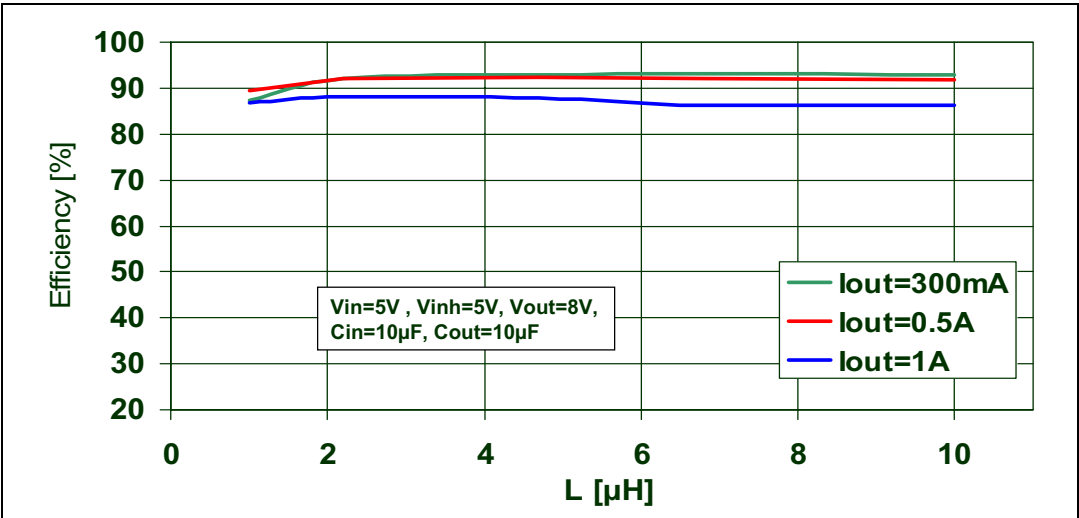


Figure 19. ST8R00W efficiency vs. inductor

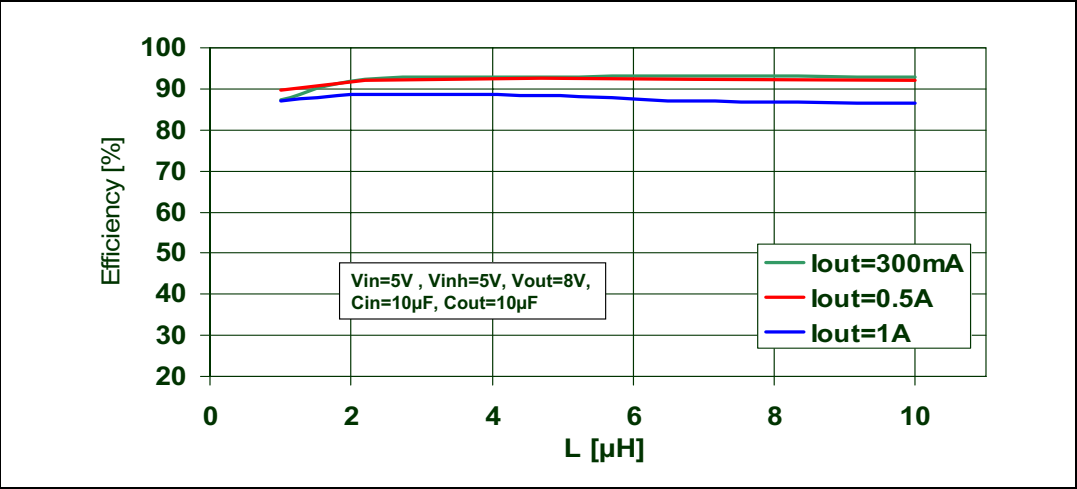


5 BOM with most-used components

Table 2. Bill of materials

Name	Value	Material	Manufacturer	Part numbers
C _{IN}	10 μF	Ceramic	Murata	GRM31CR61E106KA12B
C _{OUT}	10 μF	Ceramic	Murata	GRM31CR61E106KA12B
L	4.7 μH		Coiltronics	DR73-4R7

6 Footprint recommended data

Figure 20. DFN8 4x4 recommended footprint

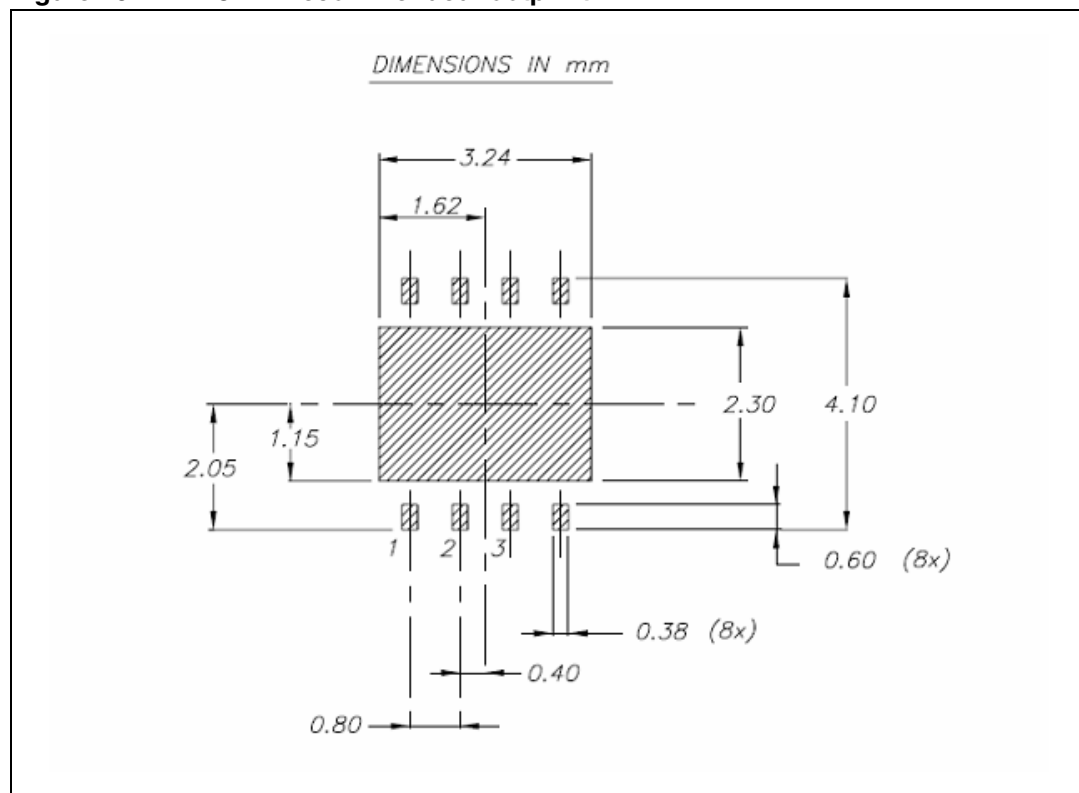

7 Revision history

Table 3. Document revision history

Date	Revision	Changes
13-May-2008	1	Initial release
03-Dec-2009	2	Modified Equation 9: on page 12.

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2009 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com

