

AN2929 Application note

Wide range [90 V - 265 V] input, 5 V - 12 W output VIPER27LN demonstration board with improved standby performance

Introduction

In consumer applications such as LCD or plasma TVs, some models of DVD recorders, settop boxes with hard disk, as well as desktop computers, the power supply often includes two modules: the main power supply that provides most of the power and is off when the application is in standby mode and the auxiliary power supply that provides energy for specific peripherals such as USB ports, remote receivers, and modems.

The auxiliary power supply is also on when the application is in standby mode and it is often required that its input power be as low as possible. The demonstration board presented in this application note meets the specification of a wide range of auxiliary power supplies for these applications and is optimized for very low standby consumption, helping to meet the most stringent energy-saving requirements.



Figure 1. **VIPER27LN demonstration board**

Contents

1	Boa	rd description
	1.1	Electrical specifications 5
	1.2	Schematic and bill of material 5
	1.3	Transformer
2	Test	ing the board
	2.1	Typical board waveforms
	2.2	Precision of the regulation and output voltage ripple
	2.3	Efficiency
	2.4	Light-load performance 17
	2.5	Overload protection
	2.6	Secondary winding short-circuit protection
	2.7	Output overvoltage protection 24
	2.8	Brownout protection
	2.9	EMI measurements
3	Con	clusion
4	Refe	rences
5	Revi	sion history



List of figures

Figure 1.	VIPER27LN demonstration board 1
Figure 2.	Schematic
Figure 3.	Transformer size
Figure 4.	Transformer size and pin diagram [inches (mm)]
Figure 5.	Drain current and voltage at full load 115 V _{AC} 9
Figure 6.	Drain current and voltage at full load 230 V _{AC} 9
Figure 7.	Drain current and voltage at full load 90 V _{AC} 9
Figure 8.	Drain current and voltage at full load 265 V _{AC} 9
Figure 9.	Output voltage ripple 115 V _{INAC} full load11
Figure 10.	Output voltage ripple 230 V _{INAC} full load11
Figure 11.	Output voltage ripple 115 V _{INAC} at no load (burst mode)
Figure 12.	Output voltage ripple 230 V _{INAC} 50 mA at no load (burst mode)
Figure 13.	Efficiency vs. V _{IN}
Figure 14.	Efficiency vs. load
Figure 15.	Active mode efficiency vs. V _{IN}
Figure 16.	Input voltage averaged efficiency vs. load
Figure 17.	ENERGY STAR [®] efficiency criteria
Figure 18.	Input power vs. input voltage for different loads
Figure 19.	Average switching frequency vs. input voltage
Figure 20.	Output power vs. input voltage with input power of 1 W 20
Figure 21.	Output short-circuit
Figure 22.	Operation with output shorted 22
Figure 23.	2 nd OCP tripping
Figure 24.	Operating with secondary winding shorted - restart mode
Figure 25.	OVP circuit
Figure 26.	OVP
Figure 27.	Jumper J7 setting, brownout disabled
Figure 28.	Jumper J7 setting, brownout enabled
Figure 29.	Brownout protection
Figure 30.	Input AC voltage steps from 90 V _{AC} to 75 V _{AC}
Figure 31.	Input voltage steps from 90 V _{AC} to 0
Figure 32.	115 V _{AC}
Figure 33.	230 V _{AC}



List of tables

Table 1.	Electrical specifications
Table 2.	Bill of material
Table 3.	Transformer characteristics
Table 4.	Output voltage and V _{DD} line-load regulation
Table 5.	Output voltage ripple
Table 6.	Burst mode related output voltage ripple
Table 7.	Efficiency
Table 8.	Active mode efficiencies
Table 9.	Line voltage averaged efficiency vs. load 15
Table 10.	Energy efficiency criteria for standard models
Table 11.	Energy efficiency criteria for low-voltage models 16
Table 12.	No-load input power (no brownout) 17
Table 13.	Energy consumption criteria for no load 17
Table 14.	Low-load performance P _{OUT} = 25 mW
Table 15.	Low-load performance P _{OUT} = 50 mW
Table 16.	Output power when the input power is 1 W
Table 17.	Input and output load
Table 18.	Document revision history



Unit V V A

mV

°C

60

1 Board description

1.1 Electrical specifications

The electrical specifications of the VIPER27LN demonstration board are listed in *Table 1*.

Table 1.	Electrical specifications		
Symbol	Parameter	Value	
V _{IN}	Input voltage range	[90V _{RMS} ; 265V _{RMS}]	
V _{OUT}	Output voltage	5	
I _{OUT}	Max output current	2.4	
Δ_{VOUT_LF}	Precision of output regulation	±5%	
$\Delta_{VOUT_{HF}}$	High-frequency output voltage ripple	50	

Max ambient operating temperature

Table 1.Electrical specifications

1.2 Schematic and bill of material

The schematic of the board is shown in *Figure 2*. *Table 2* gives the list of components (bill of material).

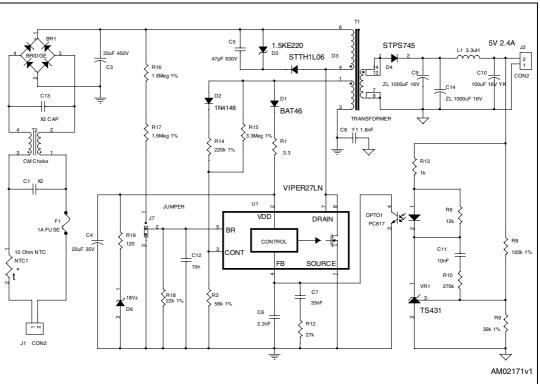


Figure 2. Schematic

 T_A



Table 2. Bill of material					
Reference	Part	Description	Manufacturer		
BR1	DF06M	600 V 1 A diodes bridge	Fairchild \ General Semiconductor		
C1, C13		22 nF X2 capacitor	Evox Rifa		
C3		450 V 33 µF electrolytic capacitor			
C4		35 V 22 µF electrolytic capacitor			
C5	Not mounted	Not mounted			
C6		25 V ceramic capacitor			
C7		25 V ceramic capacitor			
C8		Y1 2.2 nF capacitor			
C9, C14	16 V ZL 1000 µF 10X20	1000 µF 16 V electrolytic capacitor	Rubycon		
C10	16 V 100 µF YK	100 µF 16 V YK rubycon	Rubycon		
C11, C12	10 nF	25 V ceramic capacitor			
D1	BAT46	Diode	STMicroelectronics		
D2	1N4148	Diode			
D3	STTH1L06	Diode	STMicroelectronics		
D4	STPS745	Diode	STMicroelectronics		
D5	1.5KE250	Transil	STMicroelectronics		
D6	BZX79-C18	Zener diode	NXP		
F1	TR5 250 V 1 A	Fuse			
L1		3.3uH			
NTC1	B57236S160M	16 Ω NTC EPCOS			
OPTO1	PC817	Opto coupler Sharp			
R1		3.3 Ω axial resistor			
R16, R17		1600 k Ω 1% axial resistor			
R3		56 k Ω 1% axial resistor			
R6		12 k Ω axial resistor			
R8		120 k Ω 1% axial resistor			
R9		39 kΩ 1% resistor			
R10		270 k Ω axial resistor			
R14		220 k Ω 1% axial resistor			
R12		27 k Ω axial resistor			
R13		1 k Ω axial resistor			
R19		120 Ω axial resistor			
R20		Heatsink			
	l				

Table 2. Bill of material





Reference Part		Description	Manufacturer		
T1	750871111	Switch-mode power transformer	Würth Elektronik		
T2	BU15-4530R4BL	Common-mode choke	Coilcraft		
U1	VIPER27LN	Offline high-voltage converters	STMicroelectronics		
VR1	TS431AIZ-AP	Voltage reference	STMicroelectronics		

 Table 2.
 Bill of material (continued)

1.3 Transformer

The transformer characteristics are listed in the table below.

Table 3.	Transformer	characteristics
	manoronnio	

Properties	Test condition	Value
Manufacturer		Würth Elektronik
Part number		750871111
Primary inductance	Measured at 10 kHz 0.1 V	1.7 mH ± 10%
Leakage inductance	Measured at 100 kHz 0.1 V	60 µH
Primary-to-secondary turn ratio (6 - 4)/(7, 9 - 12, 14)	Measured at 10 kHz 0.1 V	13.5 ± 3%
Primary-to-auxiliary turn ratio (6 - 4)/(3 - 1)	Measured at 10k Hz 0.1 V	5.19 ± 3%
Insulation	Primary to secondary	4 kV



The figures below show the size and pin distances (inches and [mm]) of the transformer.

Figure 3. Transformer size


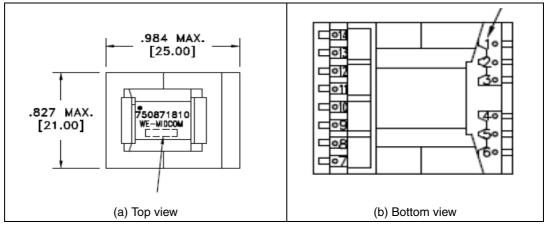


Figure 4. Transformer size and pin diagram [inches (mm)]

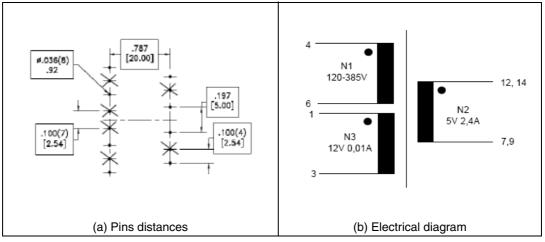



5


2 Testing the board


2.1 Typical board waveforms

Drain voltage and current waveforms were captured for the two nominal input voltages and for the minimum and the maximum voltage of the converter's input operating range.

Figure 5 and *Figure 6* show the drain current and the drain voltage waveforms at the nominal input voltages of 115 V_{AC} and 230 V_{AC} when the load is the maximum (2.4 A). *Figure 7* and *Figure 8* show the same waveforms for the same load condition, but for the minimum (90 V_{AC}) and the maximum (265 V_{AC}) input voltages.

The converter is designed to operate in continuous conduction mode (in full-load condition) at low line. CCM (continuous conduction mode) allows reducing the root mean square current values at the primary side in the power switch inside the VIPER27LN and at the secondary side in the output diode (D4) and in the output capacitors (C9 and C14). Reducing RMS currents means reducing the power dissipation (mainly in the VIPER27LN) and the stress on these components.

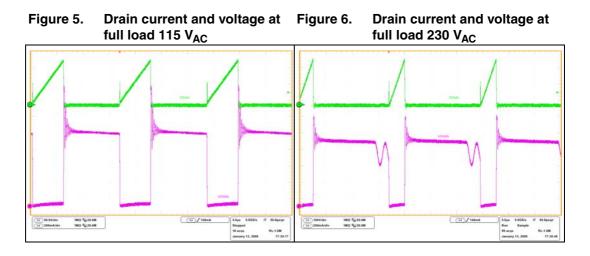

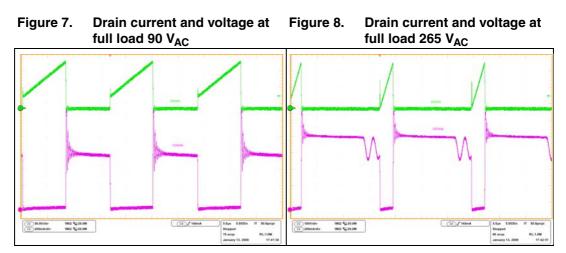

2.2 Precision of the regulation and output voltage ripple

The output voltage of the board was measured in different line and load conditions (see *Table 4*). The output voltage is practically not affected by the line condition. The V_{DD} voltage was also measured to verify that it is inside the operating range of the device.

V AA	No load		Half load		Full	oad
V _{INAC} (V)	V _{OUT} (V)	V _{DD} (v)	V _{OUT} (V)	V _{DD} (V)	V _{OUT} (V)	V _{DD} (V)
90	5.05	9.79	5.05	18.9	5.04	19.8
115	5.05	9.71	5.05	18.9	5.04	19.7
230	5.05	9.37	5.05	18.8	5.04	19.6
265	5.05	9.22	5.05	18.8	5.04	19.6

 Table 4.
 Output voltage and V_{DD} line-load regulation

In a dual-output flyback converter, when just one output is regulated, the unregulated output does not rigorously respect the turn ratio. The unregulated output voltage value depends not only on the turn ratio but also, approximately, from the output current ratio (output current of the regulated output divided by the output current of the unregulated output).

As confirmed from the results in *Table 4*, the V_{DD} voltage (unregulated auxiliary output) increases as the load on the regulated output increases. In order to avoid that the V_{DD} voltage exceeds its operating range, an external clamp was used (D6, R19). See schematic in *Figure 2*.

The ripple at the switching frequency superimposed at the output voltage was also measured and the results are given in *Table 5*. The board is provided with an LC filter for cleaner output voltage. The high-frequency voltage ripple across capacitor C9 (V_{OUT_FLY}), which is the output capacitor of the flyback converter before the LC filter, was also measured to verify the effectiveness of the LC filter and to provide complete results.

	Half load		Full load	
V _{INAC} (V _{RMS})	V _{OUT} (mV)	V _{OUT_FLY} (mV)	V _{OUT} (mV)	V _{OUT_FLY} (mV)
90	25	275	40	172
115	26	275	37	201
230	26	273	36	194
265	25	272	36	195


Table 5.Output voltage ripple

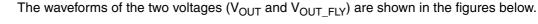

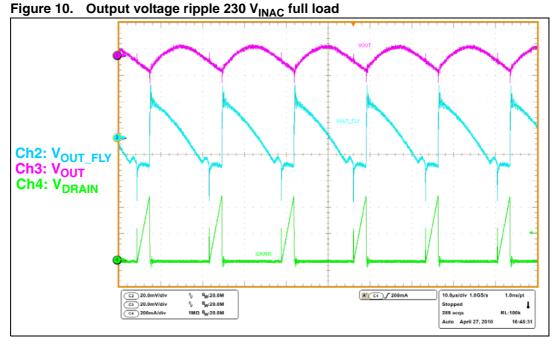


Figure 9.

Ch2: Vour_FLY Ch3: Vour Ch4: V_{DRAIN}



Output voltage ripple 115 VINAC full load



When the device is working in burst mode, a lower frequency ripple is present. In this mode of operation the converter does not supply continuous power to its output. It alternates periods when the power MOSFET is kept off and no power is processed by the converter, and periods when the power MOSFET is switching and power flows towards the converter output. Even if no load is present at the output of the converter, during no switching periods, the output capacitors are discharged by their leakage currents and by the currents needed to supply the circuitry of the feedback loop present at the secondary side. During the

Doc ID 15333 Rev 2



switching period the output capacitance is recharged. The figures below show the output voltage and the feedback voltage when the converter is not loaded. In *Figure 11* the converter is supplied with 115 V_{AC} and with 230 V_{AC} in *Figure 12*.

Figure 11. Output voltage ripple 115 V_{INAC} at no load (burst mode)

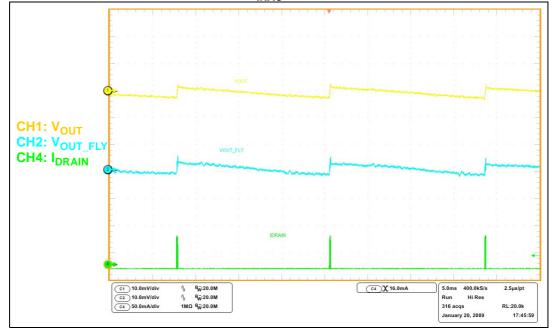


Figure 12. Output voltage ripple 230 V_{INAC} 50 mA at no load (burst mode)

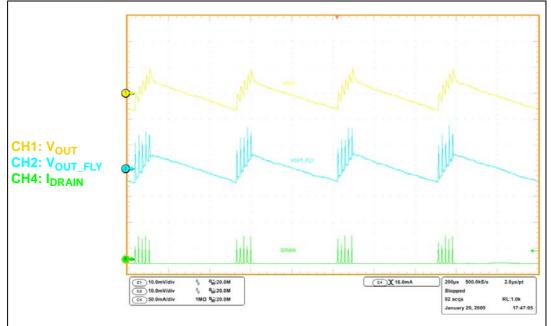




Table 6 shows the measured value of the burst mode related ripple measured in different operating conditions. The measured ripple in burst mode operation is very low and always below 25 mV.

	Edict mede folded output foldge rippie					
V _{IN}	No load (mV)	25 mA load (mV)	50 mA load (mV)			
90	5.1	13.5	14.5			
115	5.2	14.5	15.5			
230	5.4	15.4	16.9			
265	5.7	15.8	18			
	V _{IN} 90 115 230	V _{IN} No load (mV) 90 5.1 115 5.2 230 5.4	V _{IN} No load (mV) 25 mA load (mV) 90 5.1 13.5 115 5.2 14.5 230 5.4 15.4			

Table 6. Burst mode related output voltage ripple

2.3 Efficiency

The efficiency of the converter was measured in different load and line voltage conditions. According to the ENERGY STAR[®] average active mode testing efficiency method, the measurements were done with full load and with 75%, 50%, and 25% of the full load for different input voltages, see *Table 7*.


V		Efficier	ncy (%)	
V _{INAC} (V _{RMS})	Full load (2.4 A)	75% load (1.8 A)	50% load (1.2 A)	25% load (0.6 A)
90	72.46	75.34	78.503	79.841
115	74.96	76.95	79.634	80.395
230	77.70	79.04	80.690	79.990
265	77.80	78.97	80.264	78.287

Table 7. Efficiency

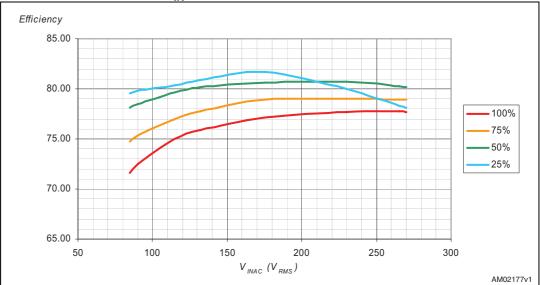
The results were plotted in the following figures for better visibility. *Figure 13* shows the efficiency versus V_{IN} for the four different load values and *Figure 14* shows the efficiency versus load for different input voltages.









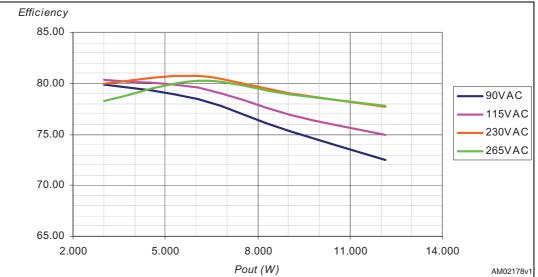



The active mode efficiency is defined as the average of the efficiencies measured at 25%, 50% and 75% of maximum load and the maximum load itself. *Table 8* gives the active mode efficiencies calculated from the *Table 7* measured values. For clarity the values from *Table 8* are plotted in *Figure 15*. *Figure 16* shows the averaged (average was done considering the efficiency at different input voltage) value of the efficiency versus load.

	Table 8.	Active	mode	efficiencies
--	----------	--------	------	--------------

V _{INAC} (V _{RMS})	Efficiency (%)
90	76.54
115	77.98
230	79.35
265	78.83


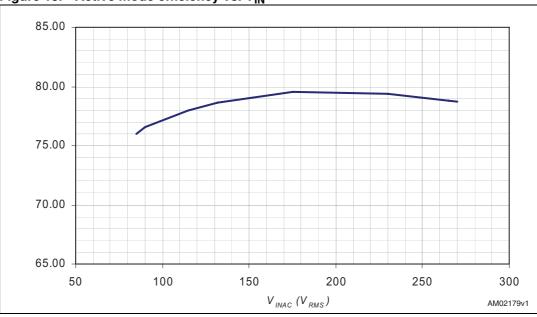


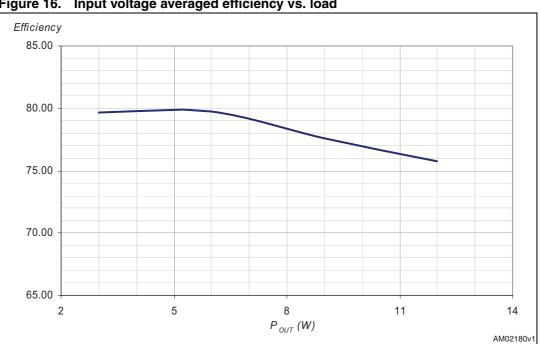

 Table 9.
 Line voltage averaged efficiency vs. load

	,
Load (% of full load)	Efficiency (%)
100	79.39
75	79.85
50	78.67
25	75.56





Input voltage averaged efficiency vs. load Figure 16.

In the version 2.0 of the ENERGY STAR® program requirement for single voltage external AC-DC power supplies (see Section 4: References), the power supplies are divided in two categories: low-voltage power supplies and standard power supplies with respect to the nameplate output voltage and current. An external power supply, in order to be considered a low-voltage power supply, needs to have a nameplate output voltage lower than 6 V and a nameplate output current greater than or equal to 550 mA.

The tables below give the EPA energy efficiency criteria for AC-DC power supplies in active mode for standard models and for low-voltage models, respectively.

Nameplate output power (Pno)	Minimum average efficiency in active mode (expressed as a decimal)
$0 \text{ W} < P_{no} \le 1 \text{ W}$	= 0.48 * P _{no} + 0.140
$1 \text{ W} < P_{no} \le 49 \text{ W}$	= [0.0626 * In (P _{no})] + 0.622
P _{no} > 49 W	= 0.870

Table 10.	Energy efficiency criteria for standard models
-----------	--

Table 11. Energy efficiency criteria for low-voltage models

Nameplate output power (Pno)	Minimum average efficiency in active mode (expressed as a decimal)
$0 \text{ W} < P_{no} \le 1 \text{ W}$	= 0.497 * P _{no} + 0.067
$1 \text{ W} < P_{no} \leq 49 \text{ W}$	= [0.075 * ln (P _{no})] + 0.561
P _{no} > 49 W	= 0.860



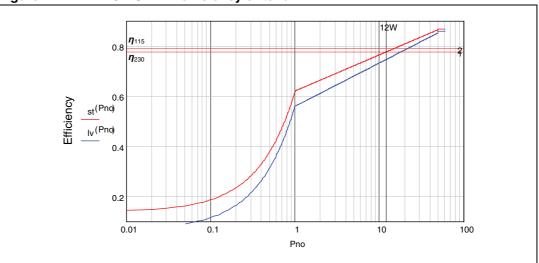


Figure 17. ENERGY STAR[®] efficiency criteria

Figure 17 shows the efficiency criteria where the red line is the criteria for the standard model and the blue line is the criteria for the low-voltage model. The P_{NO} axe is in logarithmic scale.

The power supply presented belongs to the low-voltage power supply category and, in order to be compliant with ENERGY STAR[®] requirements, needs to have efficiency higher than 74.7%. For all the considered input voltages, the efficiency results (see *Table 8*) are higher than the recommended value.

2.4 Light-load performance

The input power of the converter was measured in no load condition, with brownout protection disabled (see *Section 2.8*) for different input voltages and the results are given in *Table 12*.

V _{INAC} (V _{RMS})	Pin (mW)	f _{SW_AVG} (kHz)
90	15	0.590
115	16	0.558
230	24	0.434
265	29	0.401

Table 12. No-load input power (no brownout)

In version 2.0 of the ENERGY STAR[®] program the power consumption of the power supply when it is not loaded is also considered. The criteria for compliance are given in the table below.

 Table 13.
 Energy consumption criteria for no load

Nameplate output power (Pno)	Maximum power in no load for AC-DC EPS
$0 \text{ W} < P_{no} \le 50 \text{ W}$	< 0.3 W
50 W < P _{no} < 250 W	< 0.5 W



The performance of the VIPER27LN board is much better than required. The power consumption is about twelve times lower than the ENERGY STAR[®] limit. Even if the results seem to be disproportionally better than the requirements, it is worth mentioning that often AC-DC adapter or battery charger manufacturers have very strict requirements concerning no-load consumption and if the converter is used as an auxiliary power supply, the line filter of the entire power supply is much bigger and considerably increases the standby consumption.

Even if the ENERGY STAR[®] program does not have other requirements regarding light-load performance, in order to give complete information we have provided the input power and efficiency of the demonstration board in two other low-load cases also. *Table 14* and *Table 15* show the performances when the output load is 25 mW and 50 mW respectively.

V _{IN_AC}	P _{OUT} (mW)	P _{IN} (mW)	Eff. (%)	P _{IN} -P _{OUT} (mW)	f _{SW_AVG} (kHz)
90	25.760	48	53.22	22.640	2.017
115	26.760	49	54.95	21.940	1.886
230	25.760	61	41.95	35.640	1.461
265	25.760	67	38.74	40.740	1.355

Table 14.Low-load performance POUT = 25 mW

Table 15.	Low-load performance P _{OUT} = 50 mW
-----------	---

V _{IN_AC}	P _{OUT} (mW)	P _{IN} (mW)	Eff. (%)	P _{IN} -P _{OUT} (mW)	f _{SW_AVG} (kHz)
90	51.510	80	64.39	28.490	3.407
115	51.510	82	62.82	30.490	3.177
230	51.510	98	52.56	46.490	2.435
265	51.510	104	49.53	52.490	2.284

The input power and the average switching frequency versus the input voltage for different load conditions are shown in the following figures.



57



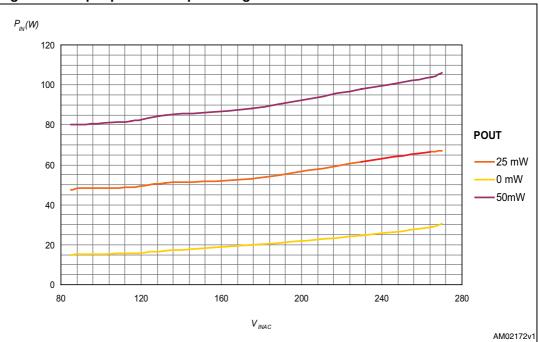


Figure 18. Input power vs. input voltage for different loads

 


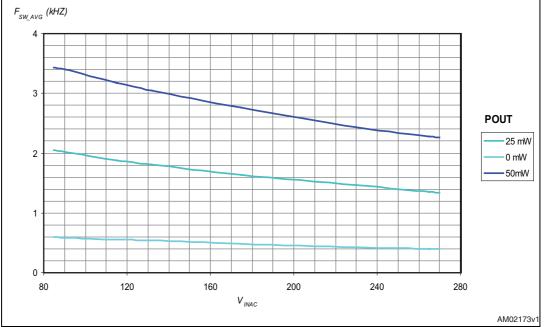


Depending on the equipment supplied, we can have several criteria to measure the standby or light-load performance of a converter. One criterion is the measure of the output power when the input power is equal to one watt. *Table 16* gives the output power needed to have 1 W of input power in different line conditions and *Figure 20* illustrates this.

Table 10. Output power when the input power is 1 w							
V _{IN} (V _{RMS})	P _{IN} (mW)	P _{OUT} (mW)	Efficiency (%)	Pin-Pout (mW)			
90	1000	767.1	76.71	232.853			
115	1000	762.1	76.21	237.910			
230	1000	752.0	75.20	248.024			
265	1000	726.2	72.62	273.815			

Table 16.Output power when the input power is 1 W

 

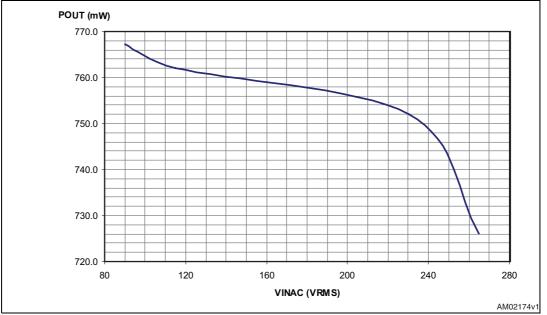

If brownout protection is required, for the same load condition the input power increases. The brownout external circuit (R16, R17 and R18 see schematic in *Figure 2*) is connected in parallel with a bulk capacitor (C3 in the schematic) and some power is dissipated on it according to the voltage across the bulk capacitor. The following formula gives the additional power dissipation in the brownout circuit:

Equation 1

$$\mathsf{P}_{\mathsf{BR}_LOSS} = \frac{\mathsf{V}_{\mathsf{BULK}_\mathsf{RMS}}^2}{(\mathsf{R16} + \mathsf{R17} + \mathsf{R18})}$$

In light-load condition the voltage across bulk capacitor can be considered constant and equal to the peak of the AC input voltage. Considering the worst case of maximum input voltage, the dissipation in the brownout circuit is:

Equation 2

$$P_{\text{BR}_\text{LOSS}} = \frac{V_{\text{ACMAX}_\text{PK}}^2}{(\text{R16} + \text{R17} + \text{R18})} = \frac{(\sqrt{2} \cdot 265 \cdot \text{V})^2}{3222 \cdot \text{k}\Omega} \cong 43 \text{mW}$$



2.5 Overload protection

The VIPER27LN has several protections, one of which prevents converter damage in case of overload or output short-circuit. If the load power demand increases, the output voltage decreases and the feedback loop reacts by increasing the voltage on the feedback pin. The increase of the feedback pin voltage leads to the PWM current set point increase which increases the power delivered to the output until this power equals the load power. If the load power demand exceeds the converter's power capability (which can be adjusted using R_{LIM}), the voltage on feedback pin continuously rises but the power delivered no longer increases. When the feedback pin voltage exceeds V_{FB_lin} (3.3 V typ.), VIPER27LN logic assumes that it is a warning for an overload event. Before shutting down the system, the device waits for a period of time set by the capacitor present on the feedback pin. In fact if the voltage on the feedback pin exceeds V_{FB_lin} , the internal pull-up is disconnected and the pin starts sourcing a 3 A current that charges the capacitor connected to it. As the voltage on the feedback pin reaches the V_{FB_olp} threshold (4.8 V typ.), VIPER27LN stops switching and is not allowed to switch again until the V_{DD} voltage goes below $V_{DD_RESTART}$ (4.5 V typ.) and rises again up to V_{DD_ON} (14 V typ.).

The following waveform shows the behavior of the converter when the output is shorted.

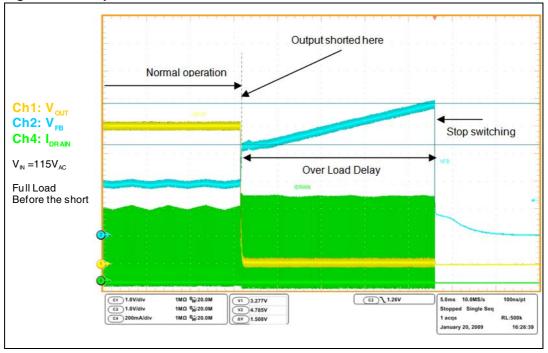


Figure 21. Output short-circuit

If the short-circuit is not removed, the system starts to work in auto-restart mode. The behavior, when a short-circuit is permanently applied on the output, is a short period of time where the MOSFET is switching and the converter tries to deliver to the output as much power as it can, and a longer period where the device is not switching and no power is processed.

The duty cycle of power delivery is very low (around 1.55%) so the average power throughput is also very low (see the figure below).

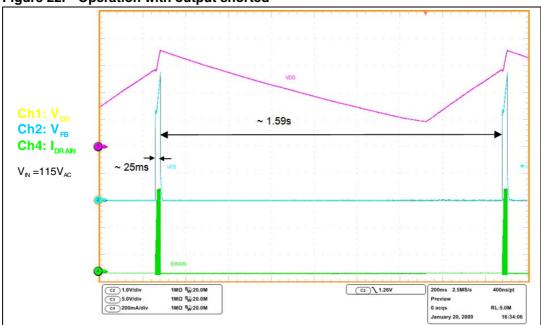


Figure 22. Operation with output shorted

2.6 Secondary winding short-circuit protection

The VIPER27LN is provided with an adjustable first level of primary overcurrent limitation that switches off the power MOSFET if this level is exceeded. This limitation acts cycle by cycle and its main purpose is to limit the maximum deliverable output power. A second level of primary overcurrent protection is also present and in this case it is not adjustable, it is fixed to 1 A (typical value). If the drain current exceeds this 2^{nd} OCP (second overcurrent protection) threshold, the device enters a warning state. The next cycle the MOSFET is switched on, and if again the second level of overcurrent protection is exceeded, the device assumes that a secondary winding short-circuit or a hard saturation of the transformer is happening and stops the entire operation. In order to re-enable the operation, the V_{DD} voltage has to be recycled which means that V_{DD} has to go down to V_{DD_RESTART}, then rise up to V_{DD_ON}. When the VIPER27LN is switched on again (V_{DD} equals V_{DD_ON}), the MOSFET can start to switch again. If the cause of the 2^{nd} overcurrent protection activation is not removed, the device goes in auto-restart mode.

This protection was tested on the present board. The secondary winding of the transformer was shorted, in different operating conditions. The following figures show the behavior of the system during these tests.



5

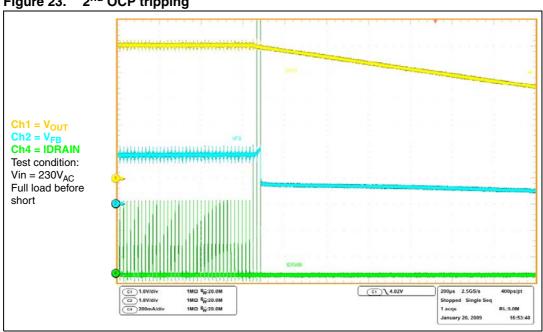


Figure 23. 2nd OCP tripping

In *Figure 23* when the board was working in full-load condition with an input voltage of 115 V_{AC} , the secondary winding was shorted. The short on the secondary winding leads to a high drain current. After two switching cycles, the system stops and continuous running with high currents in the primary as well as in the secondary windings and through the power section of the VIPER27LN is avoided. *Figure 24* shows the situation when a permanent short-circuit is applied on the secondary windings. Most of the time the power section of the VIPER27LN is off, eliminating any risk of overheating.



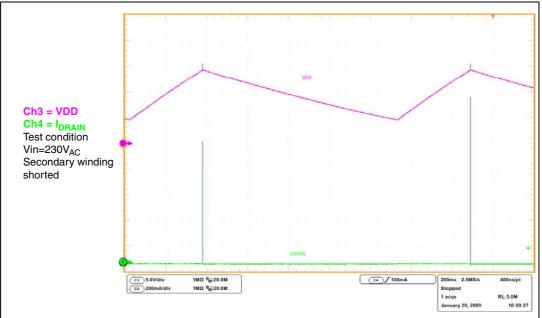


Figure 24. Operating with secondary winding shorted - restart mode

 2.7 Output overvoltage protection

An output overvoltage protection is implemented by monitoring the voltage across the auxiliary winding during the MOSFET off-time, through the D2 diode and the resistor divider R3 and R14 (see schematic of *Figure 2*) connected to the CONT pin of the VIPER27LN. If the voltage on the pin exceeds the V_{OVP} thresholds (3 V typ.), an overvoltage event is assumed and the power section is no longer allowed to switch on. To re-enable operation, the V_{DD} voltage has to be recycled. In order to provide high noise immunity and avoid that spikes erroneously trip the protection, a digital filter was implemented so the CONT pin has to sense a voltage higher than V_{OVP} for four consecutive cycles before stopping operation.



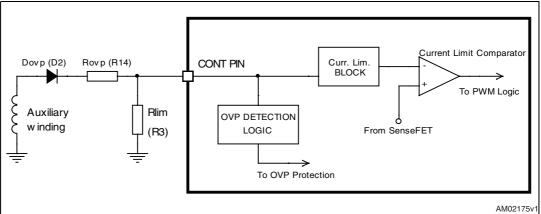


The value of the output voltage when the protection has to be tripped can be set by properly selecting the resistor divider R3 and R14. R3 is selected according to the maximum power that the converter has to provide to the output, and R14 is selected according to *Equation 3*:

Equation 3


$$R_{OVP_(R14)} = \frac{R_{LIM_(R3)}}{V_{OVP}} \cdot \left(\frac{N_{AUX}}{N_s} \cdot V_{OUT_OVP} - V_{drop_D_{ovp_(D2)}} - V_{OVP}\right)$$

The protection was tested by disconnecting the opto-coupler from the feedback pin and applying a minimum load to the converter. In this way the converter operates in open loop and delivers the maximum power that it can to the output. The excess of power with respect to the load charges the output capacitance, increasing the output voltage since the OVP is tripped and the converter stops working.

 In *Figure 26* it is possible to see that the output voltage increases and, as it reaches the value of 5.58 V, the converter stops switching. In the same figure the CONT pin voltage (Ch1, yellow waveform) is shown. The crest value of the CONT pin voltage tracks the output voltage.





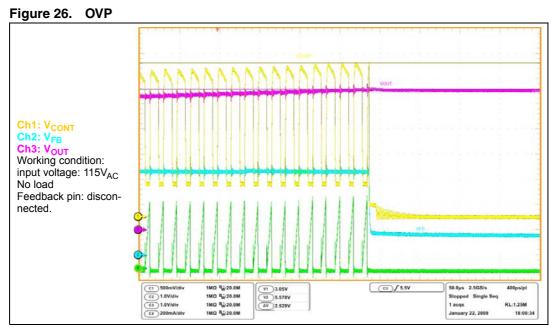

The test was performed in different line and load conditions, to check the dependence of the output voltage value, when the protection is activated, on the converter's input voltage and load.

The results are shown in Table 17.

	V _{OUT_OVP} (V)							
V _{IN} (V _{RMS})	Load							
	No load	25% (0.6 A)	50% (1.2 A)	75% (1.8 A)	100% (2.4 A)			
90	5.56	5.50	5.46	5.45	5.45			
115	5.56	5.51	5.49	5.48	5.46			
230	5.59	5.55	5.52	5.53	5.53			
265	5.59	5.54	5.54	5.53	5.53			

Table 17. Input and output load

The variation with load and line condition is very low ([5.45 V; 5.59 V],

 ΔV_{OUT_OVP} = 140 mV), less than 3%. Considering a precision of the OVP threshold on the CONT pin of 10% ([2.7 V; 3.3 V]), using as R_{OVP} and R_{LIM} 1% precision resistance and with a turn ratio between the secondary and auxiliary windings that has a precision of 5%, it is possible to fix the output overvoltage 20%, 25% higher than the nameplate output voltage of the converter, without risk of undesired protection tripping due to the spread in the values of the components (R3 and R14), of the transformer parameter (turn ratio) and of the VIPER27LN parameter (V_{OVP}).


It is possible to not implement this protection if it is not necessary, by not mounting diode D2 and resistor R14, thus reducing the number of components.




2.8 Brownout protection

The brownout protection is basically an unlatched device shutdown functionality whose typical use is to sense flyback converter input undervoltage. The VIPER27LN has a pin (BR, pin 5) dedicated to this function that must be connected to the DC HV bus. If the protection is not required, it can be disabled by connecting the pin to ground. In the present converter the brownout protection is implemented but can be disabled by changing the setting of jumper J7 (see schematic in *Figure 2*). The settings of jumper J7 are shown in *Figure 27* and *Figure 28*. The shutdown of the converter is accomplished by means of an internal comparator internally referenced to 450 mV (typ, V_{BRth}) that disables the PWM if the voltage applied to the BR pin is below the internal reference, as shown in *Figure 29*. The PWM operation is re-enabled as the BR pin voltage is more than 450 mV plus 50 mV of voltage hysteresis that ensures noise immunity. The brownout comparator is also provided with current hysteresis. An internal current generator is ON as long as the voltage applied to the brownout pin is below 450 mV and is OFF if the voltage exceeds 450 mv plus the voltage hysteresis.

Figure 27. Jumper J7 setting, brownout disabled

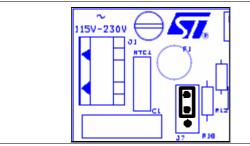

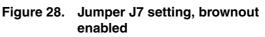


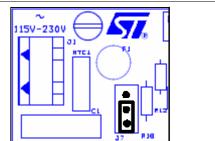


Figure 29. Brownout protection

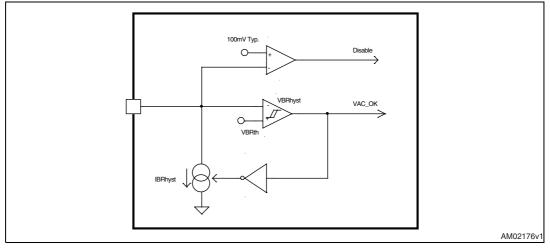



The current hysteresis provides an additional degree of freedom. It is possible to set the ON threshold and the OFF threshold for the flyback input voltage separately by properly choosing the resistors of the external divider. The following relationships can be established for the ON (V_{IN} _{ON}) and OFF (V_{IN} _{OFF}) thresholds of the input voltage:

Equation 4

$$V_{IN_OFF} = V_{BRth} \cdot \left(\frac{R_{H} + R_{L}}{R_{L}}\right)$$

Equation 5

$$V_{IN_ON} = \left(V_{BRth} + V_{BRhyst}\right) \cdot \left(\frac{R_{H} + R_{L}}{R_{L}}\right) + R_{H} \cdot I_{BRhyst}$$

where $I_{BRhyst} = 8.5 \ \mu A$ (typ.) is the current hysteresis, $V_{BRhyst} = 50 \ mV$ (typ.) is the voltage hysteresis and $V_{BRth} = 450 \ mV$ (typ.) is the brownout comparator internal reference.

One purpose of this protection is to stop operation of the converter when the line voltage is too low, avoiding an excessive root mean square current value flowing inside the main switch and consequently its overheating. Another purpose is to avoid a false restart of the converter and then having a monotonic decay to zero of the output voltage when the converter itself is unplugged from the mains. A typical situation, in most cases for converters designed for the European range (230 V_{AC}), could be a converter that, when unplugged, shuts down due to the overload protection (due to the low input voltage the converter is not able to supply the full power), but the voltage on the bulk capacitor is higher than V_{DRAIN} RESTART so the device restarts and the output voltage rises again. This situation could be dangerous for some loads, and in many applications it is better to avoid it.

The following figures show how the brownout protection works in the VIPER27LN board when used. *Figure 30* shows the behavior of the board when the input voltage is changed from 90 V_{AC} to 75 V_{AC} with a full load applied. The system stops switching and the output load, no longer supplied, decays monotonically to zero.



57


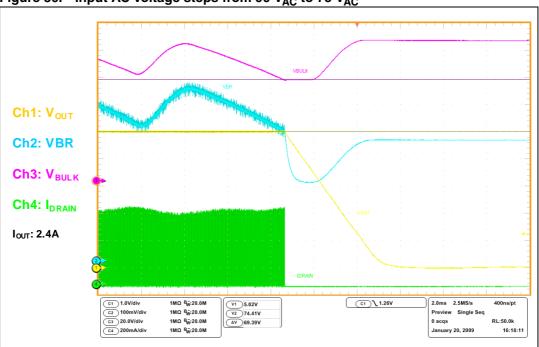



Figure 30. Input AC voltage steps from 90 V_{AC} to 75 V_{AC}

Figure 31. Input voltage steps from 90 V_{AC} to 0

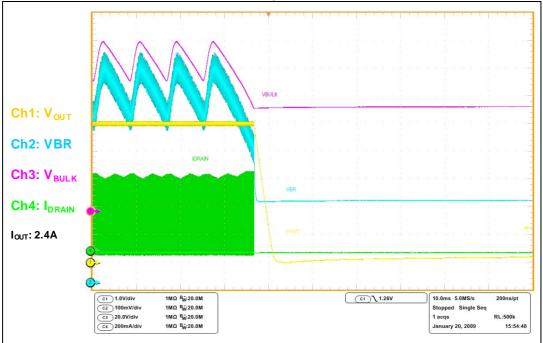

2.9 EMI measurements

A pre-compliance test for EN55022 (Class B) European normative was also performed and the results are shown in the two figures below.

 


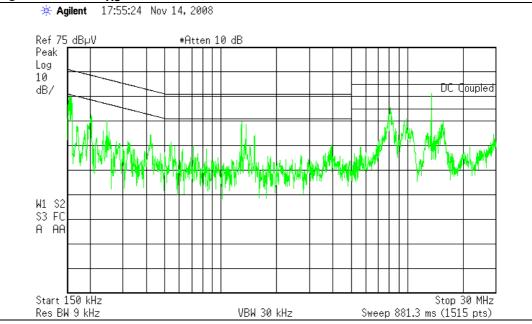


Figure 33. 230 V_{AC}

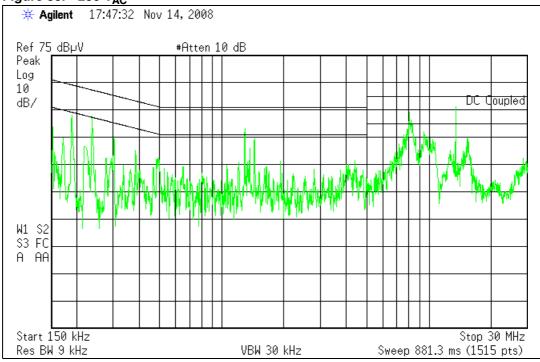



3 Conclusion

The presented flyback converter is suitable for different applications and can be used as an external adapter or as an auxiliary power supply in consumer products. Special attention was given to low-load performance and the bench results are good with very low input power in light-load condition. The efficiency was compared to the requirements of the ENERGY STAR[®] program (version 2.0) for external AC/DC adapters with very good results in that the measured active mode efficiency was always higher than the minimum required.

4 References

[1] ENERGY STAR $^{\!\! \ensuremath{\mathbb{R}}}$ program requirements for single voltage external AC-DC adapter (Version 2.0)

[2] VIPER27 datasheets



5 Revision history

Table 18. Document revision history

D	ate	Revision	Changes	
07-Ma	ay-2010	1	Initial release	
06-Ap	or-2011	2	Modified: Table 2: Bill of material	



Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2011 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan -Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com

Doc ID 15333 Rev 2

