

AN842

APPLICATION NOTE

7-segment display drive using the ST6-REALIZER

INTRODUCTION

Seven segment devices are often preferred in display applications where high luminescence is required, both for indoor and outdoor applications.

Controlling the display is normally but one of many tasks handled by a typical application. The techniques described in this note are of a general nature and may be applied to a variety of applications.

Hardware considerations are reviewed and generation of control software using the ST6-REALIZER is described.

1 PRINCIPLE OF OPERATION

A 7-Segment Display consists of 7 LED's arranged in a figure-eight pattern, such that by selectively powering various combinations of segments alphanumeric characters may be displayed; a further LED is present which, when powered, causes a dot or decimal point to be displayed (Figure 1). Each LED is turned on by forward biasing its respective anode, all segment cathodes being commoned (Common Anode devices also exist).

The Digital Point LED is generally used to display numbers containing a non-integer part. Table 1 illustrates the required segment patterns for numeric representation, including the optional Decimal Point character.

Figure 1. Structure of a 7 segment display

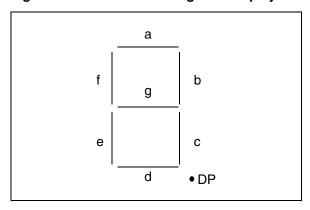


Table 1. LED's turned on for a given digit

	а	b	С	d	е	f	g	DP
0	1	1	1	1	1	1	0	Х
1	0	1	1	0	0	0	0	Х
2	1	1	0	1	1	0	1	Х
3	1	1	1	1	0	0	1	Х
4	0	1	1	0	0	1	1	Х
5	1	0	1	1	0	1	1	Х
6	1	0	1	1	1	1	1	Х
7	1	1	0	0	0	0	0	Х
8	1	1	1	1	1	1	1	Х
9	1	1	1	1	0	1	1	Х
DP	Х	Х	Х	Х	Х	Х	Х	1

X = Don't care

Biasing can be either continuous or multiplexed as long as the refresh frequency is high enough to ensure image persistence for the human eye (at least 20 cycles per second to avoid flicker).

2 PRACTICAL IMPLEMENTATION

2.1 Hardware layout

Biasing is achieved using the ST62 MCU's I/O lines. One line is used to bias the common cathode, while 7 lines are assigned to LED segments a - g and a further line, if required, to the DP. Each segment of the display can thus be turned on or off, depending on the value written to the corresponding I/O line.


2.2 Software generation

Control software is automatically generated by the ST6-REALIZER, on the basis of a functional description.

The digit to be displayed is available as a variable, "Digit value". The display control software must then write the relevant value to the I/O lines in accordance with Table 1.


The ST6-REALIZER library provides a component, the *lookuptable*, for this kind of application. This table assigns to each variable input value a constant output value defined in the ROM memory of the ST62 MCU. If a lookup table is defined for each LED or segment, the output data is of BIT type as shown in the Figure 2 for segment g.

Figure 2. Lookup table for segment g

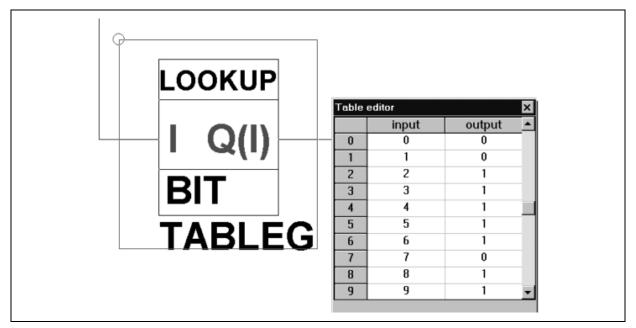

Finally, the resultant bits are transferred to the I/O port via the digout components (Figure 3).

Figure 3. 7-segment drive with bitwise lookup table

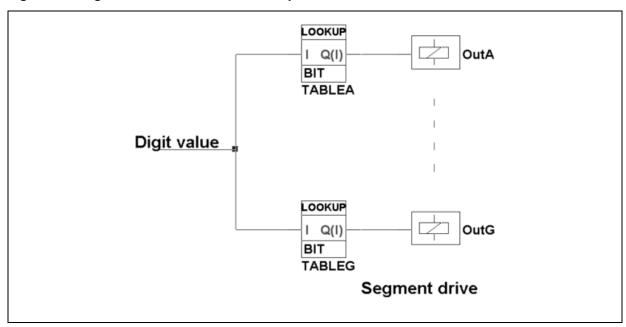

However this approach implies the use of 7 lookup tables (1 for each segment). This means the MCU has to scan a table 7 times, with consequent impact on execution time. A better alternative is to concatenate the 7 segments into a bytewise variable, and therefore use only one lookup table with output data of UBYTE type. In this case, the content of the lookup table is a byte defined as described in Table 2:

Table 2. 7-segment coding in one byte

D7	D6	D5	D4	D3	D2	D1	D0
Don't care	g	f	е	d	С	b	а

The resulting byte is then transferred to 7 *digout* components by using an unpacker component, *bunpack*, and gives the complete description as per Figure 4.

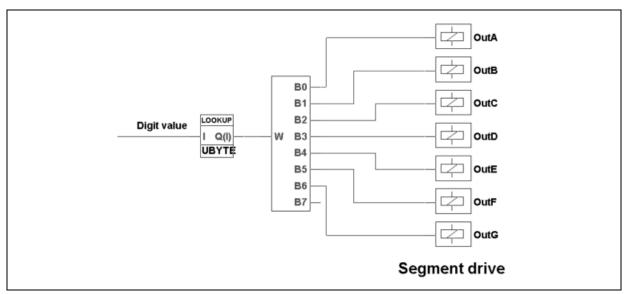


Figure 4. 7-segment drive with bytewise lookup table

By using the simulation features of the ST6-REALIZER, the reduction in execution time has been quantified as follows:


7 bitwise lookup tables: 5170µs 1 bytewise lookup table: 1125µs

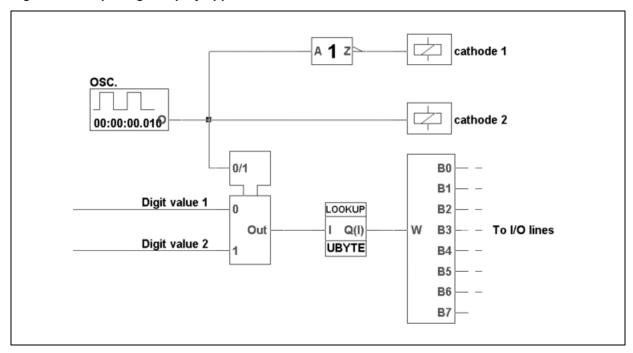2.3 Multiple digit display

These concepts can be extended to multiple-digit display systems. The simplest approach is to drive each digit separately, which requires at least 7 I/O lines per digit (excluding DP and assuming the common cathodes are tied to an external supply). It is possible to greatly reduce the number of I/O lines by adopting a multiplexing technique. In this scheme, each of the segments are common for all display digits, while the cathodes are driven sequentially to select the active digit. The 7 I/O lines which drive the segments are then driven in accordance with the currently driven cathode. The lookup table is common to all digits but its input will vary depending on the digit to be displayed.

The input thus depends on the cathode selection signal, which must switch with a period shorter than the persistence time of the human eye in order to avoid flicker. In the present case, 20ms has been chosen. Figure 5 illustrates such an application, where two digits are used to display values ranging from 0 to 99.





3 REVISION HISTORY

Table 3. Revision history

Date	Revision	Description of changes	
November 1995	1	Initial release	
13-June-2008	2	Logo modified	

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2008 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com