

# AN-7701

## FL7701 Design Tool Flow

### Overview

This document is intended to provide in-depth guidance to using the Fairchild Design Tool for FL7701. Use the Design Tool with the product datasheet.

### Step-by-Step


1. Enter the input voltage.
2. Enter the LED characteristics (forward voltage).
3. Enter the LED counts.
4. Enter the LED peak current.
5. Enter the LED rms current.
6. Enter the target system efficiency.
7. Enter the desired switching frequency.

### Example:

- 220V Input Voltage
- 3.5V Forward Voltage
- 10 LEDs in series
- 500mA<sub>pk</sub>
- 300mA<sub>rms</sub>
- 85% efficiency
- 45kHz

**Table 1. Design Values to Enter**

Item		Value	Units
Maximum Input Voltage	$V_{IN,MAX,AC}$	220	V
LED Forward Voltage	$V_f$	3.5	V
Number of LEDs	$N_{number\_LED}$	10	EA
LED Peak Current	$I_{LED,peak}$	500	mA
LED rms Current	$I_{VAE,rms}$	300	mA
Efficiency	$E_{ff}$	85	%
Switching Frequency	$f_{SW}$	45	kHz

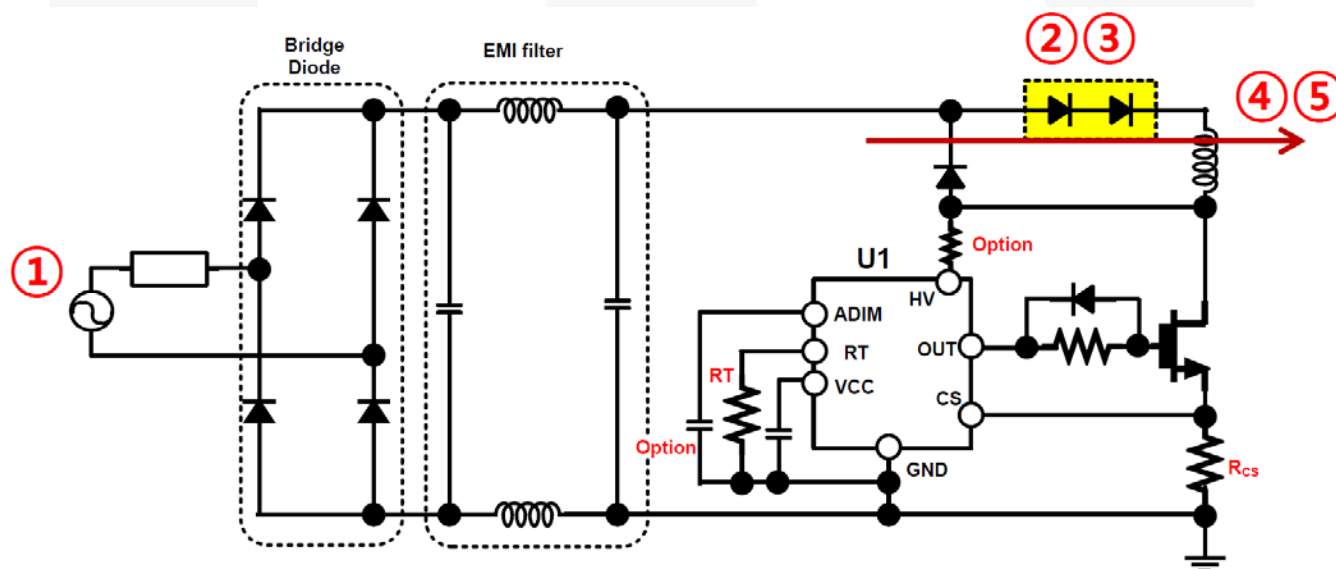

**Figure 2. Output Capacitor Selection Guide Plot**

## Calculation Results

**Table 2. Internal Process**


Item		Value	Units
Current Ripple	$\Delta I =$	151.5	mA
LED Minimum Current	$I_{MIN} =$	348.53	mA
LED Current Ave. Peak	$(I_{MAX} + I_{MIN}) / 2 =$	424	mA
Minimum Duty Cycle	$D_{MIN} =$	13.237	%
Output Voltage	$V_O =$	35.000	V

**Table 3. Results**

Item		Value	Units
Inductance	$L_M =$	4.455	mH
Current Sensing Resistor	$R_{CS} =$	1.000	$\Omega$
Frequency Setting Resistor	$R_f =$	44.919	k $\Omega$

**Table 4. Expected Power**

Item		Value	Units
Expected Output Power	$P_{OUT} =$	10.500	W
Expected Input Power	$P_{IN} =$	12.353	W

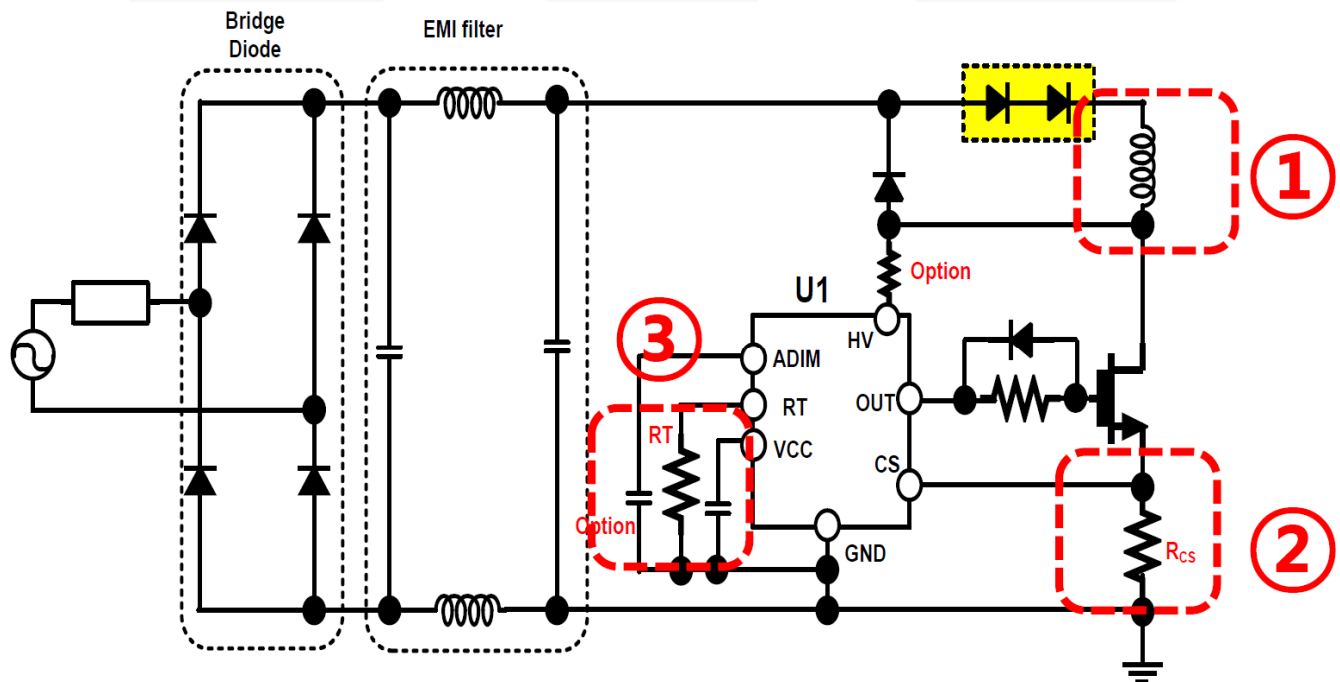

**Figure 3. Output Capacitor Selection Guide Plot and Table**

**Notes:**

1. Inductance.
2. Sensing resistor value ( $R_{CS}$ ).
3.  $R_T$  value.
4. Can omit  $R_T$ , when  $f_{SW}$  is close to 45kHz.

## Related Resources

Locate the Design Tool at:

[http://www.fairchildsemi.com/design\\_tools/led-driver-design-tool/](http://www.fairchildsemi.com/design_tools/led-driver-design-tool/)

Consult the product datasheet at:

[\*FL7701 — Smart Non-isolated PFC Buck LED Driver\*](#)

Follow us on Twitter at:

[twitter.com/fairchildSemi](https://twitter.com/fairchildSemi)

View product and company videos, listen to podcasts, and comment on our blog at:

[www.fairchildsemi.com/engineeringconnections](http://www.fairchildsemi.com/engineeringconnections)

Visit us on Facebook at:

[www.facebook.com/FairchildSemiconductor](https://www.facebook.com/FairchildSemiconductor)

---

### DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION, OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

### LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION.

As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.