

## AN9006

### IGBT Application Note For Camera Strobe



#### Camera Strobe System Summary

The Camera Strobe System (Portable & DSC) is a lighting system for taking pictures in relatively dark areas, without the accompanying negative effect on picture quality. The strobe system is becoming smaller, lighter and easier to control, increasing the popularity of DSC and portable automatic cameras.


#### 1) Strobe System Control Methods

The control methods are largely divided into two groups: One uses SCR, and the other uses IGBT. The advantages and disadvantages of both methods are compared below:


**Table 1: Comparison of Control Methods**

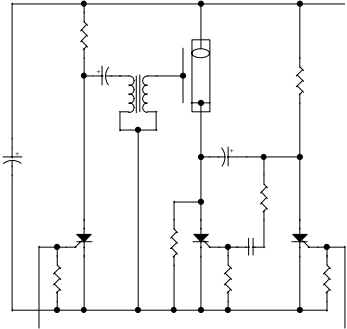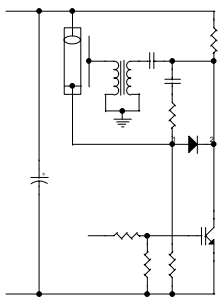Item	SCR Control	IGBT Control	Remarks
Circuit Configuration	<ul style="list-style-type: none"> <li>Complicated</li> </ul> 	<ul style="list-style-type: none"> <li>Simple (Can be directly operated from Logic)</li> </ul> 	
Current Capacity	<ul style="list-style-type: none"> <li>Up to hundreds Amp.</li> </ul>	<ul style="list-style-type: none"> <li>Up to 150A (@ logic level)</li> </ul>	
Disadvantages	<ul style="list-style-type: none"> <li>Low battery efficiency (full electric discharge)</li> <li>Hard to achieve red eye prevention function</li> <li>Need SCR for turn-off</li> <li>Limitation in luminosity control</li> </ul>	<ul style="list-style-type: none"> <li>High intensity luminosity is difficult.</li> </ul>	
Advantages	<ul style="list-style-type: none"> <li>High intensity luminosity is possible</li> </ul>	<ul style="list-style-type: none"> <li>Fast response time</li> <li>Red eye prevention function is possible</li> <li>High battery Efficiency</li> </ul>	


**Figure 1: Camera System Block Diagram**

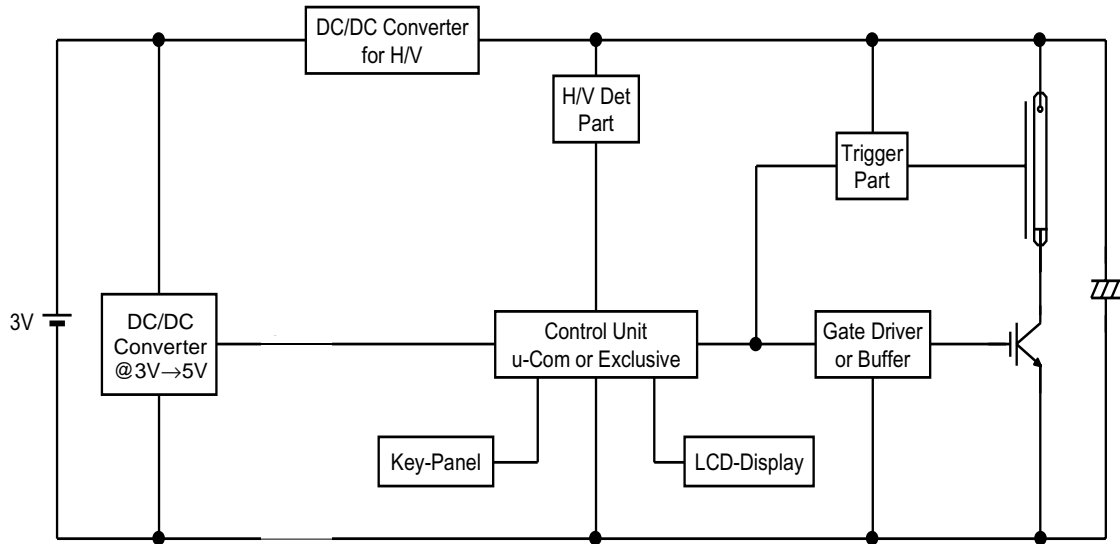

**Figure 2: Strobe System's Circuit Diagram**

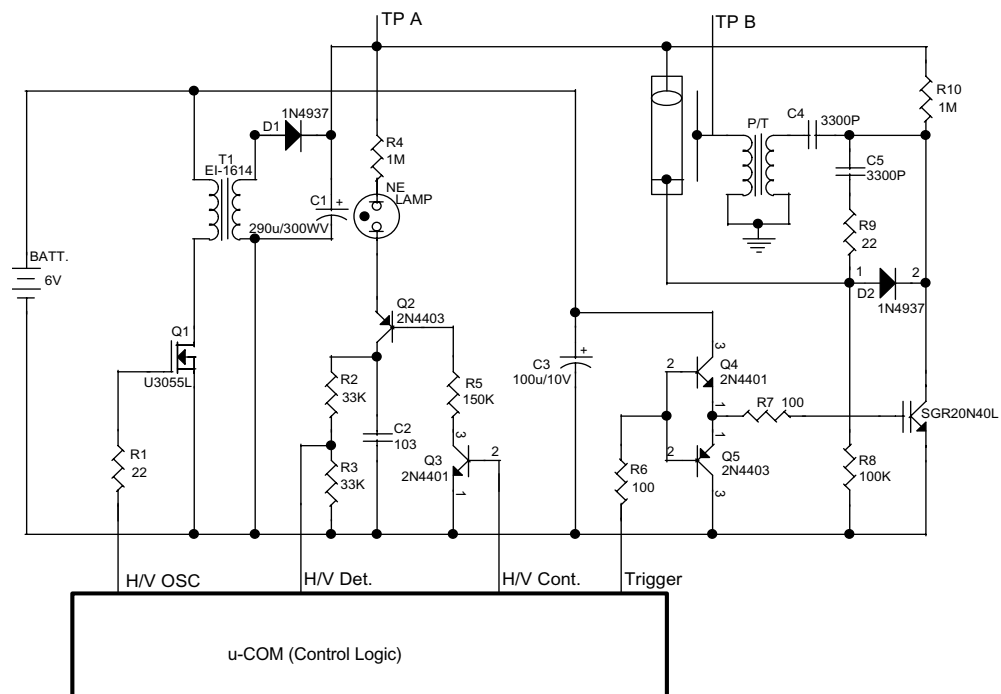

**Figure 3: Timing Chart for Each Block**

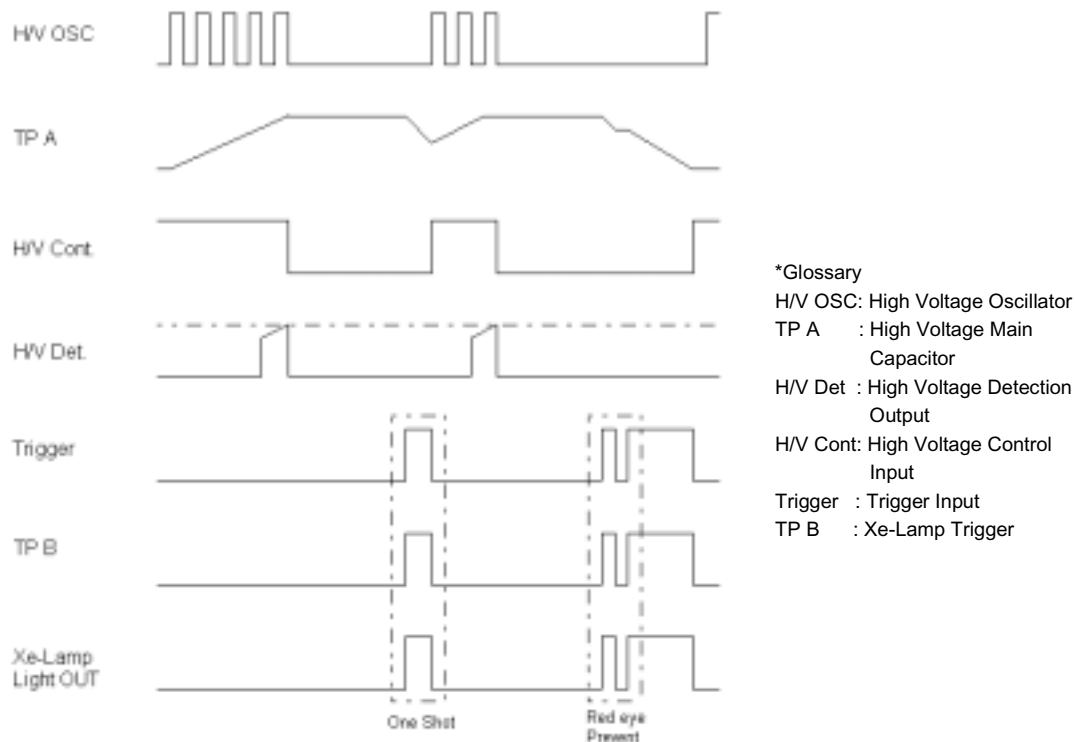


< Timing Chart for Each Block >

## 2) Control Power Block Configuration

Portable cameras and DSC use 3 V or 6 V batteries, but lately the 3 V battery is becoming more prevalent. When using a 3 V power source, the IGBT's gate drive Voltage is insufficient, even with a logic level IGBT. Hence, a boost-up circuit is reequired for DC power voltage. The boost-up circuit, used in a portable strobe system, is divided into two types.


1. Boost-up circuit using u-COM  
The circuit has the PWM Controller function built-in within the u-COM for system control, and produces about 100-150 KHz of S/W frequency for reducing transformer size. Duty control functionality is also available.
2. Boost-up circuit using a DC/DC Converter  
This is the most commonly used circuit. It is used independently without the control of a u-COM. The converter used, most often, is the RS5RM series type with RICOH's PWM and built in voltage detection . This circuit mainly boosts 3 V power up to 5 V. It has a switching frequency of 50 KHz, and the duty is variable up to a maximum of 90%. When the output voltage is lower than a specific value, it is compensated for by increasing the duty. When it is higher than a set value, it saves energy in the coil while the internal TR is on. When the TR is turned off, the 3 V power voltage and organic voltage are combined to provide 5 V output.

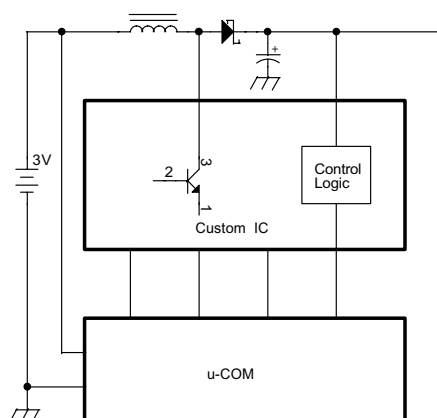**(b) Boost-up Circuit using a DC/DC Converter**




### 3). Fairchild Strobe IGBT Demo System

### Figure 5: System Circuit

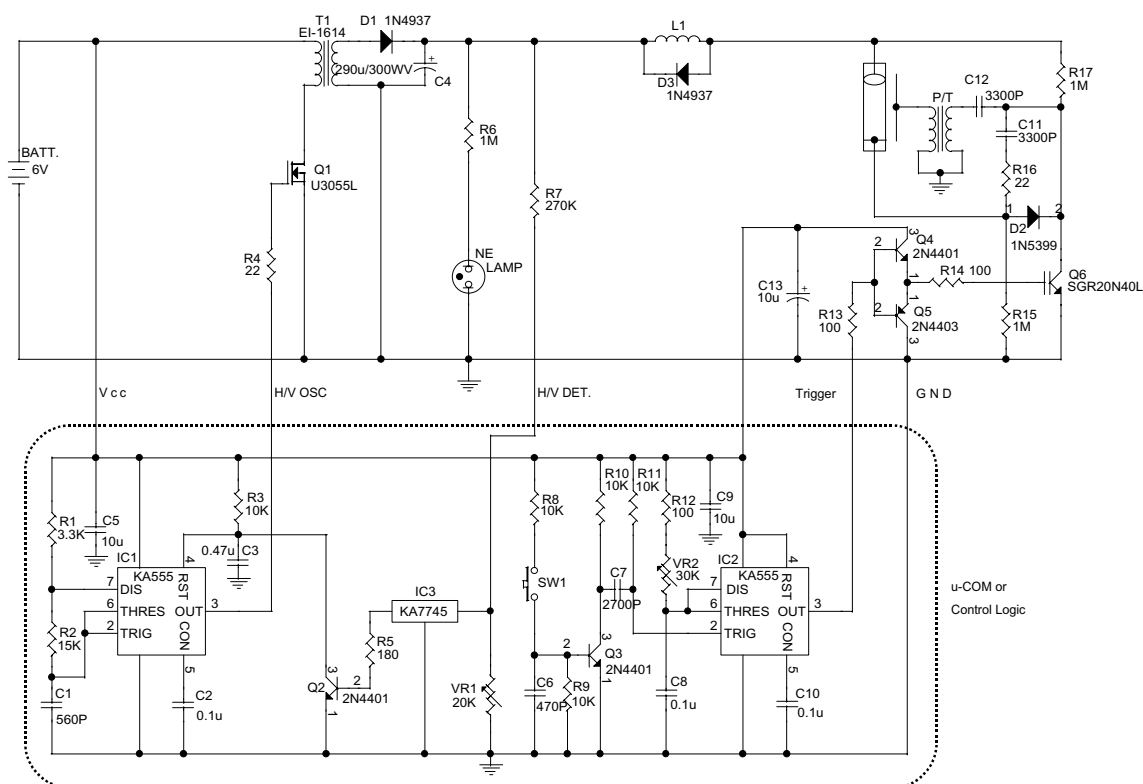

**Figure 6: Strobe System Function Waveforms**

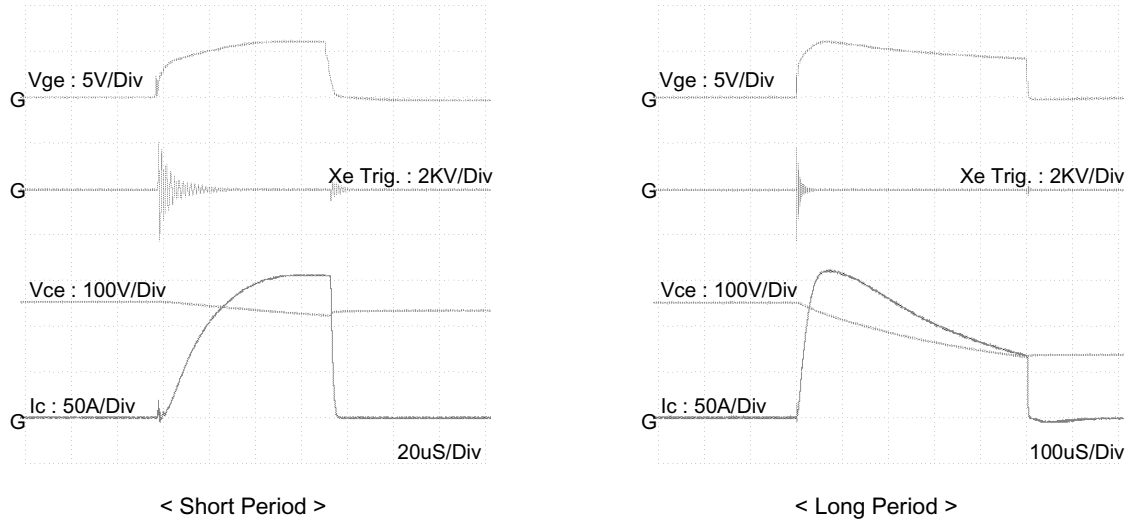


#### 4) System Block Explanation

##### 1. DC/DC Converter Block

The DC/DC Converter Block takes the 6 V power and produces the HV needed for lamp lumination. It functions as a 100 Khz Forward Type Switching Regulator using a KA555.

**Figure 7: DC/DC Converter Block**

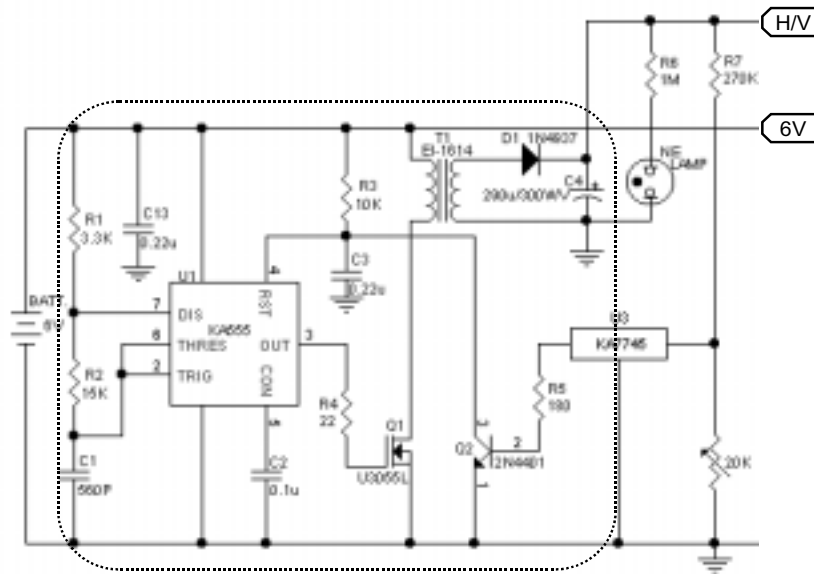

Rev E, December 2002

The switching frequency and duty are set by the resistance (R1) between KA555's  $V_{CC}$  and Pin 7, the resistance (R2) at connecting pins 7, 6 and 2, and the capacitor (C1) value.

$f = 100 \text{ KHz}$  (@  $T = 10 \mu\text{S}$ )

$T_{on} = 4.5 \mu\text{S}$ ,  $T_{off} = 5.5 \mu\text{S}$

$T_{off} = 0.67 * R2 * C1$  (Here,  $C1 = 560 \text{ pF}$ )

$Rb = T_{off} / (0.67 * C1)$

$= 5.5 \mu\text{S} / (0.67 * 560 \text{ pF}) = 14658\Omega$  (here the standard resistance is  $15 \text{ k}\Omega$ )

$T_{on} = 0.67 * (R1+R2) * C1$

Duty =  $R2 / (R1+2R2) = 0.45$

$= 15\text{k}\Omega / (R1 + (2 * 15 \text{ k}\Omega))$

$R1 = 3.3 \text{ k}\Omega$

KA555's pin 4 (Reset) receives a signal detected in Block 2's HV, and is able to stop KA555. The Reset block (4) changes to Reset mode between 0.4 and 1.0 V (Min/Max), so you must be careful with the voltage level.

## 2. Design of the Boosting Transformer

The transformer's size is EI-1614. A smaller size is better for making the product smaller and lighter. In this design the most commonly available smallest size is used.



First calculate the 1st order coil  $N_p$ .

Then calculate the 2nd order coil  $N_s$ .

$N_p = (V_{in} * t_{on} / B * A_e) * 10^8$

$= (6\text{V} * 4.5\mu\text{S} / 2200\text{G} * 0.1982) * 10^8$


$= 6.19 \text{ T}$  (approximately 6T)

(The battery's voltage failure and a discharge of up to 5.2 V are factored into the design)

$N_s = (V_s * N_p) / V_{in(min)}$

$= (300\text{V} * 6\text{T}) / 5.2\text{V} = 346.15\text{T}$  (approximately 346T)

### Figure 8: H/V Detection Block

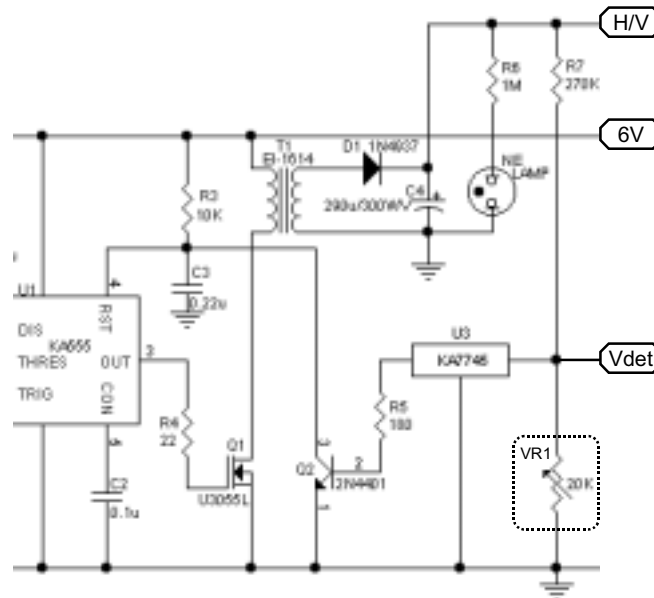


When Vdet. block's voltage is below 4.5 V, the KA7745's output is low, and when it is over 4.5 the output is high. The high output activates Q2, lowers KA555's pin 4's level, and stops the DC/DC converter by putting it in a Reset Condition. The voltage is detected by dividing HV using resistance, and HV is set to the required value (200-300 V) using VR1. The NE-lamp shows the condition of the energy stored in the capacitor.

#### 4. Strobe Light Duration Control Block for Lighting Duration

This block outputs a trigger signal using the Time IC KA555, activating it to mono-stable mode, and by receiving an external trigger signal. The output pulse (duration of luminescence) is adjusted using the  $R_t$  and  $C_t$  connected to pins 6 and 7 on the KA555.

**Figure 9: Strobe Light Duration Control Block for Lighting Duration**

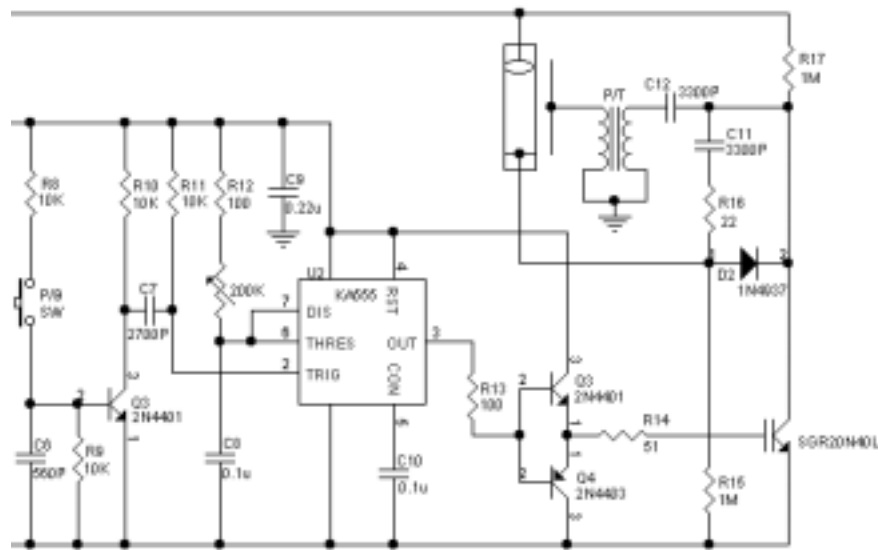

In mono-stable mode,  $T = 1.1 \cdot R_t \cdot C_t$ . Hence, the Xenon-lamp's luminescence duration is maintained between the following:

$$T(\min) = 1.1 \cdot 100\Omega \cdot 0.1\mu\text{F} = 11\mu\text{s}$$

$$T(\max) = 1.1 \cdot 200.1\text{k}\Omega \cdot 0.1\mu\text{F} = 22\text{ms}$$

The KA555 has a source/sink capability of upto 200 mA, and directly activates the IGBT (SGR20N40L). But in this system a Buffer Block is added using TR just in case there is a shortage of gate drive capability.

- SGR15N40L and SGR20N40L are logic level IGBTs, and can be operated directly from many different types of logic ICs, as long as the control logic part's output current is above 100 mA.



## 5. Strobe Unit

This unit is composed of the Xenon lamp and the trigger transformer. The trigger pulse ionizes the gas mixture within the Xenon lamp. It also receives a signal (about 250-300 V) when the S/W element IGBT is on, and produces an HV trigger signal of about 4 to 5 kV by using the pulse transformer's turn number and ratio. The pulse transformer can be designed as follows.

$$V(\text{trig}) = \frac{N_2}{N_1} \times V_{in}$$



The \$V\_{in}\$ is about 250 to 300 V, and the voltage is determined by the turn ratio. If the trigger pulse voltage is low, the Xenon lamp does not luminate or does so irregularly. If it is too high, the Xenon lamp's electrode may discharge or damage other parts nearby. The trigger pulse output wire should be as close as possible to the Xenon lamp trigger's electrode.

## 5). Notes for Constructing a Strobe System

- The energy capacity of a small strobe lamp is below 20 W-S, and it should not be exceeded. (refer to the of the Xenon tube specifications)
- The P/T (trigger transformer) should be designed for an output of about 4 to 5 kV. If it is too low, the Xenon lamp does not luminate or does so irregularly . If it is too high, the Xenon lamp's electrode discharges and may damage neighboring parts.
- The wire between the energy storing capacitor and the Xenon lamp should be as short and thick as possible.


## Comparison of Fairchild Strobe IGBTs with Competitors'

Table 2: FAIRCHILD Strobe IGBT Line-up & Competitor

Gate Drive Volt. [V]	Rating		FAIRCHILD	Mitsubishi	Toshiba	Remark
	V	A				
4.5	400	130	SGR15N40L	CT20ASJ-8	GT5G103	D-PAK
			SGU15N40L			I-PAK
	150	150	SGR20N40L	CT25ASJ-8	GT8G103	D-PAK
			SGU20N40L		GT8G121	I-PAK


## Package Dimensions

Figure 10: D-PAK

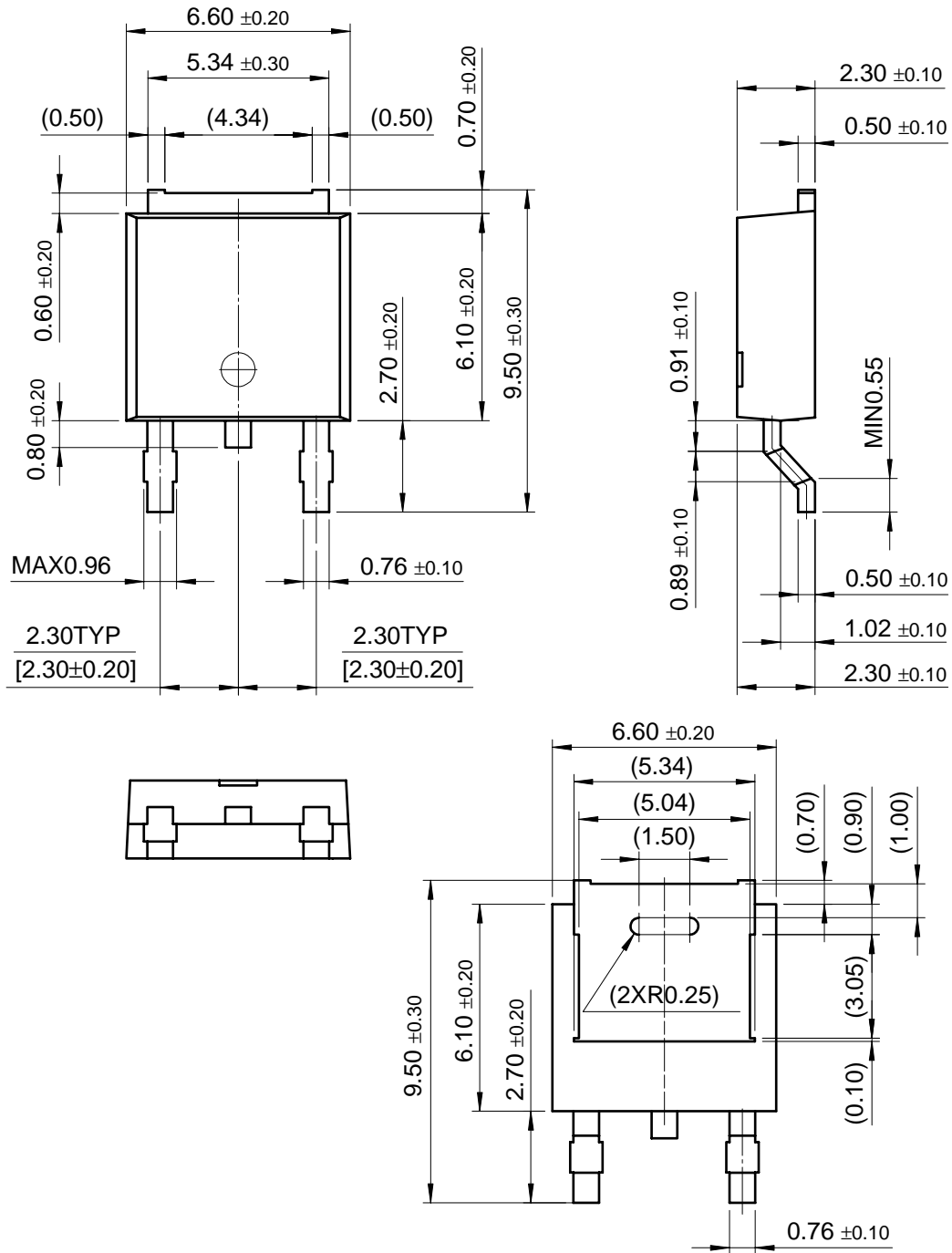

Rev E, December 2002

**Figure 11: I-PAK**

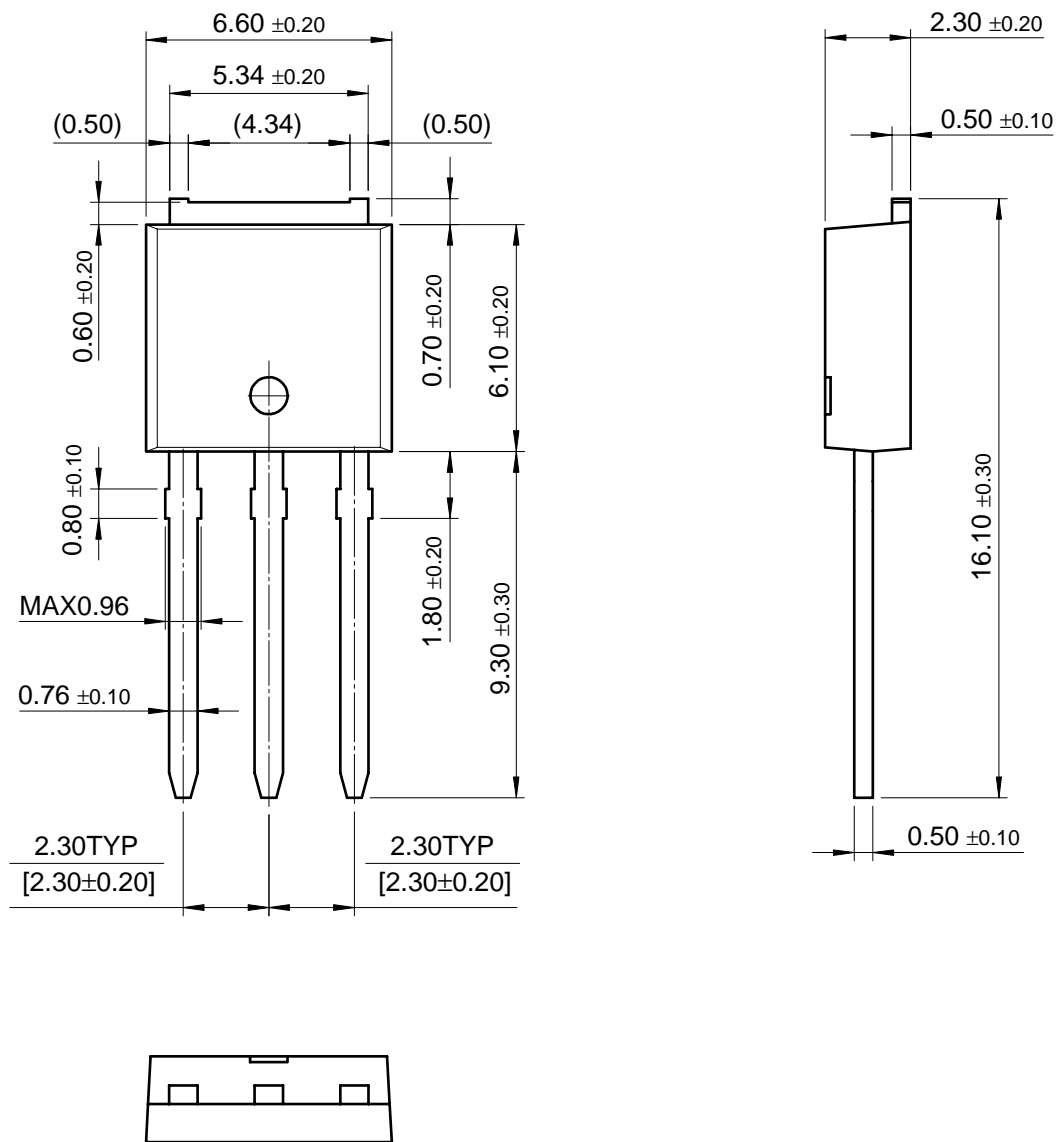

Rev E, December 2002

## TRADEMARKS

The following are registered and unregistered trademarks Fairchild Semiconductor owns or is authorized to use and is not intended to be an exhaustive list of all such trademarks.

ACEx™	FACT™	ImpliedDisconnect™	PACMAN™	SPM™
ActiveArray™	FACT Quiet series™	ISOPLANAR™	POP™	Stealth™
Bottomless™	FAST®	LittleFET™	Power247™	SuperSOT™-3
CoolFET™	FASTR™	MicroFET™	PowerTrench®	SuperSOT™-6
CROSSVOLT™	FRFET™	MicroPak™	QFET™	SuperSOT™-8
DOME™	GlobalOptoisolator™	MICROWIRE™	QST™	SyncFET™
EcoSPARK™	GTO™	MSX™	QT Optoelectronics™	TinyLogic™
E <sup>2</sup> CMOS™	HiSeC™	MSXPro™	Quiet Series™	TruTranslation™
EnSigna™	I <sup>2</sup> C™	OCX™	RapidConfigure™	UHC™
Across the board. Around the world.™		OCXPro™	RapidConnect™	UltraFET®
The Power Franchise™		OPTOLOGIC®	SILENT SWITCHER®	VCX™
Programmable Active Droop™		OPTOPLANAR™	SMART START™	

## DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

## LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF FAIRCHILD SEMICONDUCTOR INTERNATIONAL.

As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

## PRODUCT STATUS DEFINITIONS

### Definition of Terms

Datasheet Identification	Product Status	Definition
Advance Information	Formative or In Design	This datasheet contains the design specifications for product development. Specifications may change in any manner without notice.
Preliminary	First Production	This datasheet contains preliminary data, and supplementary data will be published at a later date. Fairchild Semiconductor reserves the right to make changes at any time without notice in order to improve design.
No Identification Needed	Full Production	This datasheet contains final specifications. Fairchild Semiconductor reserves the right to make changes at any time without notice in order to improve design.
Obsolete	Not In Production	This datasheet contains specifications on a product that has been discontinued by Fairchild semiconductor. The datasheet is printed for reference information only.