

AN-9759 GreenBridge[™] to Replace Conventional Diode Bridge in Power Over Ethernet Applications

Summary

A Power Device (PD) in a Power over Ethernet (PoE) application requires a bridge circuit to regulate the polarity of the input power when the Power Source Equipment (PSE) supplying power to the PD is equipped with an Uninterruptible Power Supply (UPS). The simple diode bridge design has been used without major concerns at low cost. However, as PD gets hungrier for power, the conduction loss of the diode bridge caused by the forward-voltage drop becomes one of the main issues to be solved efficiently. Fairchild's GreenBridge[™] solution reduces power losses in the bridge circuit and leads to an efficient and cost-effective PoE system. In this application note, the GreenBridge drive circuit is examined and test results with a typical diode bridge are presented.

Power Over Ethernet

Power over Ethernet (PoE) introduces a new facet to Ethernet networking, delivering DC power through a CAT5 network cable. Figure 1 shows a typical PoE system. It is convenient to install PDs; such as IP telephones, wireless LAN access points, and security cameras; without any wall power lines because the CAT5 cable delivers data as well as power required by those PDs. In addition, the PoE system is energy efficient because the PSE communicates to the PD first and provides regulated power PD for demands. The power management block of PD must be designed carefully to operate efficiently at limited input power from the PSE.



Figure 1. Typical PoE System

The IEEE802.3af/3at standard defines the power class for PD as described in Table 1.

PD Class	Maximum PD Power
0	0.5 to 13W
1	0.5 to 3.84W
2	3.84 to 6.49W
3	6.49 to 13W
4	13 to 25W

Table 1. IEEE802.3af/3at PoE Classification

GreenBridge™

To improve the conduction loss and efficiency of the conventional diode bridge, Fairchild Semiconductor integrates dual P-channel and dual N-channel MOSFETs in a compact and thermally enhanced package. Table 2 the GreenBridge FDMQ8203 electrical parameters.



Figure 2. GreenBridge™ Configuration and Pin Map

Table 2. GreenBridge[™] FDMQ8203 Parameters

Part No.	MOSFET	BV _{DSS}	R _{DS(ON)} [mΩ]	Q _g [n C]	
		(•)	Max.	Тур.	
ESMOSOO	Q1, Q4	100	110	2.9	50
F31VIQ0203	Q2, Q3	-80	190	13	50

APPLICATION NOTE

AN-9759

The package plays a critical role in power supply performance. The thermally enhanced MLP 4.5x5mm package shown in Figure 3 is able to increase power density and save PCB space.



Figure 3. MLP 4.5x5mm Package

A bridge circuit in the PD regulates power polarity from the PSE so all power loss is conduction loss. Replacing the diode bridge with the GreenBridgeTM device, shown in Figure 4, reduces conduction loss to improve PD efficiency.

As current flow is turned on, the current flows through the corresponding P- or N-channel MOSFET of the GreenBridge device. As a result, the $R_{DS(on)}$ of GreenBridge solution reduces the conduction loss when compared to a diode bridge from the forward voltage, V_F .



Figure 5. Conventional Diode Bridge in PD

GreenBridge power loss is calculated by:

 $=I^{2} x R_{DS(ON)} - Pch + I^{2} x R_{DS(ON)} - Nch$ (1)

Diode bridge power loss is calculated by:

$$=2 \times V_F \times I \tag{2}$$

The self-driven gate circuit for GreenBridge FDMQ8203 is configured as illustrated in Figure 6, which consists of transistors, diodes, Zener diodes, and resistors.



Figure 6. Self-Driven Gate Drive Circuits for GreenBridge

Figure 6 shows the current flow from SW+ to SW-. Q1 and Q4 in the GreenBridge device turn on, while Q2 and Q3 are off. Red lines indicate the power flow path and green lines express the bias current of the self-driven gate circuit. Zener diodes limit the gate-to-source voltage of the GreenBridge device, not to exceed BV_{GSS} . The gate voltage of Q1 and Q4 are defined as:

$$V_{gs_Q1} = Zener Voltage_10V + V_{F_D}$$
 (3)

$$V_{gs_Q4}$$
 = Zener Voltage_10V + V_{F_D} (4)



When PD is plugged into the PSE, the PSE recognizes the presence of the PD by checking the current through a $25k\Omega$ $(\pm 1.3k\Omega)$ resistor on the PD. It is the resistance detection process of the PoE standard. The PSE provides two consecutive voltages, V1=2.7V and V2=10.1V, shown in Figure 7, to the PD for the resistance detection mode and records measured current values, I1 and I2 by V1 and V2, respectively. The computed $\Delta V / \Delta I$ by the PSE ensures the presence of a PD and the PSE moves on to identify the PD power class. During this step, the GreenBridge device should not compromise the resistance detection procedure by bypassing the current through the body diode. The recommended gate drive circuit in Figure 6 helps the GreenBridge device stay turned off and bypasses the current via body diode at 2.7V and 10.1V from the PSE. Without the safe gate drive circuit, the GreenBridge device can turn on at the 10.1V input given by the PSE during the resistance detection because the MOSFETs of the GreenBridge device have a 4V maximum threshold voltage. This could cause resistance detection to fail.

AN-9759

Below is how the PSE calculates in this scenario:

- I1 = $(2.7V 1.4V) / 25K\Omega = 0.052mA$ GreenBridge device turns off at 2.7V. Current flows through body diode, causing body diode voltage drop (2 x 0.7V).
- I2=10.1V/25KΩ =0.404mA
- GreenBridge device turns on at 10.1V. Current flows through the channel of GreenBridge device.
- Measured $\Delta V / \Delta I = (10.1V-2.7V) / (0.404mA 0.052mA) = 21.02K\Omega$
- The measured $\Delta V/$ ΔI does not meet the $25k\Omega$ $(\pm 1.3k\Omega)$ standard.

After the resistance detection process, the input voltage from the PSE increases more than twice (Zener voltage _10V+ V_{F_D}) and the GreenBridge device turns on completely. The current begins flowing through the conduction channel of the GreenBridge device.



Figure 8. Signal at Initial Operation

GreenBridge[™] Performance

The 25W PD power block is designed as listed in Table 3 for the test between the GreenBridge FDMQ8203 and the conventional Schottky diode bridge with S210 (100V / 2A).

Table 3.	PD Power	Design	Specification
----------	----------	--------	---------------

PoE Class	Class 4	
IEEE Standard	IEEE802.3at	
DCDC Topology	Flyback	
Input Voltage	36V ~ 57V	
Output Voltage	5V	
Maximum Output Current	5A	
Output Power	25W	
Switching Frequency	250KHz	

At 25W maximum output power and 36V minimum input voltage, the estimated input current is 0.7A through the GreenBridge solution or diode bridge. Based on equations [1] and [2], the computed power loss gap between the GreenBridge solution and the diode bridge is 0.83W. ($R_{DS(on)}$ _Pch = 190m Ω , $R_{DS(on)}$ _Nch=110m Ω , typical diode $V_F = 0.7V$):

- GreenBridge power loss is calculated by: = 0.7A x 0.7A x 110mΩ+0.7A x 0.7Ax190mΩ = 0.147W
- Diode bridge power loss is calculated by: = $0.7V \ge 0.7A \ge 2 = 0.98W$

Figure 9 shows that the GreenBridgeTM FDMQ8203 improves the efficiency by 2.41% and saves the total power loss by 0.82W compared to diode bridge at 25W maximum output power and 36V minimum input voltage conditions.



Figure 9. Efficiency & Power Loss Comparison of GreenBridge™ Solution and Diode Bridge at V_{IN}=36V, V_{OUT}=5V, f_{SW}=250KHz, T_A=25°C



GreenBridge™ Top View, Temperature: 45°C Figure 10. Thermal Performance Comparison of Green Bridge™ Solution and Diode Bridge at V_{IN}=36V, V_{OUT}=5V, f_{Sw}=250KHz, T_A=25°C



Diode Bridge Top View, Temperature: 53.4°C Figure 11. Thermal Performance Comparison of GreenBridge™ Solution and Diode Bridge at V_{IN}=36V, V_{OUT}=5V, f_{SW}=250KHz, T_A=25°C

3

APPLICATION NOTE

AN-9759

Figure 10 and Figure 11 show the thermal performance of the GreenBridge solution at lower temperature because of the lower thermal impedance of the MLP 4x4.5mm package and lower power loss even thought the GreenBridge package size is 45% smaller.

Table 4.	Comparison	Summary
----------	------------	---------

	GreenBridge™	Diode Bridge
Power Loss	Good (0.82W ↓)	Bad
Thermal	Good (8.4°C ↓)	Bad
Solution Size	Good (45% ↓) 48.74mm ² (FDMQ8203: 22.5mm ² Gate circuits: 26.24mm ²)	Bad 88.48mm ²
Complexity	Complex	Simple

Finally, Table 4 shows that the GreenBridgeTM solution saves power loss and PCB area.

Authors

SungJin Kuen - LV Applications Engineer

Edgar Kim - LV Applications Engineer

References

[1] GreenBridge[™] Evaluation Kit for Power over Ethernet 25W Flyback DCDC User Guide

Related Resources

<u>FDMQ8203</u> — GreenBridgeTM Series of High-Efficiency Bridge Rectifiers Dual N-Channel and Dual P-Channel PowerTrench® MOSFET N-Channel: 100 V, 6 A, 110m Ω P-Channel: -80V, -6 A, 190m Ω

DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION, OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION. As used herein:

- Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
- A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

In a PoE application, the PSE delivers the limited power defined by PoE power class. The PD should be designed carefully to maximize the efficiency. Using Fairchild's GreenBridgeTM solution instead of the conventional diode bridge reduces power loss and increases the power density. This results in lower PD class rating and saved PCB area. An efficient and cost-effective PoE system can be achieved with Fairchild's innovative GreenBridge solution.