

Fairchild Reference Design

The following user guide supports the demonstration kit for the FL7732. It should be used in conjunction with the FL7732 datasheet as well as Fairchild's application notes and technical support team. Please visit Fairchild's website at www.fairchildsemi.com

Application	Fairchild Device	Input Voltage Range	Output Power	Output Voltage (Rated Current)
LED Bulb	FL7732	90-265V _{AC}	8.4W	60V(0.14A)

Key Features

- Cost effective solution without input bulk capacitor and feedback circuitry
- Power Factor Correction
- Accurate constant-current (CC) Control
- Linear frequency control for better efficiency and easy design
- Constant current regulation vs output voltage change (35~75V) : $<\pm 2.19\%$
- Constant current regulation vs line voltage change (90~265Vac) : $<\pm 3.27\%$
- Output open & short circuit protection with auto restart
- System efficiency up to 90.93%
- PF and THD at nominal voltages: PF(>0.9), THD($<25\%$)

1. Schematics

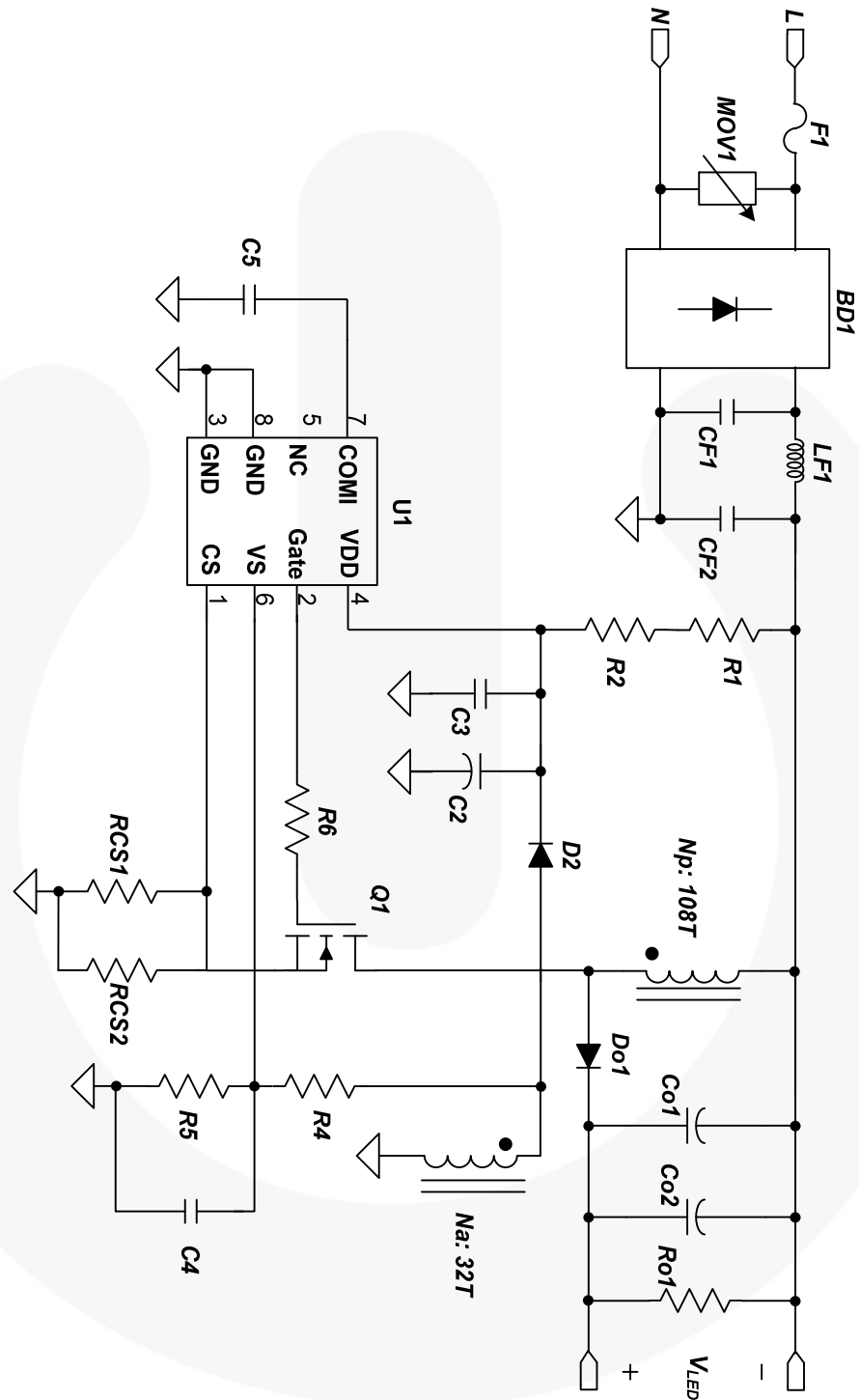


Figure 1. Schematic

2. Bill of Material

Item No.	Part Reference	Value	Qty	Description	Manufacturer
1	BD1	MB6S	1	Bridge Diode	Fairchild
2	CF1, CF2	MPE400V683K	2	683/400V, Film Capacitor	Sungho
3	Co1, Co2	KMG 47uF/100V	1	47u/100V, Electrolytic Capacitor	Samyoung
4	C2	KMG 10uF/35V	1	10uF/35V, Electrolytic Capacitor	Samyoung
5	C3	C0805C104K3RACTU	1	104/25V, SMD Capacitor 2012	Kemet
6	C4	C0805C200M3GACTU	1	200/25V, SMD Capacitor 2012	Kemet
7	C5	C1206C105K3PACTU	1	105/25V, SMD Capacitor 2012	Kemet
8	D2	1N4003	1	1A/200V, Diode	Fairchild
9	Do1	ES3J	1	3A/600V, Fast Rectifier	Fairchild
10	F1	SS-5-1A	1	1A/250V, Fuse	Bussmann
11	LF1	R06153KT00	1	10mH, 8Ø Filter inductor	Bosung
12	MOV1	SVC 471D07	1	Varistor	Samwha
13	C2	KMG 10uF/35V	1	10uF/35V, Electrolytic Capacitor	Samyoung
14	Rcs1	RC0805JR-071R2L	1	1.2Ω, SMD Resistor 2012	Yageo
15	Rcs2	RC0805JR-071R8L	1	1.8Ω, SMD Resistor 2012	Yageo
16	Ro1	RC1206JR-07220KL	1	220kΩ, SMD Resistor 3216	Yageo
17	R1,R2	RC1206JR-07100KL	2	100kΩ, SMD Resistor 3216	Yageo
18	R4	RC0805JR-07150KL	1	150kΩ, SMD Resistor 2012	Yageo
19	R5	RC1206JR-0724KL	1	24kΩ, SMD Resistor 3216	Yageo
20	R6	RC0805JR-0710RL	1	10Ω, SMD Resistor 2012	Yageo
21	T1	RM6	1	Transformer	TDK
22	Q1	FQU5N60C	1	2.8A/600V, MOSFET	Fairchild
23	U1	FL7732	1	Main Controller	Fairchild

3. Transformer

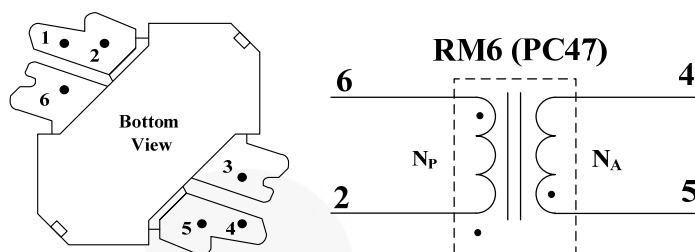


Figure 2. Transformer Bobbin Structure

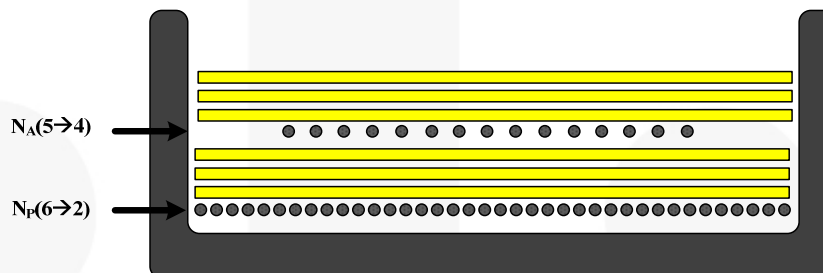


Figure 3. Configuration and Transformer Winding Structure

Table 1. Winding specifications.

No	Winding	Pin(S → F)	Wire	Turns	Winding Method
1	Np	6 → 2	0.25Ø	108Ts	Solenoid Winding
2	Insulation : Polyester Tape t = 0.025mm, 3Layers				
3	Na	5 → 4	0.13Ø	32Ts	Solenoid Winding
4	Insulation : Polyester Tape t = 0.025mm, 3Layers				

Table 2. Electrical Characteristics.

	Pin	Spec.	Remark
Inductance	6– 2	1.4mH ± 10%	60kHz, 1V
Leakage		15 uH	60kHz, 1V Short all output pins

4. Performance

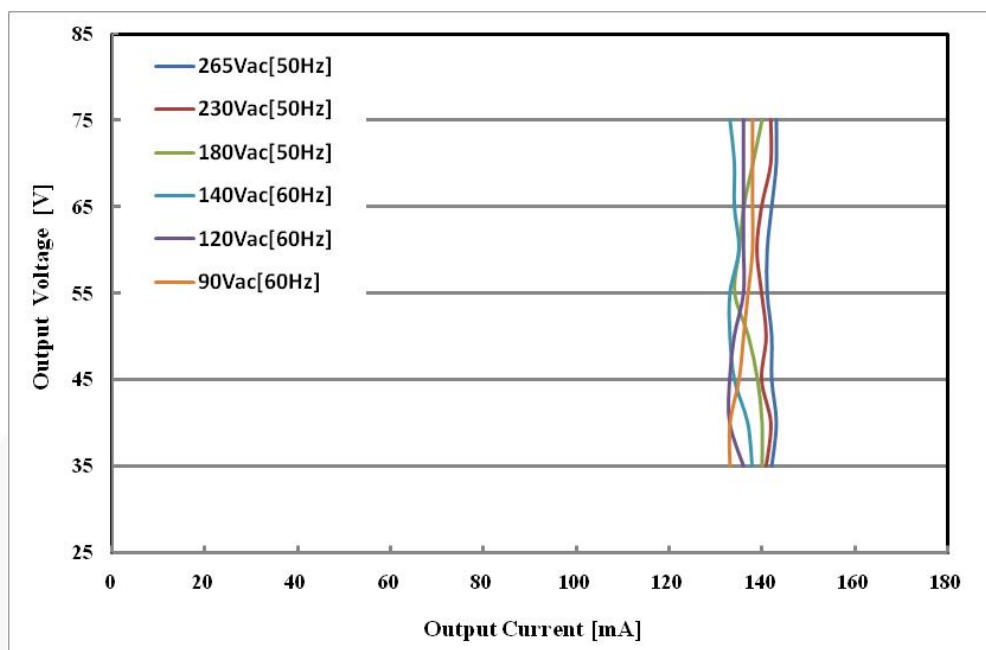


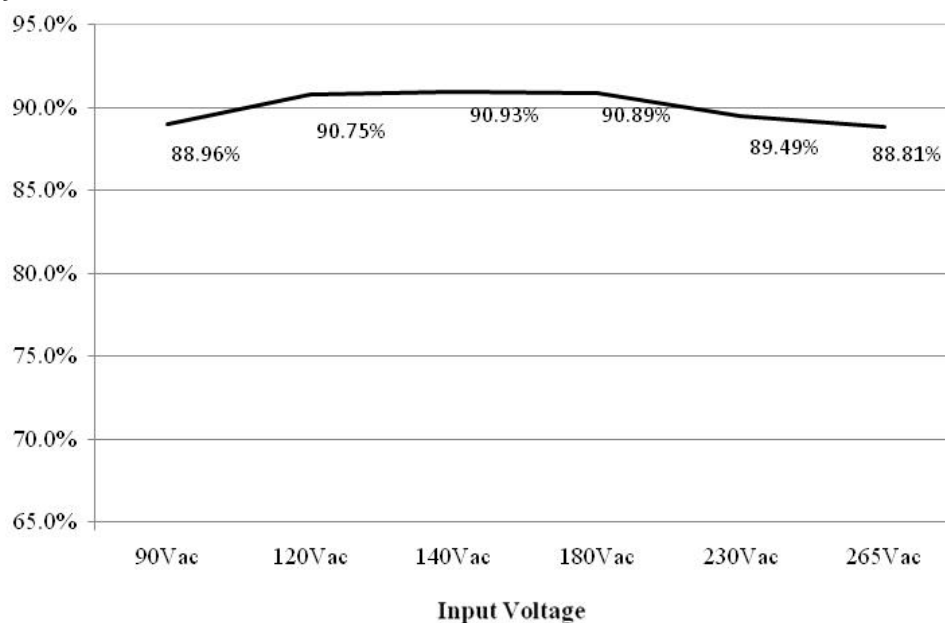
Figure 4. Constant Current Regulation – Measured by LED Load

Table 3. Constant Current Regulation by Output Voltage Change (35~75V)

Input Voltage	Min Current	Max Current	Tolerance
90V _{AC} [60Hz]	133mA	138mA	± 1.85%
120V _{AC} [60Hz]	133mA	136mA	± 1.12%
140V _{AC} [60Hz]	133mA	138mA	± 1.85%
180V _{AC} [50Hz]	134mA	140mA	± 2.19%
230V _{AC} [50Hz]	139mA	142mA	± 1.07%
265V _{AC} [50Hz]	141mA	143mA	± 0.70%

Table 4. Constant Current Regulation by Line Voltage Change (90~265Vac)

Output Voltage	90Vac [60Hz]	120Vac [60Hz]	140Vac [60Hz]	180Vac [50Hz]	220Vac [50Hz]	265Vac [50Hz]	Tolerance
65V	138 mA	136 mA	134 mA	138 mA	142 mA	143 mA	± 2.90%
60V	138 mA	136 mA	135 mA	136 mA	140 mA	142 mA	± 2.17%
55V	138 mA	136 mA	133 mA	135 mA	139 mA	141 mA	± 2.92%
50V	137 mA	136 mA	133 mA	134 mA	140 mA	141 mA	± 3.27%

Efficiency

Figure 5. System Efficiency
Table 5. System Efficiency

Input Voltage	Input Power	Output Current	Output Voltage	Output Power	Efficiency
90Vac [60Hz]	8.93 W	135 mA	58.84 V	7.94 W	88.96 %
120Vac [60Hz]	8.58 W	132 mA	58.78 V	7.79 W	90.75 %
140Vac [60Hz]	8.46 W	131 mA	58.72 V	7.69 W	90.93 %
180Vac [50Hz]	8.76 W	135 mA	58.81 V	7.96 W	90.89 %
230Vac [50Hz]	9.08 W	138 mA	58.91 V	8.13 W	89.49 %
265Vac [50Hz]	9.24 W	139 mA	58.95 V	8.21 W	88.81 %

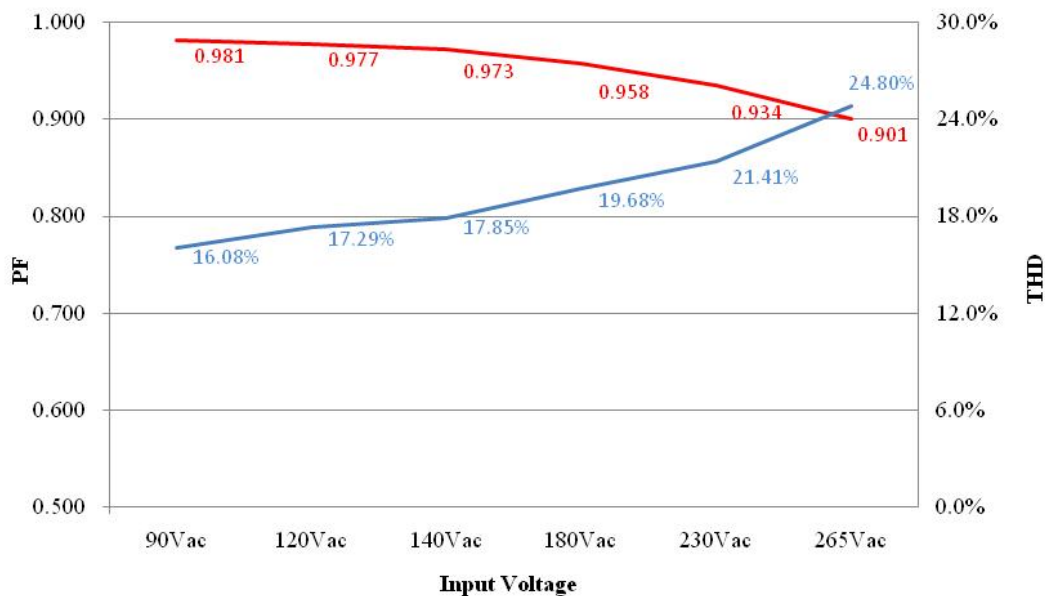


Figure 6. PF & THD

Table 6. PF & THD

Input Voltage	Output Current	Output Voltage	Power Factor	THD
90Vac [60Hz]	135 mA	58.84 V	0.981	16.08%
120Vac [60Hz]	132 mA	58.78 V	0.977	17.29%
140Vac [60Hz]	131 mA	58.72 V	0.973	17.85%
180Vac [50Hz]	135 mA	58.81 V	0.958	19.68%
230Vac [50Hz]	138 mA	58.91 V	0.934	21.41%
265Vac [50Hz]	139 mA	58.95 V	0.901	24.80%

5. Related Resources

[Datasheet link FL7732](#)

<http://www.fairchildsemi.com/referencedesign/>

Reference Design Disclaimer

Fairchild Semiconductor Corporation ("Fairchild") provides these reference design services as a benefit to our customers. Fairchild has made a good faith attempt to build for the specifications provided or needed by the customer. Fairchild provides this product "as is" and without "recourse" and MAKES NO WARRANTY, EXPRESSED, IMPLIED OR OTHERWISE, INCLUDING ANY WARRANTY OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE.

Customer agrees to do its own testing of any Fairchild reference designs in order to ensure design meets the customer needs. Neither Fairchild nor Customer shall be liable for incidental or consequential damages, including but not limited to, the cost of labor, requalifications, rework charges, delay, lost profits, or loss of goodwill arising out of the sale, installation or use of any Fairchild product.

Subject to the limitations herein, Fairchild will defend any suit or proceeding brought against Customer if it is based on a claim that any product furnished hereunder constitutes an infringement of any intellectual property rights. Fairchild must be notified promptly in writing and given full and complete authority, information and assistance (at Fairchild's expense) for defense of the suit. Fairchild will pay damages and costs therein awarded against Customer but shall not be responsible for any compromise made without its consent. In no event shall Fairchild's liability for all damages and costs (including the costs of the defense by Fairchild) exceed the contractual value of the products or services that are the subject of the lawsuit. In providing such defense, or in the event that such product is held to constitute infringement and the use of the product is enjoined, Fairchild, in its discretion, shall procure the right to continue using such product, or modify it so that it becomes noninfringing, or remove it and grant Customer a credit for the depreciated value thereof. Fairchild's indemnity does not extend to claims of infringement arising from Fairchild's compliance with Customer's design, specifications and/or instructions, or the use of any product in combination with other products or in connection with a manufacturing or other process. The foregoing remedy is exclusive and constitutes Fairchild's sole obligation for any claim of intellectual property infringement and Fairchild makes no warranty that products sold hereunder will not infringe any intellectual property rights.

All solutions, designs, schematics, drawings, boards or other information provided by Fairchild to Customer are confidential and provided for Customer's own use. Customer may not share any Fairchild materials with other semiconductor suppliers.