

## Fairchild Reference Design

The following reference design supports inclusion of FLS0116 in design of LED illumination. It should be used in conjunction with the FLS0116 datasheet as well as Fairchild's application notes and technical support team. Please visit Fairchild's website at <http://www.fairchildsemi.com>.

Application	Fairchild Device	Input Voltage Range	Rated Output Power	Output Voltage (Rated Current)
LED Bulb	FLS0116M	90-264V <sub>AC</sub>	2.7W	28V/(97mA)

### Key Features

- Built-in MOSFET (1A/550V)
- Digital implemented active PFC function
- Built in HV supplying circuit: Self biasing
- AOCV function with auto restart mode
- Cycle-by-cycle current limit
- Current sense pin open protection
- Low operating current: 0.85mA (typ.)
- Under-Voltage Lockout with 5V Hysteresis.
- Programmable Oscillation Frequency
- Programmable LED Current
- Analog Dimming Function
- Soft-Start Function
- Precise Internal Reference:  $\pm 3\%$

# 1. Schematics

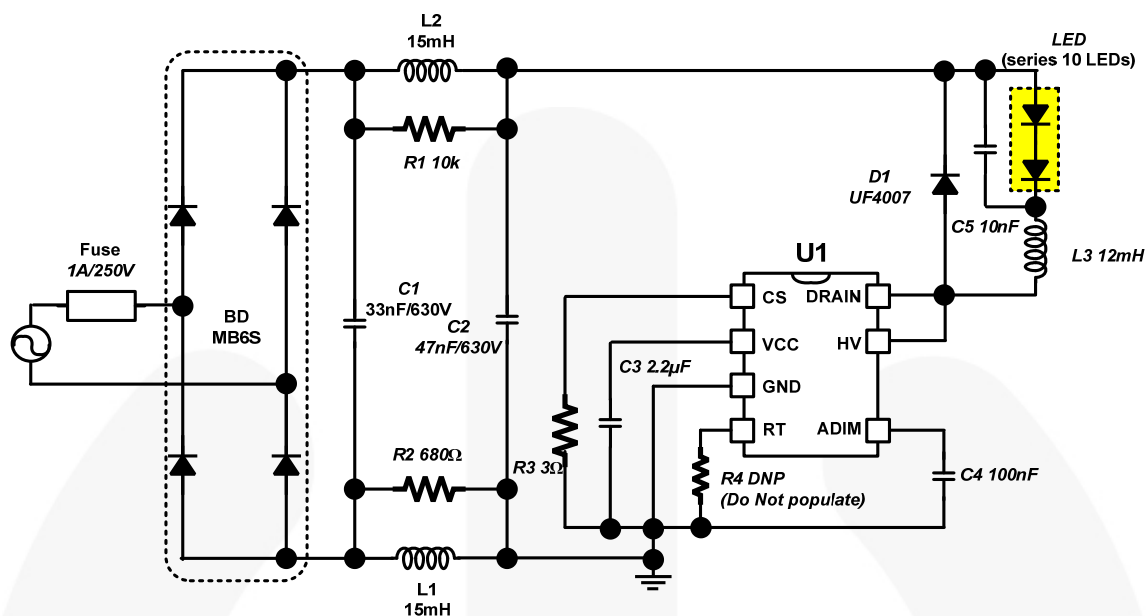


Figure 1. Schematic

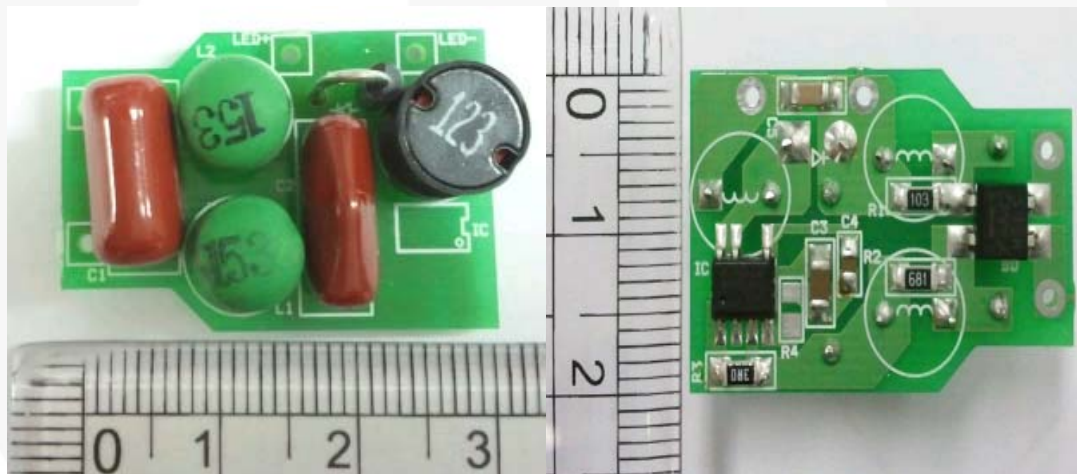


Figure 2. A Photograph of the evaluation board

## 2. Bill of Materials

**Table 1. BOM Table**

Item No.	Part Reference	Part Number	Qty.	Description	Manufacturer
1	U1	FLS0116M	1	Controller	Fairchild Semiconductor
2	BD	MB6S	1	0.5A/600V, Bridge Diode	Fairchild Semiconductor
3	C1	MPE 630V333K	1	333/630V <sub>AC</sub> , Film Capacitor	Sungho
4	C2	MPE 630V473K	1	473/630V <sub>AC</sub> , Film Capacitor	Sungho
5	C3	C1206C225K3PACTU	1	225/25V SMD Capacitor 3216	Kemet
6	C4	C0805C104K3RACTU	1	104/25V SMD Capacitor 2012	Kemet
7	C5	C1206C103KDRACTU	1	103/630V SMD Capacitor 3216	Kemet
8	D1	UF4007	1	1A/1000V, Ultra-Fast Recovery	Fairchild Semiconductor
9	L1,L2	R06153KT00	2	15mH, Filter Inductor	Bosung
10	L3	RFB0810-123L	1	12mH, Inductor	Coil Craft
11	R1	RC1206JR-07103RL	1	10k $\Omega$ , SMD Resistor 3216	Yageo
12	R2	RC1206JR-07680RL	1	680 $\Omega$ , SMD Resistor 3216	Yageo
13	R3	RC1206JR-073RL	1	3 $\Omega$ , SMD Resistor 3216	Yageo
-	R4	-	0	Open	

### 3. Performance

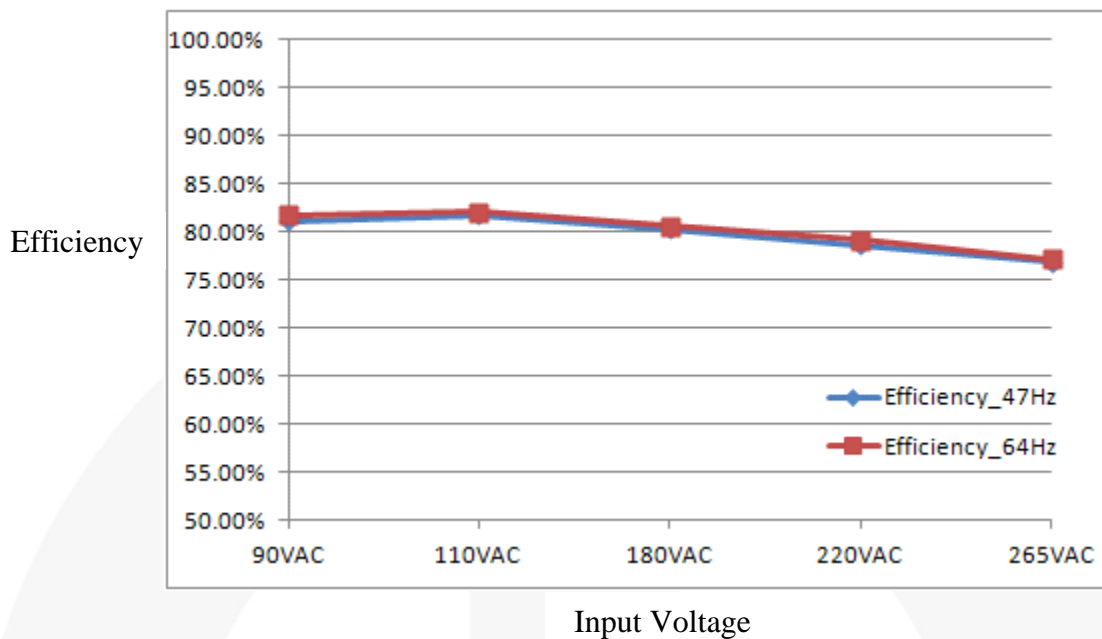


Figure 3. Efficiency Curve

Table 2. Efficiency test result

Input Voltage (V <sub>AC</sub> )	Frequency (Hz)	Efficiency (%)
90V <sub>AC</sub>	47Hz	81.12
	64Hz	81.73
110V <sub>AC</sub>	47Hz	81.72
	64Hz	82.08
180V <sub>AC</sub>	47Hz	80.26
	64Hz	82.57
220V <sub>AC</sub>	47Hz	78.64
	64Hz	79.12
265V <sub>AC</sub>	47Hz	76.84
	64Hz	77.14


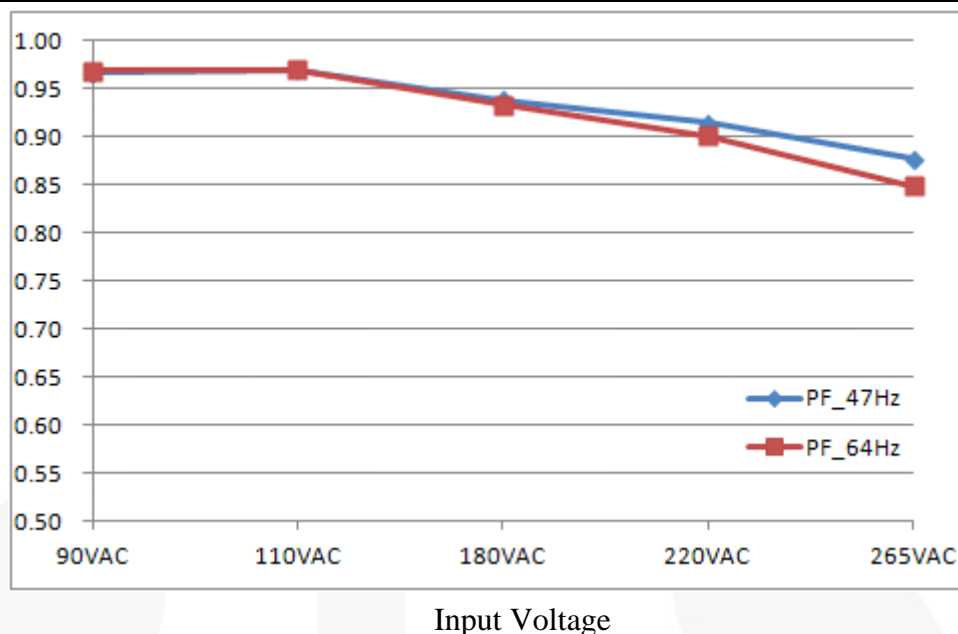


Figure 4. Power Factor Performance

Table 3. PF Test Result

Input Voltage		Power Factor
90V <sub>AC</sub>	47Hz	0.97
	64Hz	0.97
110V <sub>AC</sub>	47Hz	0.97
	64Hz	0.97
180V <sub>AC</sub>	47Hz	0.94
	64Hz	0.94
220V <sub>AC</sub>	47Hz	0.91
	64Hz	0.90
265V <sub>AC</sub>	47Hz	0.88
	64Hz	0.85

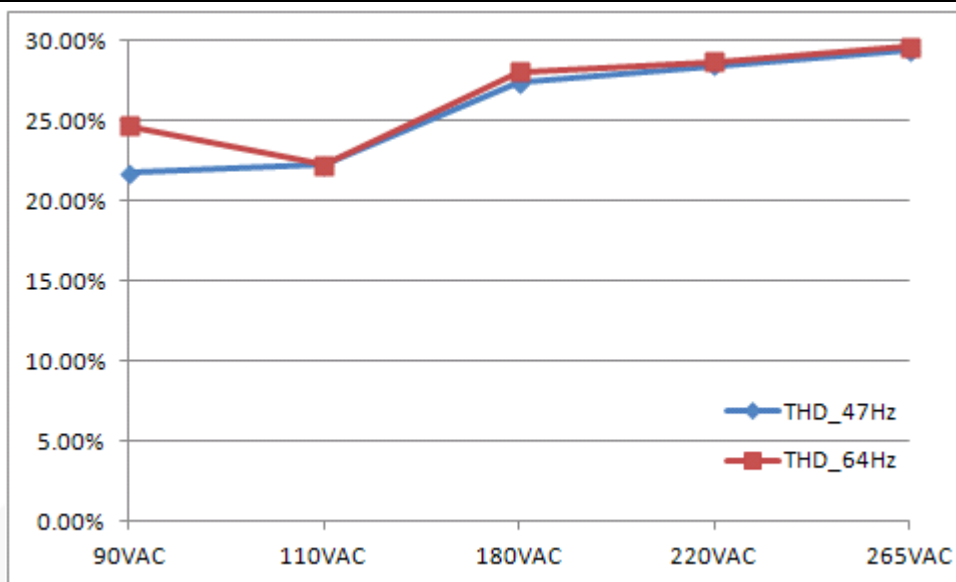

Input Voltage  
Figure 5. THD Performance

Table 4. THD Test Result

Input Voltage (V <sub>AC</sub> )	Frequency (Hz)	THD (%)
90V <sub>AC</sub>	47Hz	21.74
	64Hz	24.70
110V <sub>AC</sub>	47Hz	22.24
	64Hz	22.23
180V <sub>AC</sub>	47Hz	27.38
	64Hz	28.09
220V <sub>AC</sub>	47Hz	28.46
	64Hz	28.72
265V <sub>AC</sub>	47Hz	29.37
	64Hz	29.64

## 4. Related Resources

[Datasheet link FLS0116](#)

<http://www.fairchildsemi.com/referencedesign/>

---

### Reference Design Disclaimer

Fairchild Semiconductor Corporation ("Fairchild") provides these reference design services as a benefit to our customers. Fairchild has made a good faith attempt to build for the specifications provided or needed by the customer. Fairchild provides this product "as is" and without "recourse" and MAKES NO WARRANTY, EXPRESSED, IMPLIED OR OTHERWISE, INCLUDING ANY WARRANTY OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE.

Customer agrees to do its own testing of any Fairchild reference designs in order to ensure design meets the customer needs. Neither Fairchild nor Customer shall be liable for incidental or consequential damages, including but not limited to, the cost of labor, requalifications, rework charges, delay, lost profits, or loss of goodwill arising out of the sale, installation or use of any Fairchild product.

Subject to the limitations herein, Fairchild will defend any suit or proceeding brought against Customer if it is based on a claim that any product furnished hereunder constitutes an infringement of any intellectual property rights. Fairchild must be notified promptly in writing and given full and complete authority, information and assistance (at Fairchild's expense) for defense of the suit. Fairchild will pay damages and costs therein awarded against Customer but shall not be responsible for any compromise made without its consent. In no event shall Fairchild's liability for all damages and costs (including the costs of the defense by Fairchild) exceed the contractual value of the products or services that are the subject of the lawsuit. In providing such defense, or in the event that such product is held to constitute infringement and the use of the product is enjoined, Fairchild, in its discretion, shall procure the right to continue using such product, or modify it so that it becomes noninfringing, or remove it and grant Customer a credit for the depreciated value thereof. Fairchild's indemnity does not extend to claims of infringement arising from Fairchild's compliance with Customer's design, specifications and/or instructions, or the use of any product in combination with other products or in connection with a manufacturing or other process. The foregoing remedy is exclusive and constitutes Fairchild's sole obligation for any claim of intellectual property infringement and Fairchild makes no warranty that products sold hereunder will not infringe any intellectual property rights.

All solutions, designs, schematics, drawings, boards or other information provided by Fairchild to Customer are confidential and provided for Customer's own use. Customer may not share any Fairchild materials with other semiconductor suppliers.