

Fairchild Reference Design

The following user guide supports the demonstration kit for the FLS3217M. It should be used in conjunction with the FLS3217M datasheet as well as Fairchild's application notes and technical support team. Please visit Fairchild's website at www.fairchildsemi.com

Application	Fairchild Device	Input Voltage Range	Output Power	Output Voltage (Rated Current)
LED Bulb	FLS3217M	90-265V _{AC}	3.5W	35V(0.1A)

Key Features

- Cost effective solution without input bulk capacitor and feedback circuitry
- Power Factor Correction
- Accurate constant-current (CC) Control
- Linear frequency control for better efficiency and easy design
- Constant current regulation vs output voltage change (19.5~36.3V) : $< \pm 2.22\%$
- Constant current regulation vs line voltage change (90~265Vac) : $< \pm 2.17\%$
- Output open & short circuit protection with auto restart
- System efficiency up to 87.4%
- PF and THD: PF(> 0.9), THD($< 30\%$)

1. Schematics

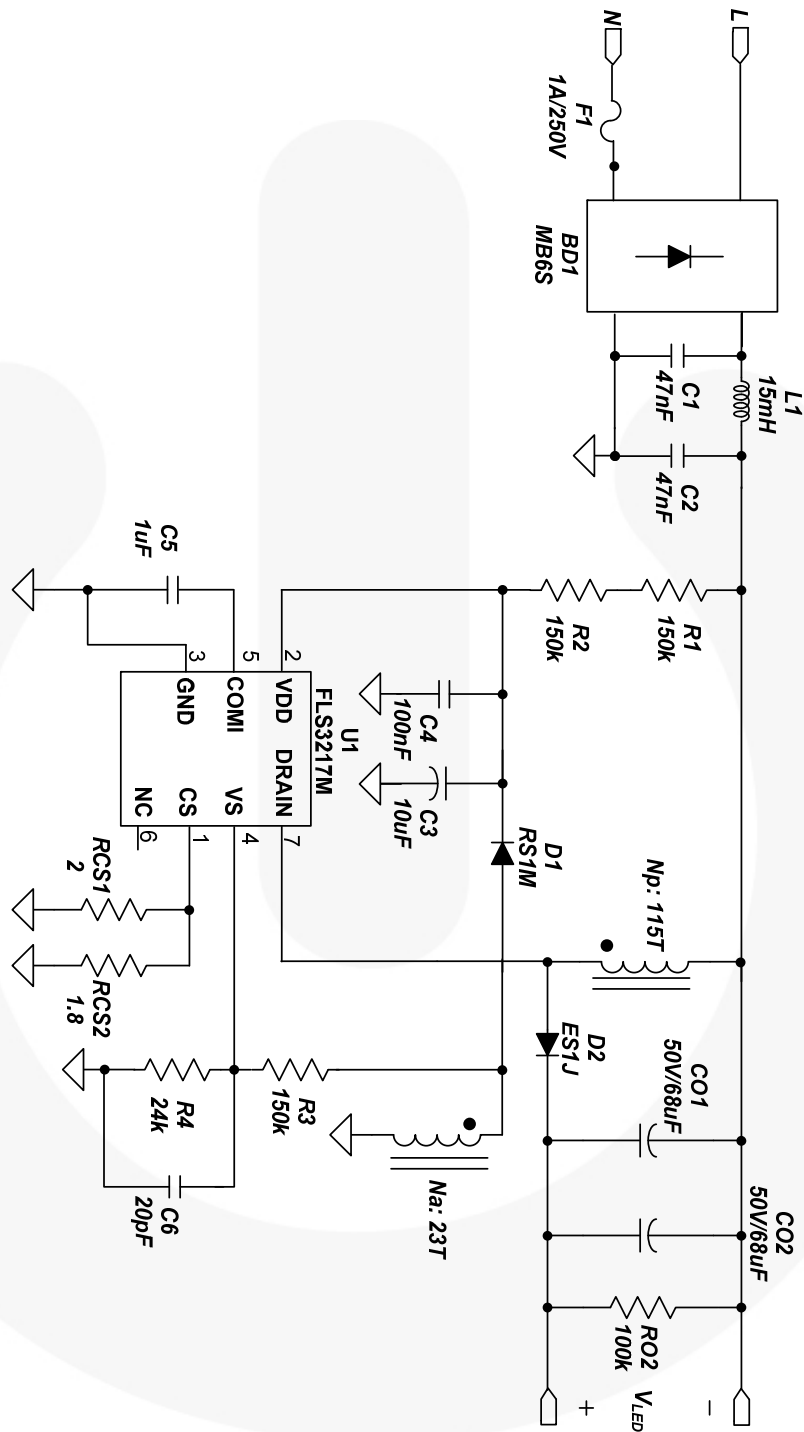


Figure 1. Schematic

2. Bill of Material

Item No.	Part Reference	Part number	Qty	Description	Manufacturer
1	BD1	MB6S	1	Bridge Diode	Fairchild
2	CO1,CO2	KMG 68uF/50V	2	68u/50V, Electrolytic Capacitor	Samyoung
3	C1, C2	B32560J473K	2	473/400V, Film Capacitor	EPCOS
4	C3	KMG 10uF/35V	1	10u/35V, Electrolytic Capacitor	Samyoung
5	C4	C0805C104K3RACTU	1	104/25V, SMD Capacitor 2012	Kemet
6	C5	C1206C105K3PACTU	1	105/25V, SMD Capacitor 2012	Kemet
7	C6	C0805C200M3GACTU	1	20/25V, SMD Capacitor 2012	Kemet
8	D1	RS1M	1	1A/1000V, Diode	Fairchild
9	D2	ES1J	1	1A/600V, Fast Rectifier	Fairchild
10	F1	SS-5-1A	1	1A/250V, Fuse	Bussmann
11	L1	R06153KT00	1	15mH, 8Ø Filter inductor	Bosung
12	R1,R2	RC1206JR-07150KL	2	150kΩ, SMD Resistor 3216	Yageo
13	RCS1	RC0805JR-072RL	2	2.0Ω, SMD Resistor 2012	Yageo
14	RCS2	RC0805JR-071R8L	2	1.8Ω, SMD Resistor 2012	Yageo
15	RO1	RC1206JR-07150KL	1	150kΩ, SMD Resistor 3216	Yageo
16	R3	RC0805JR-07150KL	1	150kΩ, SMD Resistor 2012	Yageo
17	R4	RC0805JR-0724KL	1	24kΩ, SMD Resistor 2012	Yageo
18	T1	RM6	1	Transformer	TDK
19	U1	FLS3217M	1	Main Driver	Fairchild

3. Transformer

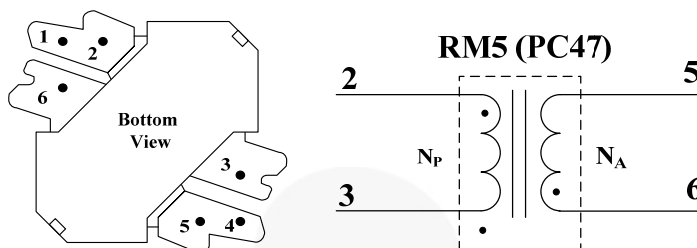


Figure 2. Transformer Bobbin Structure and Pin Configuration

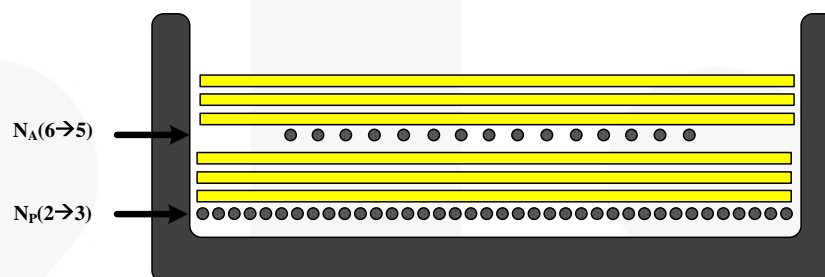


Figure 3. Transformer Winding Structure

Table 1. Winding specifications.

No	Winding	Pin(S → F)	Wire	Turns	Winding Method
1	Np	2 → 3	0.15Ø	160Ts	Solenoid Winding
2	Insulation : Polyester Tape t = 0.025mm, 3Layers				
3	Na	6 → 5	0.10Ø	74Ts	Solenoid Winding
4	Insulation : Polyester Tape t = 0.025mm, 3Layers				

Table 2. Electrical Characteristics.

	Pin	Spec.	Remark
Inductance	2 - 3	2.0mH ± 10%	60kHz, 1V
Leakage	2 - 3	30 uH	60kHz, 1V Short all output pins

4. Performance

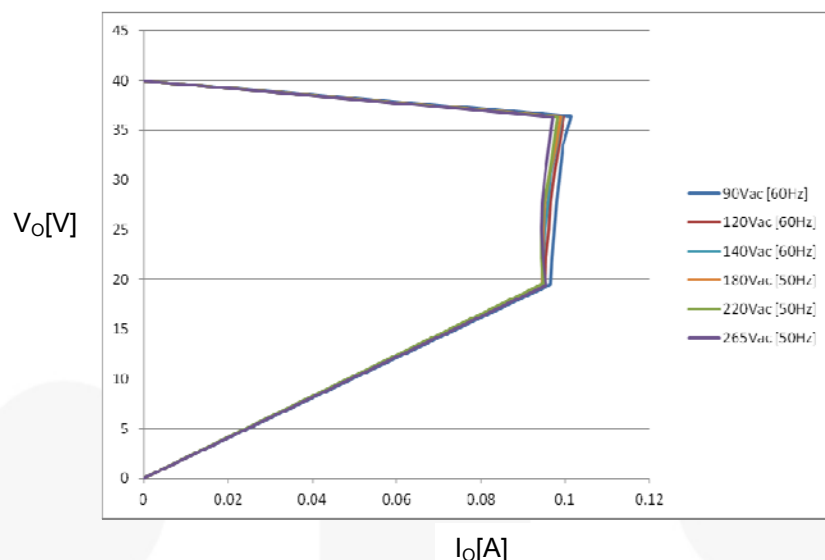


Figure 4. Constant Current Regulation – Measured by 7-LED to 13-LED

Table 3. Constant Current Regulation by Output Voltage Change

Input Voltage	Min Current[A]	Max Current[A]	Tolerance
90V _{AC} [60Hz]	0.097	0.102	±2.41%
120V _{AC} [60Hz]	0.095	0.100	±2.16%
140V _{AC} [60Hz]	0.095	0.099	±2.22%
180V _{AC} [50Hz]	0.095	0.099	±2.18%
220V _{AC} [50Hz]	0.094	0.098	±1.89%
265V _{AC} [50Hz]	0.094	0.097	±1.44%

Table 4. Constant Current Regulation by Line Voltage Change (90~265Vac)

Output Voltage	90V _{AC} [60Hz]	120V _{AC} [60Hz]	140V _{AC} [60Hz]	180V _{AC} [50Hz]	220V _{AC} [50Hz]	265V _{AC} [50Hz]	Tolerance
36.3V	0.102A	0.100A	0.099A	0.099A	0.098A	0.097A	±2.17%
33.5V	0.100A	0.099A	0.098A	0.098A	0.097A	0.096A	±1.66%
30.7V	0.099A	0.098A	0.097A	0.096A	0.096A	0.095A	±1.77%

Efficiency

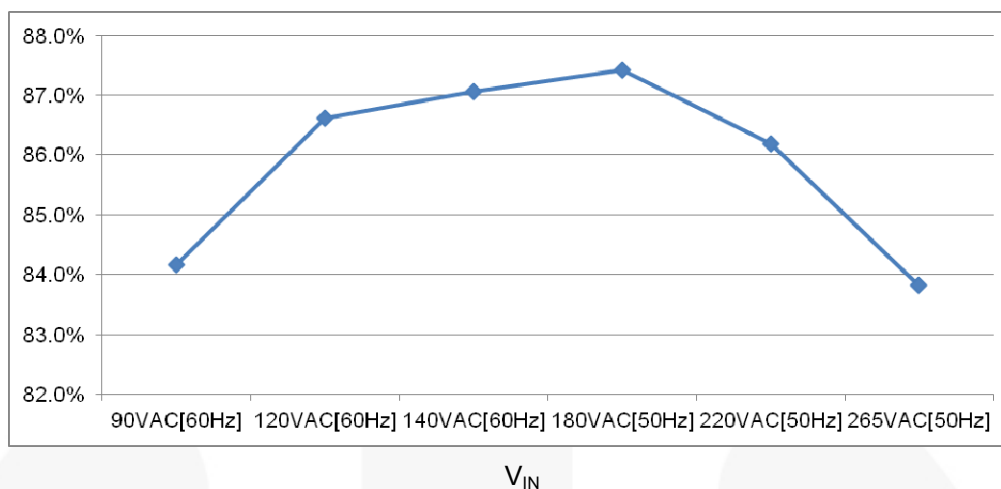


Figure 5. System Efficiency (13-LED)

Table 5. System Efficiency

Input Voltage	Input Power[W]	Output Current[A]	Output Voltage[V]	Output Power[W]	Efficiency
90V _{AC} [60Hz]	4.340	0.101	36.24	3.653	84.16%
120V _{AC} [60Hz]	4.180	0.100	36.2	3.621	86.62%
140V _{AC} [60Hz]	4.140	0.100	36.18	3.604	87.06%
180V _{AC} [50Hz]	4.140	0.100	36.17	3.619	87.42%
220V _{AC} [50Hz]	4.160	0.099	36.15	3.585	86.19%
265V _{AC} [50Hz]	4.210	0.098	36.12	3.529	83.81%

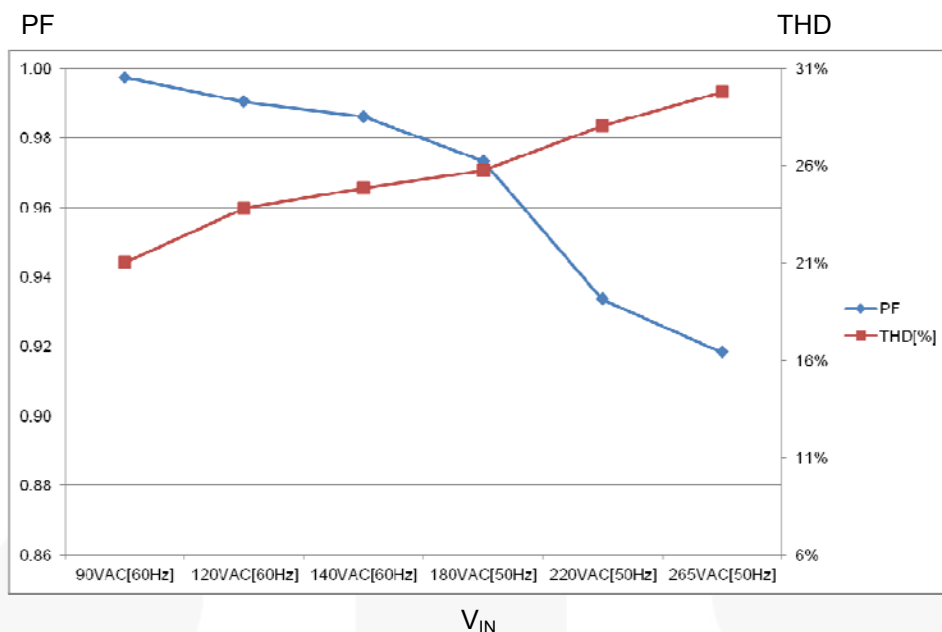


Figure 6. PF & THD

Table 6. PF & THD

Input Voltage	PF	THD
90V _{AC} [60Hz]	0.997	21.03%
120V _{AC} [60Hz]	0.990	23.81%
140V _{AC} [60Hz]	0.986	24.85%
180V _{AC} [50Hz]	0.973	25.74%
220V _{AC} [50Hz]	0.934	28.05%
265V _{AC} [50Hz]	0.918	29.78%

5. Related Resources

[Datasheet link FLS3217](#)

<http://www.fairchildsemi.com/referencedesign/>

Reference Design Disclaimer

Fairchild Semiconductor Corporation ("Fairchild") provides these reference design services as a benefit to our customers. Fairchild has made a good faith attempt to build for the specifications provided or needed by the customer. Fairchild provides this product "as is" and without "recourse" and MAKES NO WARRANTY, EXPRESSED, IMPLIED OR OTHERWISE, INCLUDING ANY WARRANTY OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE.

Customer agrees to do its own testing of any Fairchild reference designs in order to ensure design meets the customer needs. Neither Fairchild nor Customer shall be liable for incidental or consequential damages, including but not limited to, the cost of labor, requalifications, rework charges, delay, lost profits, or loss of goodwill arising out of the sale, installation or use of any Fairchild product.

Subject to the limitations herein, Fairchild will defend any suit or proceeding brought against Customer if it is based on a claim that any product furnished hereunder constitutes an infringement of any intellectual property rights. Fairchild must be notified promptly in writing and given full and complete authority, information and assistance (at Fairchild's expense) for defense of the suit. Fairchild will pay damages and costs therein awarded against Customer but shall not be responsible for any compromise made without its consent. In no event shall Fairchild's liability for all damages and costs (including the costs of the defense by Fairchild) exceed the contractual value of the products or services that are the subject of the lawsuit. In providing such defense, or in the event that such product is held to constitute infringement and the use of the product is enjoined, Fairchild, in its discretion, shall procure the right to continue using such product, or modify it so that it becomes noninfringing, or remove it and grant Customer a credit for the depreciated value thereof. Fairchild's indemnity does not extend to claims of infringement arising from Fairchild's compliance with Customer's design, specifications and/or instructions, or the use of any product in combination with other products or in connection with a manufacturing or other process. The foregoing remedy is exclusive and constitutes Fairchild's sole obligation for any claim of intellectual property infringement and Fairchild makes no warranty that products sold hereunder will not infringe any intellectual property rights.

All solutions, designs, schematics, drawings, boards or other information provided by Fairchild to Customer are confidential and provided for Customer's own use. Customer may not share any Fairchild materials with other semiconductor suppliers.