Reference Design RD-325

Fairchild PFM Controller FAN7621 - 384W Design

Featured Device	Application	Input Voltage Range	Output Voltage (Rated Current)	Rated Output Power	Topology
FAN7621 FEP16FT/FET16FTA FEP16BT/FET16BTA FCPF11N60	PDP TV	340~400V_{DC}	210V /1.4A 60V / 1.5A	384W	LLC Resonant Half-Bridge Converter

Key Features

FAN7621

- Variable Frequency Control with 50% Duty Cycle for Half-Bridge Resonant Converter Topology
- High Efficiency through Zero Voltage Switching (ZVS)
- Fixed Dead Time: 350ns
- Up to 300kHz Operating Frequency
- Pulse Skipping for Frequency Limit (Programmable) at Light-Load Condition
- Remote On/Off Control Using Control Pin
- Various Protection Functions: Over-Voltage Protection (OVP), Overload Protection (OLP), Over-Current Protection (OCP), Abnormal Over-Current Protection (AOCP), and Internal Thermal Shutdown (TSD)

FEP16FT

- 300V/16A Ultra-Fast Recovery Rectifier, Common Cathode
- Low Forward-Voltage Drop: 1.3V at T_A = 25°C, 8A

FEP16FTA

- 300V/16A Ultra-Fast Recovery Rectifier, Common Anode
- Low Forward-Voltage Drop: 1.3V at T_A = 25°C, 8A

FEP16BT

- 100V/16A Ultra-Fast Recovery Rectifier, Common Cathode
- Low Forward-Voltage Drop: 0.95V at T_A = 25°C, 8A

FEP16BTA

- 100V/16A Ultra-Fast Recovery Rectifier, Common Anode
- Low Forward-Voltage Drop: 0.95V at T_A = 25°C, 8A

FCPF11N60

- 600V/11A SuperFET™
- Low Gate Charge: Typical: 40°C
- Low $R_{DS,ON}$: 0.38Ω Max. at T_A 25°C

1. Schematic

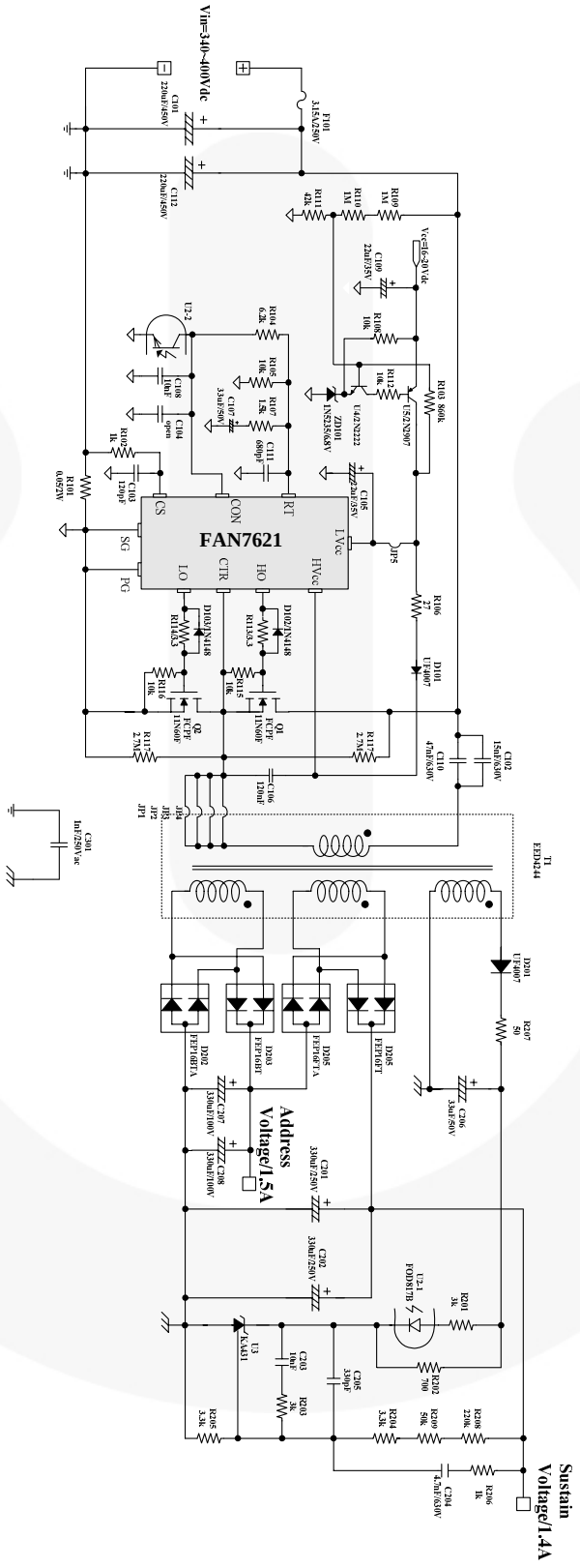

Figure 1. Schematic

2. Transformer

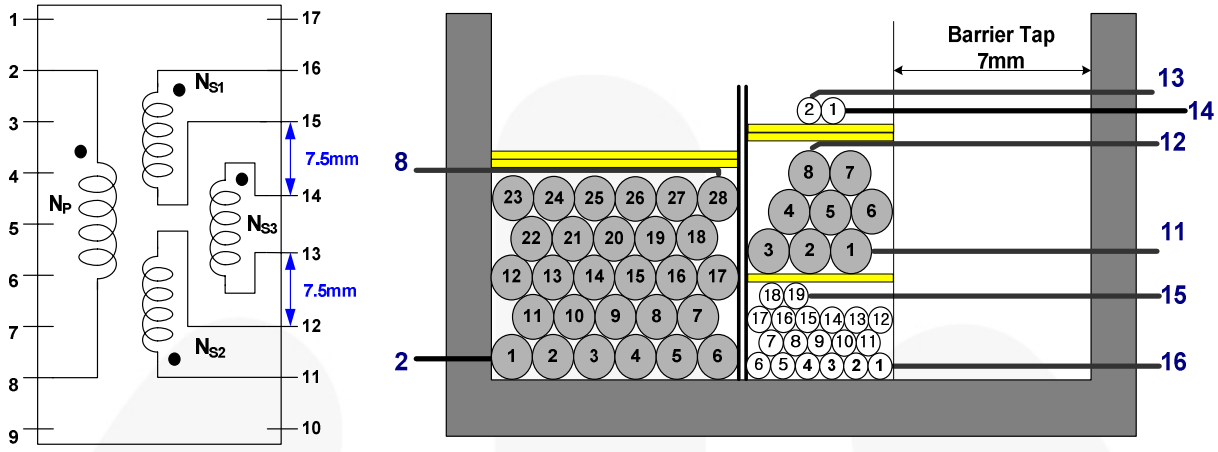

Figure 2. Transformer Schematic Diagram

2.1. Winding Specification

	Pin (S → F)	Wire	Turns	Winding Method
N_{S3}	14 → 13	0.12φ×25 (Litz Wire)	2	Solenoid
N_{s2}	11 → 12	0.08φ×126 (Litz Wire)	8	Solenoid
N_{s1}	16 → 15	0.12φ×25 (Litz Wire)	19	Solenoid
N_P	2 → 8	0.08φ×126 (Litz Wire)	28	Solenoid

Core: EED4244D (Ae=158 mm2)
Bobbin: EED4244D (Horizontal, 17Pins, 9/8 pins at each side)

2.2. Electrical Characteristics

	Pin	Specification	Remark
Primary-Side Inductance (L_p)	2 – 8	240μH ± 5%	100kHz, 1V, All Other Pins Open
Primary-Side Effective Leakage Inductance (L_r)	2 – 8	40μH ± 10%	All Other Pins Shorted

3. Typical Characteristics

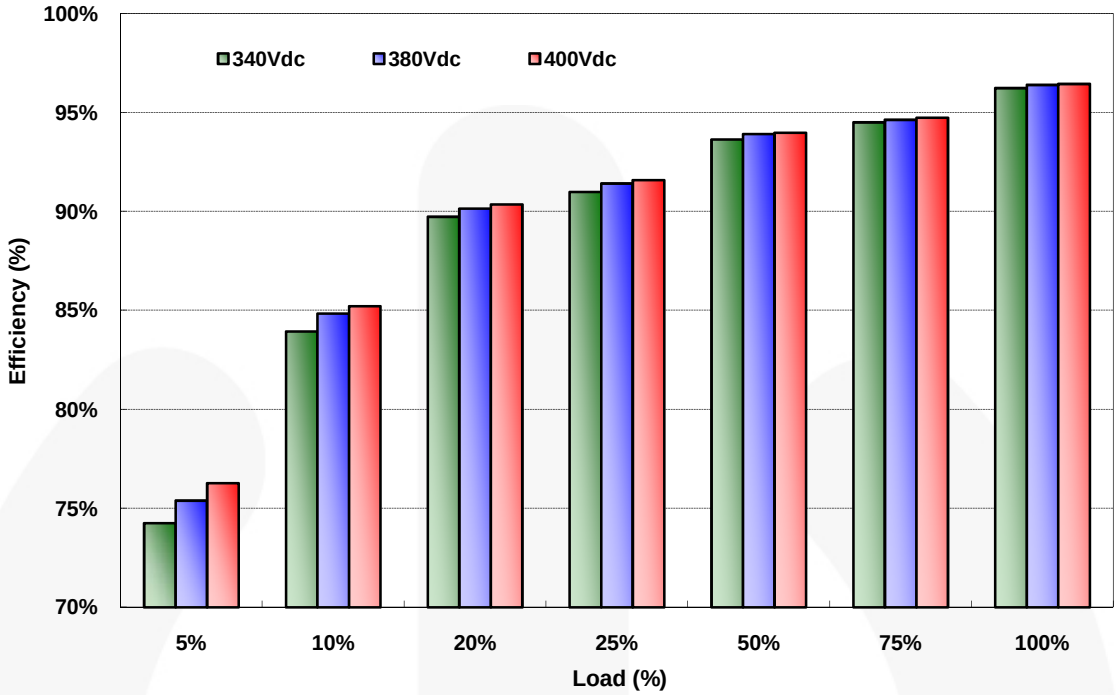

Figure 3. Efficiency

4. Related Resources

FAN7621 — PFM Controller for Half-Bridge Resonant Converters

AN-4151 — Half-Bridge LLC Replacement Converter Design Using FSFR-Series Fairchild Power Switches (FPS™)

Reference Design Disclaimer

Fairchild Semiconductor Corporation ("Fairchild") provides these reference design services as a benefit to our customers. Fairchild has made a good faith attempt to build for the specifications provided or needed by the customer. Fairchild provides this product "as is" and without "recourse" and MAKES NO WARRANTY, EXPRESSED, IMPLIED OR OTHERWISE, INCLUDING ANY WARRANTY OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE.

Customer agrees to do its own testing of any Fairchild reference designs in order to ensure design meets the customer needs. Neither Fairchild nor Customer shall be liable for incidental or consequential damages, including but not limited to, the cost of labor, re-qualifications, rework charges, delay, lost profits, or loss of goodwill arising out of the sale, installation or use of any Fairchild product.

Subject to the limitations herein, Fairchild will defend any suit or proceeding brought against Customer if it is based on a claim that any product furnished hereunder constitutes an infringement of any intellectual property rights. Fairchild must be notified promptly in writing and given full and complete authority, information and assistance (at Fairchild's expense) for defense of the suit. Fairchild will pay damages and costs therein awarded against Customer but shall not be responsible for any compromise made without its consent. In no event shall Fairchild's liability for all damages and costs (including the costs of the defense by Fairchild) exceed the contractual value of the products or services that are the subject of the lawsuit. In providing such defense, or in the event that such product is held to constitute infringement and the use of the product is enjoined, Fairchild, in its discretion, shall procure the right to continue using such product, or modify it so that it becomes noninfringing, or remove it and grant Customer a credit for the depreciated value thereof. Fairchild's indemnity does not extend to claims of infringement arising from Fairchild's compliance with Customer's design, specifications and/or instructions, or the use of any product in combination with other products or in connection with a manufacturing or other process. The foregoing remedy is exclusive and constitutes Fairchild's sole obligation for any claim of intellectual property infringement and Fairchild makes no warranty that products sold hereunder will not infringe any intellectual property rights.

All solutions, designs, schematics, drawings, boards or other information provided by Fairchild to Customer are confidential and provided for Customer's own use. Customer may not share any Fairchild materials with other semiconductor suppliers.